

Hybrid model for transistors at low frequency

H- Parameters

→ Vacuum Tubes before BJT

↓
Analysis

① Z-Parameters \Rightarrow Impedance parameters

② Y-Parameters \Rightarrow Admittance parameters

→ Transition to \rightarrow 1947

By using these parameters, analysis became problematics.


③ Third parameter developed?

H- Parameters
(Hybrid)

Mix of constants with diff units

H-Parameter

* → are applicable for two port network

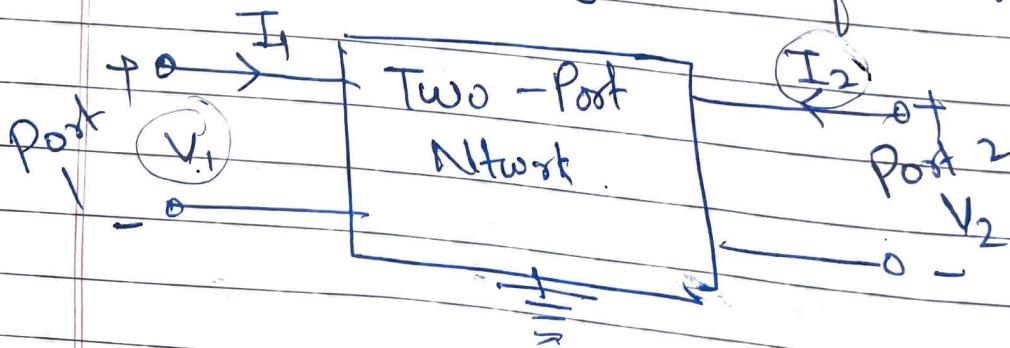

- In BJT \rightarrow it is considered to be as 2-port network in any config.
- 4 terminals
- Estimation of BJT became easier using H-Parameter.
- * → Mix of constants having different units
- * → $V_1, I_1, V_2 \& I_2$ are total current & voltages (AC & DC both).
(By using these, we will check the parameter)
- AC signal is superimposed on DC sig.

→ Fundamental Relationship b/w Dependable

$V_1 \& I_2$ = Dependable Variable.

Functions

Relation \rightarrow $V_1 = f(I_1, V_2) \Rightarrow I_1 \& V_2$ are independent variables
 $I_2 = f(V_1, I_1)$

For Small Signal operation.

charge in voltage $\rightarrow dV_1 = \frac{\partial V_1}{\partial I_1} dI_1 + \frac{\partial V_1}{\partial V_2} dV_2$ - (1)
rate of change of voltage small signal impedance ratio of reverse vtg.

Coh. \rightarrow $dI_2 = \frac{\partial I_2}{\partial I_1} dI_1 + \frac{\partial I_2}{\partial V_2} dV_2$ - (2)

" current $\rightarrow dI_2 = \frac{\partial I_2}{\partial I_1} dI_1 + \frac{\partial I_2}{\partial V_2} dV_2$ - (2)
F. c. gain output admittance current ratio

$$dV_1 = h_{11} dI_1 + h_{12} dV_2 \quad (1)$$

$$dI_2 = h_{21} dI_1 + h_{22} dV_2 \quad (2)$$

change in v_{tg}

$$\begin{cases} V_1 = h_{11} i_1 + h_{12} V_2 & (3) \\ i_2 = h_{21} i_1 + h_{22} V_2 & (4) \end{cases}$$

equations

$$\begin{cases} V_1 = h_{11} i_1 + h_{12} V_2 & (3) \\ i_2 = h_{21} i_1 + h_{22} V_2 & (4) \end{cases}$$

$$(3) i_2 = h_{21} i_1 + h_{22} V_2 \quad (4)$$

Applicable for all co
we have to find out value of

$h_{11}, h_{12}, h_{21}, h_{22}$

det $\begin{vmatrix} V_2 & -1 \\ i_2 & 0 \end{vmatrix} = 0$, IOP, \Rightarrow S.C. for A.C.

$$V_1 = h_{11} i_1 \quad \text{consid.}$$

$$h_{11} = \frac{V_1}{i_1}$$

$$h_{11} = \frac{V_1}{i_1} \Rightarrow \frac{V_1}{i_1} = \frac{V_1}{V_2} \times \frac{V_2}{i_1} \Rightarrow \frac{V_2}{i_1} = \frac{V_2}{V_1} \times \frac{V_1}{i_1} = \frac{V_2}{V_1} \times h_{11}$$

Impedance (Ω)
Unit

When $V_2 = 0$

$$i_2 = h_{21} v_1 \quad \text{denoted by } h_f$$

$$h_f = h_{21} = \left. \frac{i_2}{v_1} \right|_{V_2=0} \Rightarrow \text{Forward current gain}$$

Now $i_1 = 0 \rightarrow I/P \rightarrow 0.0 \text{ C for AC}$

$$v_1 = 0 + h_{12} v_2$$

$$h_{12} = h_{12} = \left. \frac{v_1}{v_2} \right|_{i_1=0} \Rightarrow \text{Reverse voltage gain}$$

$$i_2 = 0 + h_{22} v_2$$

$$h_o \Rightarrow h_{22} = \left. \frac{i_2}{v_2} \right|_{i_1=0} \Rightarrow \text{Output Admittance (mho)}$$

$\text{Impedance} = \frac{v_2}{i_2}$

Now,

$$v_1 = h_i i_1 + h_{12} v_2$$

$$i_2 = h_f i_1 + h_o v_2$$

$h_i = \text{Input Impedance} = \Omega$

$h_{12} = \text{const quant} = R \cdot V.G$

$h_f = \text{dimension less}$

$h_o = \text{Siemens}$

different
units
so hybrid.

Now for C-E config.

$$h_f \Rightarrow h_{fe}$$

$$h_f \Rightarrow h_{je}$$

$$h_\infty \Rightarrow h_{ee}$$

$$h_0 \Rightarrow h_{oe}$$

⇒ Manufacturer provides h -values,
they are not interchangeable

⇒ Conditional parameters

⇒ Popular model dynamic I/P resist

By using
h-parameter

$$\begin{bmatrix} e_i \\ i_o \\ A_i \\ A_o \end{bmatrix} \rightarrow \text{can be calc. of m.a.}$$

gain

H-parameter Equivalent ckt

$$v_1 = h_{11} i_1 + h_{12} v_2 \quad (1)$$

$$i_2 = h_{21} i_1 + h_{22} v_2 \quad (2)$$

Dependent Variable

Dependent on calculate h

→ Matrix Representation.

$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$

h-para matrix

2x1

2x2

2x1

↓ Independent Variable

$$v_1 = h_1 i_1 + h_{21} v_2 \quad (3)$$

Reverse VTG ratio.

$$i_2 = h_2 i_1 + h_0 v_2 \quad (4)$$

OP Admittance.

→ By using these two equation, the make equivalent model \Rightarrow II-Model.

Equation (3) resistance current.

$$v_1 = \frac{h_1 i_1}{\downarrow V} + \frac{h_{21} v_2}{\downarrow V} \quad (\text{Voltage})$$


Use eq (3) to KVL, for eq (3)

ASSUMPTIONS

Date _____
Page _____

$V_1 = \text{det I/P voltage}$

$h_{ij} = \text{Resistance}$

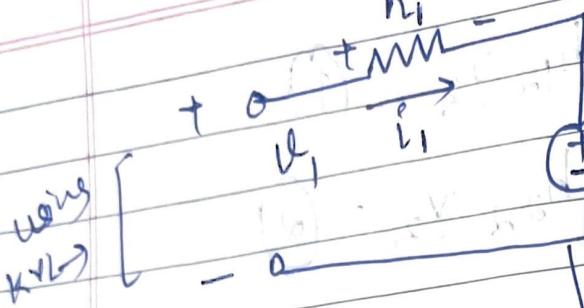

$h_{21}V_1 \rightarrow \text{Voltage Source}$

$$+V_1 - h_1^i i_1 - h_{21}V_2 = 0$$

$$V_1 = h_1^i i_1 + h_{21}V_2$$

- (3)

Same

Voltage controlled

Vtg source

because in 2-port network
Output O/P Vtg is V_2

Now eq (4)

Different form, i.e.

Current form.

$$i_2 = h_{21}i_1 + h_{22}V_2$$

For h_{21}

Admittance

current ratio

(Reciprocal

Invert \rightarrow Dimensionless

of Resistance


or Impedance)

$$i = \frac{V}{R}$$

$$= \frac{V}{1/R} \rightarrow \text{wta.}$$

$$i = VR = V_2 h_{22}$$

Use KCL for eq 4,

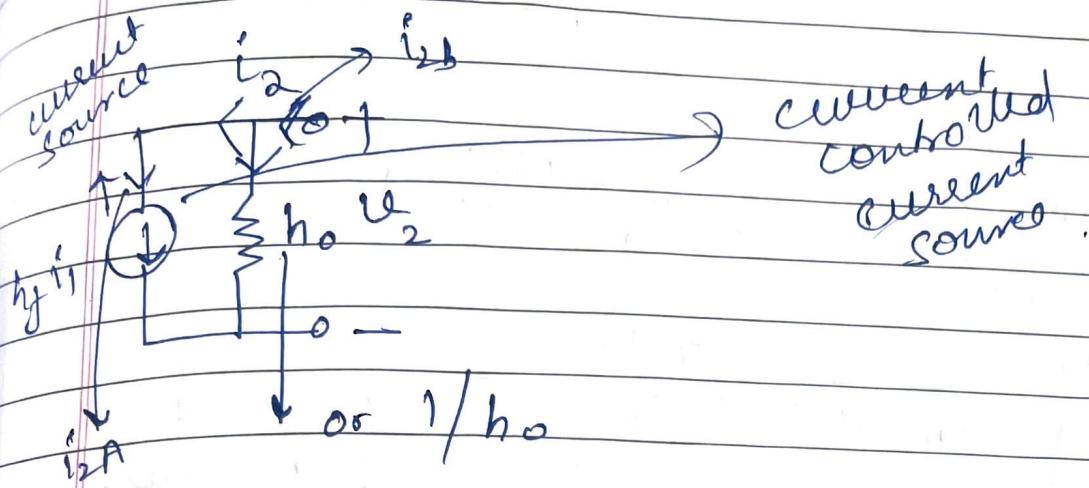


$$i_2 = i_{2a} + i_{2b} \quad h_o = \text{Admittance}$$

$$= h_f i_1 + \frac{v_2}{1/h_o} \rightarrow \text{impedance.}$$

$$i_2 = h_f i_1 + h_o v_2$$

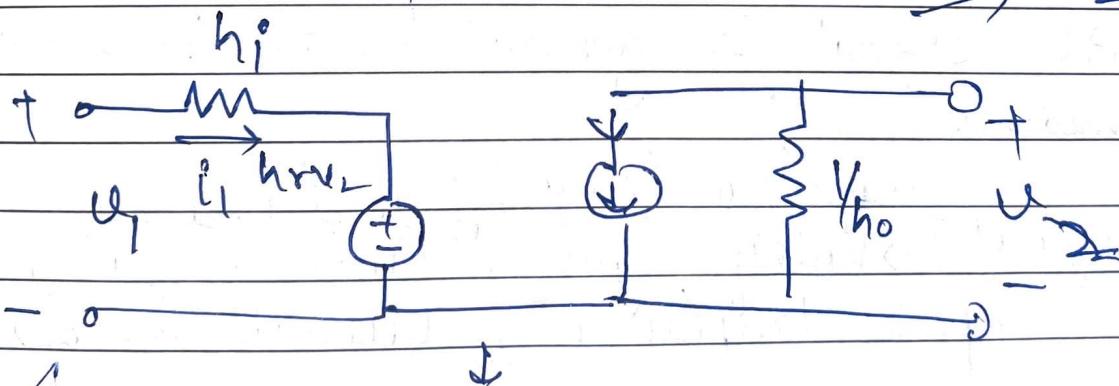Now, Equivalent Model. $\rightarrow \pi\text{-model}$




Generalised model for all config.
Join

Current source dependent on i_1

& V_{tg} " dep on v_2



Replace transi by h -model.

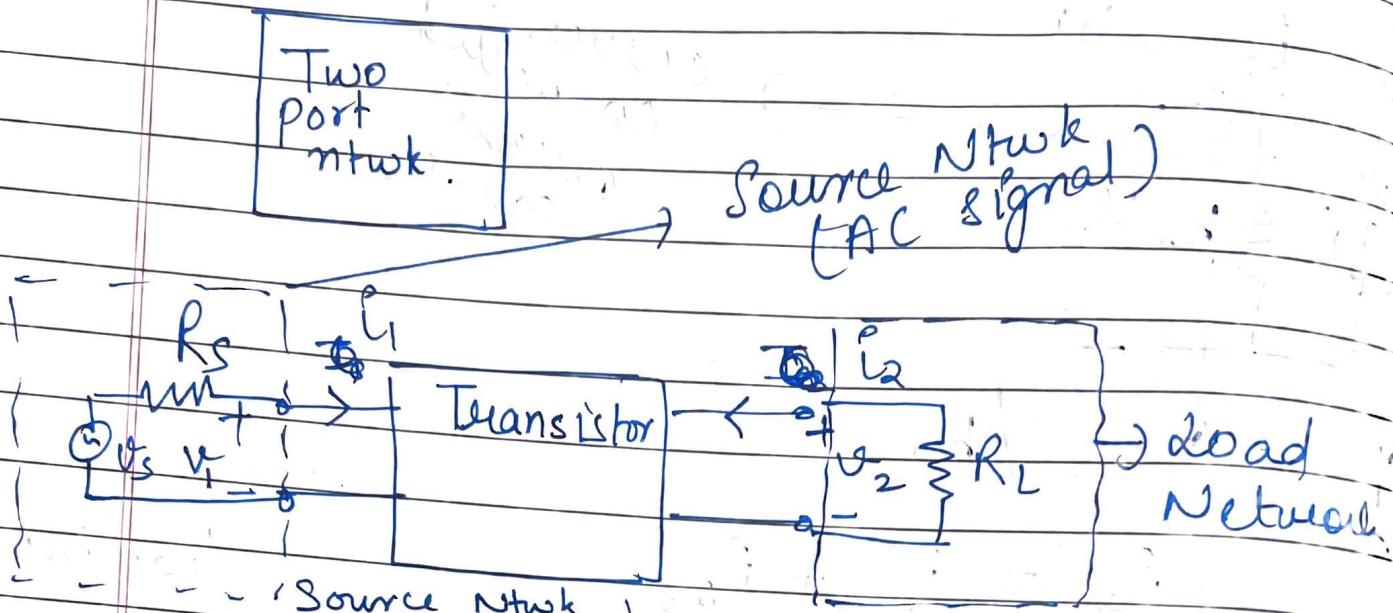Small Signal Amplifier using h - Parameter



1. Transformer is also 2 - Port Network.

$$R_s = \text{Ext Source}$$

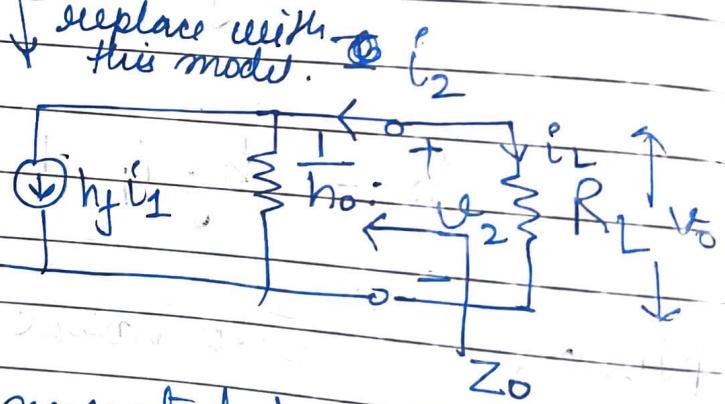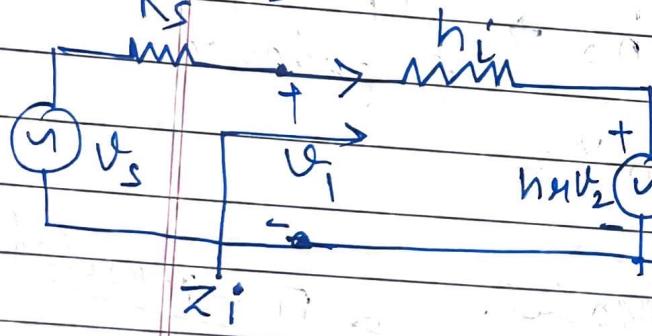

- AC signal is generated from Generator, transducer

- For Transistor (Amplifier) find Parameters.
- Analysis of 1 → Voltage gain, Current gain, Input Impedance, Output Impedance

- (1) Voltage Gain
- (2) Current gain
- (3) Input Impedance
- (4) Output Impedance

$\rightarrow \text{Indep}$

$$\begin{cases} V_1 = h_i i_1 + h_o V_2 - \textcircled{1} \\ i_2 = h_f i_1 + h_o V_2 - \textcircled{2} \end{cases}$$

Al ready
found

Dependent variable
h-parameters are provided by
manufactures. $h_i, h_r, h_f \& h_o \Rightarrow$ Non-Parameters
 \rightarrow we have to find

i_1, V_1, i_2, V_2 \Rightarrow Unknown Parameters.

① Voltage Gain

$$A_V = \frac{\text{O/P vfg}}{\text{I/P vfg}} = \frac{V_2}{V_1}$$

$$\Rightarrow V_2 = V_o = i_L R_L \quad (\text{From circuit})$$

direction of i_L is opp to i_2

$$V_2 = -i_2 R_L$$

$$\boxed{i_2 = -\frac{V_2}{R_L}}$$

Put value of i_2 in eq $\textcircled{2}$

$$-\frac{V_2}{R_L} = h_f i_1 + h_o V_2$$

$$-\frac{V_2}{R_L} - h_o V_2 = h_f i_1$$

$$-\frac{v_2}{R_L} \left[\frac{1}{R_L} + h_o \right] = h_f i_1$$

$$i_1 = -\frac{v_2}{h_f} \left[h_o + \frac{1}{R_L} \right]$$

Put in eq ①

~~$$v_1 = h_i \left[-\frac{v_2}{h_f} \left(h_o + \frac{1}{R_L} \right) \right]$$~~

~~$\frac{-h_i}{h_f}$~~ + $h_{21} v_2$ - ②

We have to find out $\frac{v_2}{v_1}$

$$= -\frac{v_2 h_i}{h_f} \left(\frac{h_o R_L + 1}{R_L} \right) + h_{21} v_2$$

$$= -v_2 \left[\frac{h_i (h_o R_L + 1)}{h_f R_L} + h_{21} \right]$$

$$v_1 = -v_2 \left[\frac{h_i (1 + h_o R_L) + h_{21} h_f R_L}{h_f R_L} \right]$$


Voltage

$$\text{gain} = \frac{v_2}{v_1} = -\frac{h_f R_L}{h_i (1 + h_o R_L) + h_{21} h_f R_L}$$

A_V

This is called Exact Analysis

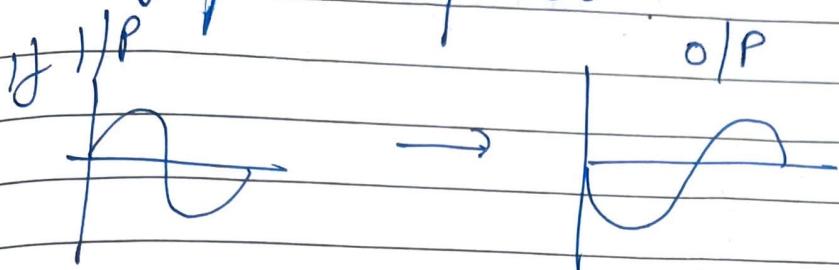Negative sign indicate that o/p vtg is out of phase by 180° .



Interest should be in eq ①

② Current Gain

$$A_i = \frac{i_L \rightarrow \text{output current}}{i_1 \rightarrow \text{I/P current}} = -\frac{i_2}{i_1}$$

In eq ②

v_2 = Unknown

we know

$$\Rightarrow V_o = i_L R_L$$

$$\Rightarrow V_2 = V_o = i_2 R_L \Rightarrow -i_2 R_L$$

$$V_2 = -i_2 R_L \quad \text{--- ①}$$

Put value in eq ②

$$i_2 = h_f i_1 + h_o V_2$$

$$i_2 = h_f i_1 + h_o (-i_2 R_L)$$

$$i_2 = h_f i_1 - h_o i_2 R_L$$

$$i_2 (1 + h_o R_L) = h_f i_1$$

$$A_{\text{v}} = \frac{i_2}{i_1} = \frac{h_f}{(1 + h_o R_L)}$$

$$A_{\text{v}}^o = -\frac{i_2}{i_1}$$

$$A_{\text{v}}^o = -\frac{h_f}{(1 + h_o R_L)}$$

for C-E conf

$$A_{\text{v}}^o = -\frac{h_{fe}^{\times}}{(1 + h_o R_L)} \text{ suffix}$$

③ Input Impedance

Z_i^o = Internal Input Impedance.

Z_i^o or R_i^o is same for low frequency

$$R_i^o = Z_i^o = \frac{V_1}{I_1} \Rightarrow \text{Unconditional}$$

From $V_1 = h_{ii_1} + h_{ov_2} - ①$
 $i_2 = h_{fi_1} + h_o v_2 - ②$
 $\Rightarrow V_2 = V_o = i_2 R_L$

$$V_2 = -i_2 R_L$$

$$i_2 = -\frac{V_2}{R_L}$$

Put value of i_2 in eq(2)

$$-\frac{v_2}{R_L} = h_f i_1 + h_o v_2$$

$$-v_2 \left(\frac{1}{R_L} + h_o \right) = h_f i_1$$

$$-v_2 \left(\frac{1 + h_o R_L}{R_L} \right) = h_f i_1$$

$$v_2 = \frac{-h_f i_1}{\left(\frac{1 + h_o R_L}{R_L} \right)}$$

$$v_2 = -\frac{h_f i_1 R_L}{1 + h_o R_L}$$

Put value of v_2 in eq(1)

$$v_1 = h_i i_1 + h_{o1} \left(-\frac{h_f i_1 R_L}{1 + h_o R_L} \right)$$

$$= i_1 \left(h_i - \frac{h_f h_{o1} R_L}{1 + h_o R_L} \right)$$

Input Impedance

$$Z_{in}^o = \frac{v_1}{i_1} = h_i - \frac{h_f h_{o1} R_L}{1 + h_o R_L}$$

Z_i depend
on R_L

For C-E, suffix e


(4)

Output Impedance

$$Z_o = ?$$

Independent Source will be reduced to zero.

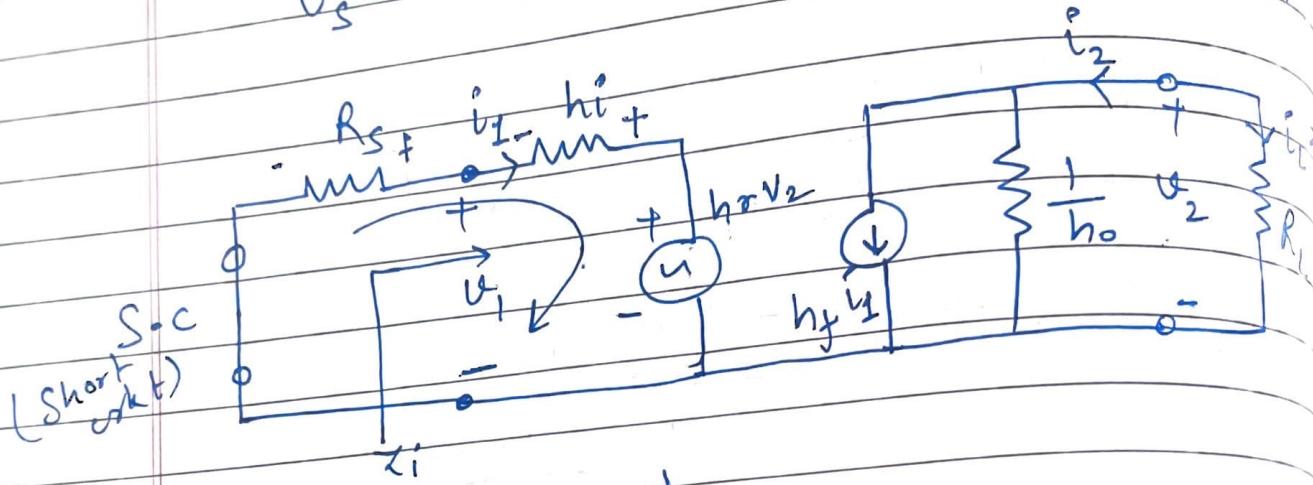$v_s = \text{Independent Source} = 0 = \text{Short circuit}$



$$Z_o = \frac{v_o}{i_2} \quad \text{when } v_s = 0$$

use
know
that

$$\begin{cases} v_1 = h_i i_1 + h_{f1} v_2 & -\text{(1)} \\ i_2 = h_{f1} i_1 + h_o v_2 & -\text{(2)} \end{cases}$$

find out

Apply KVL to IIP section,

$$0 + i_1 R_s + i_1 h_i + h_r v_2 = 0$$

$$i_1 (h_i + R_s) = -h_r v_2$$

$$i_1 = \frac{-h_r v_2}{h_i + R_s}$$

Put value of i_1 in eq (2)

$$i_2 = h_f \left(\frac{-h_{re}v_2}{h_i + R_s} \right) + h_o v_2$$

$$= v_2 \left[\frac{-h_{re}h_f}{h_i + R_s} \right] + h_o$$

$$Y = \frac{i_2}{v_2} \Rightarrow \boxed{\left[h_o - \frac{h_{re}h_f}{h_i + R_s} \right]}$$

output

$$\text{Impedance } Z_o = \frac{v_2}{i_2} = \frac{1}{h_o - \frac{h_{re}h_f}{h_i + R_s}}$$

for C-E conf.

$$Z_o = \frac{1}{h_{oe} - \frac{h_{re}h_{fe}}{h_i + R_s}}$$

\Rightarrow Exact Values \Rightarrow Exact Analysis
of Small signal
transistor