

# Digital Electronics

Electronics refers to a study of flow of electrons and its dynamics.

Digital Electronics

Analog  
Electronics

Digital electronics

$$(0,1) \cdot A + A = (0+A)(A+1)$$

1 → True → ON → Activate,  
 0 → False → OFF → Deactivate.

$$1 \cdot A + 0 \cdot A = (1+A)A$$

George Boole introduced Boolean Algebra

Boolean Algebra consists of

- Basic Laws
- Theorems

## Basic Laws of Boolean Algebra

$$A + A = A \quad \boxed{\text{idempotency law}}$$

$$A \cdot A = A$$

$$A + 1 = 1$$

$$A + 0 = A$$

$$A + \bar{A} = 1 \quad (\text{Full Set})$$

$$A \cdot \bar{A} = 0 \quad (\text{Null set})$$

$$\bar{\bar{A}} = A \quad (\text{double inversion})$$

Date \_\_\_\_\_

## Boolean theorems

### ~~Boolean theorems~~

#### ~~De Morgan's theorems~~

##### 1) De Morgan's theorem

De Morgan's theorem works on the principle  
to change the sign and break the bar.

$$(i) \bar{A} \cdot \bar{B} = \bar{A} + \bar{B}$$

$$(ii) A + B = \bar{A} \cdot \bar{B}$$

##### 2) Transposition theorem

$$(A + B)(A + C) = A + (B \cdot C)$$

##### 3) Distribution theorem

$$A + (B \cdot C) = (A + B)(A + C)$$

$$A(B + C) = A \cdot B + A \cdot C$$

~~A~~

##### 4) Consensus Theorem

→ It is used for elimination of redundant variable.

→ It contains 3 variables.

→ Only one variable is in complemented or uncomplemented form.

→ Then the related terms for that complemented or uncomplemented variable is the answer.

E.g.)  $f = \bar{A}$

$$Y(A, B, C) = AB + \bar{B}C + AC$$

$$= AB + \bar{B}C$$

$$\text{Q.2} \quad Y(A, B, C) = (A + \bar{B})(B + C)(A + C)$$

$$= (A + \bar{B})(B + C)$$

$$(A + \bar{B})(B + C) =$$

$$\text{Q.2} \quad Y(A, B, C) = AB + \bar{A}C + BC$$

$$= AB + \bar{A}C$$

Qn

(i)  $Y = AB + A\bar{B} + \bar{A}\bar{B}$

$$Y = B(\bar{A} + A) + \bar{A}\bar{B}$$

$$Y = B + \bar{A}\bar{B}$$

(ii)  $Y(A, B, C) = ABC + A\bar{B}C + A\bar{B}\bar{C}$

 ~~$= A\bar{C}(B + \bar{B}) + A\bar{B}\bar{C}$~~ 

$$= AC + A\bar{B}\bar{C}$$

(iii)  $Y = A + \bar{A}B + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}D$

~~$= (A + \bar{A})(A + B) + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}D$~~ 
 ~~$= A + B + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}D$~~ 
 ~~$= A + B + \bar{A}C$~~

~~$= A + \bar{A}(B + \bar{B}C + \bar{B}\bar{C}D)$~~

~~$= A + \bar{A}[(B + \bar{B})(B + C) + \bar{B}\bar{C}D]$~~

~~$= A + \bar{A}[B + C + \bar{B}\bar{C}D]$~~

~~$= A + \bar{A}[(B + \bar{B})(B + \bar{C}D) + C]$~~

~~$= A + \bar{A}[B + C + \bar{C}D]$~~

~~$= A + \bar{A}[B + (C + \bar{C})(C + D)]$~~

~~$= A + \bar{A}(B + C + D)$~~

Date \_\_\_\_\_

Qn

$$Y = \overline{(AB + C)}(\overline{A} + B + C)$$

$$Y = \overline{(AB + C)}(\overline{A} \cdot \overline{B} + C)$$

$$Y = AB \cdot \overline{A} \cdot \overline{B} + ABC + \overline{A} \overline{B} \overline{C} + C \overline{C}$$

$$Y = \overline{ABC} + \overline{ABC}$$

$$Y = \overline{ABC} + \overline{ABC}$$

$$Y = \overline{ABC} \cdot \overline{\overline{ABC}}$$

$$Y = (\overline{A} + \overline{B} + \overline{C}) \cdot (\overline{\overline{A}} + \overline{\overline{B}} + \overline{\overline{C}})$$

$$Y = (\overline{A} + \overline{B} + \overline{C}) \cdot (A + B + C)$$

Qn

$$Y = \overline{AC} [\overline{ABD}] + \overline{ABC\overline{D}} + A\overline{BC}$$

$$Y = \overline{AC} [\overline{A} + \overline{B} + \overline{D}] + \overline{ABC\overline{D}} + A\overline{BC}$$

$$Y = \overline{AC} [A + \overline{B} + \overline{D}] + \overline{ABC\overline{D}} + A\overline{BC}$$

$$Y = \overline{AAC} + \overline{AB} + \overline{ADC} + \overline{ABC\overline{D}} + A\overline{BC}$$

$$Y = \overline{AAC} + \overline{AB} + \overline{ADC}(1+B) + A\overline{BC}$$

$$Y = \overline{ABC} + \overline{ADC} + A\overline{BC}$$

$$Y = \overline{BC}(\overline{A} + A) + \overline{ADC}$$

$$Y = \overline{BC} + \overline{ADC}$$

$$Y = C(\overline{B} + \overline{AD})\overline{A} + A$$

Q Proof the following :-

$$BCD + A\bar{C}\bar{D} + ABD = BCD + \bar{A}\bar{C}\bar{D} + AB\bar{C}$$

Sol L.H.S =  $BCD + A\bar{C}\bar{D} + ABD$

L.H.S

$$BCD + A\bar{C}\bar{D} + ABD$$

$$= BCD + A\bar{C}\bar{D} + ABD(C + \bar{C})$$

$$= BCD + A\bar{C}\bar{D} + ABCD + AB\bar{C}\bar{D}$$

$$= BCD(1 + A) + A\bar{C}\bar{D}(\bar{D} + BD)$$

$$= BCD + A\bar{C}\bar{D}[(\bar{D} + B) \cdot (\bar{D} + D)]$$

$$= BCD + A\bar{C}\bar{D} + A\bar{C}B$$

R.H.S

Hence proved

~~B~~

If  $A\bar{B} + \bar{A}B = C$ , show that  $A\bar{C} + \bar{A}C = B$

Given :-  $A\bar{B} + \bar{A}B = C$

To Prove :-  $A\bar{C} + \bar{A}C = B$

$$\text{L.H.S} = A\bar{C} + \bar{A}C$$

$$= A[\overline{CAB} + \overline{\bar{A}B}] + \bar{A}[\overline{A\bar{B}} + \overline{\bar{A}B}]$$

~~$$= A[\overline{A\bar{B}} + \overline{\bar{A}B}] + \cancel{\bar{A}\overline{AB} + \bar{A}\bar{A}B}$$~~

$$= A[(\bar{A} + \bar{B})(\bar{A} + B)] + \bar{A}B$$

$$= A[(\bar{A} + B)(A + \bar{B})] + \bar{A}B$$

~~$$= A[\cancel{\bar{A}\bar{A}} + \cancel{\bar{A}\bar{B}} + AB + \cancel{BB}] + \bar{A}B$$~~

$$= A[\bar{A}\bar{B} + AB] + \bar{A}B$$

~~$$= \cancel{A\bar{A}B} + AAB + \cancel{\bar{A}B} -$$~~

$$= AB + \bar{A}B$$

$$= B(A + \bar{A})$$

~~$$(A + \bar{A})B + (A + \bar{A})\bar{A}B$$~~

~~$$= (A + \bar{A})(A + \bar{A})B + (A + \bar{A})\bar{A}B$$~~

$$= R.H.S$$

Hence Proved

Report and

R.H.S

### Ques. for Practice

Simplify the following expression using the Boolean Algebra :-

1.  $Y = \bar{A}B + AB + \bar{A}\bar{B}$
2.  $Y = ABC + A\bar{B}C + AB\bar{C}$
3.  $Y = \overline{(AB + \bar{C})} (\overline{A+B} + C)$

### Boolean Func<sup>n</sup> Representation

↓  
Std. form  
(Minimized form)

↓  
Canonical form

All the terms don't have each variables (literals)

All the terms contains each variables (literals)

e.g.  $F(A, B, C) = \bar{A}BC + ABC + A\bar{B}\bar{C}$

↓  
SOP

↓  
POS

↓  
sum of Product

↓  
product of sum

Canonical SOP form

(minterm SOP form)

Canonical POS form

(maxterm POS form)

## SOP Form

The SOP expression usually takes the form of two or more variables ANDed together

$$\text{e.g. } Y = \bar{A}BC + A\bar{B} + AC$$

$$Y = \bar{B}\bar{C}D + A\bar{B}D + CD$$

→ SOP form is used for construction of Truth Table and timing diagrams.

→ SOP circuits can be constructed using a special gate called "AND-OR-Inverter" gate.

### Canonical SOP form

(1) In this form, each term contains all the binary variables.

(2) Each term of this form is called min-term

\* (3) In minterm, we assign '1' to uncomplemented variable, and '0' to each complemented variable

(4)  $n$ - binary variables have  $2^n$  possible combinations and each of these combination is called minterm

(5) Minterms are represented by  $\Sigma m (----)$

(6) This form is used to write the logical expression only for those outputs which are "1"

No. of Possible combination of  $n$ -variables is  $2^n$

$$\text{e.g. } Y(A, B, C) = A + B + C$$

$$\text{No. of Possible combination} = 2^3 = 8$$

A	B	C	Minterm
0	0	0	$\bar{A} \bar{B} \bar{C} \rightarrow m_0$
0	0	1	$\bar{A} \bar{B} C \rightarrow m_1$
0	1	0	$\bar{A} B \bar{C} \rightarrow m_2$
0	1	1	$\bar{A} B C \rightarrow m_3$
1	0	0	$A \bar{B} \bar{C} \rightarrow m_4$
1	0	1	$A \bar{B} C \rightarrow m_5$
1	1	0	$A B \bar{C} \rightarrow m_6$
1	1	1	$A B C \rightarrow m_7$

Ques Find the minterms corresponding to decimal no. 5 and 13.

$$Y = \bar{A}(\bar{A} + A) + (\bar{A} + A)(\bar{B} + B) = Y$$

~~$$\text{Ans} \quad 00101 \rightarrow 101 \rightarrow A \bar{B} C$$~~

$$Y = \bar{A}(\bar{A} + A) + (\bar{A} + A)(\bar{B} + B) = Y$$

Ques Obtain the Canonical SOP form for the given Boolean func.

$$Y = \bar{A}(\bar{A} + A) + (\bar{A} + A)(\bar{B} + B) = Y$$

Find the total no. of minterms.

~~Sol<sup>m</sup>~~

$$Y(A, B, C) = A + BC$$

$$= A \cdot 1 \cdot 1 + 1 \cdot BC$$

$$= A(B + \bar{B})(C + \bar{C}) + (A + \bar{A})BC$$

$$= A(BC + B\bar{C} + \bar{B}C + \bar{B}\bar{C}) + ABC + \bar{A}\bar{B}C$$

$$= (ABC + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C}) + (ABC) + (\bar{A}\bar{B}C)$$

$$= AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + ABC + \bar{A}\bar{B}C$$

$\therefore$  Total no. of minterms = 5

$$Y(A, B, C) = \sum m(6, 5, 4, 7, 3)$$

$$Y(A, B, C) = \sum m(3, 4, 5, 6, 7)$$

~~Q<sup>m</sup>~~

Find the no. of min-terms in Canonical SOP form for the given Boolean fun<sup>n</sup>:-

$$Y(A, B, C) = A + \bar{B}C$$

$$Y = A(\bar{B} + B)(\bar{C} + C) + (\bar{A} + A)\bar{B}C$$

$$Y = A(\bar{B}\bar{C} + \bar{B}C + B\bar{C} + BC) + (\bar{A} + A)\bar{B}C$$

$$Y = A\bar{B}\bar{C} + A\bar{B}C + ABC + A\bar{B}C + \bar{A}\bar{B}C$$

$$Y = A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + ABC + \bar{A}\bar{B}C$$

$$Y = 100 + 1001 + 110 + 111 + 001$$

$$Y = \sum m(4, 5, 6, 7, 1)$$

B

Find the minimized SOP expression for the given Truth Table.

A	B	Y
0	0	1✓
0	1	0
1	0	1✓
1	1	0

Soln

$$\begin{aligned} Y(A, B) &= \bar{A}\bar{B} + A\bar{B} \\ &= \bar{B}(\bar{A} + A) \end{aligned}$$

$$(1+3)8A + (2+4)8A + \bar{B}8A = Y$$

C

Find the minimized SOP expression for the given truth table of 3-Variable Boolean func<sup>n</sup>

Inputs      output

A	B	C	Y
0	0	0	
0	1	0	
1	0	0	
1	1	0	

$$(1+3)8A + (2+4)8A + \bar{B}8A = Y$$

$$2A + 6A + 0 - 2\bar{B} = 0$$

$$2A + 6A + 17A = 0$$

$$2A + 17A = 0$$

$$2A + (17A) = 0$$

Date \_\_\_\_\_

I/PO/P

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$Y = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

3, 5, 6, 7

Q

$$Y = \bar{A}BC + A\bar{B}C + AB\bar{C} + C$$

$$Y = \bar{A}BC + A\bar{B}C + AB\bar{C}$$

~~$$Y = (\bar{A}B + A\bar{B})C + AB$$~~

$$= \bar{A}BC + A[B + \bar{B}C]$$

$$= \bar{A}BC + A[(B + \bar{B})(B + C)]$$

$$= \bar{A}BC + A(B + C)$$

$$= \bar{A}BC + AB + AC$$

~~$$= B[A + \bar{A}C] + AC$$~~

$$= B[(A + \bar{A})(A + C)] + AC$$

$$= B(A + C) + AC$$

$$= AB + BC + AC$$

## Product of Sum (POS) form

The POS expression usually takes the form of two or more ORed variables within parenthesis ANDed with two or more other variables within Parenthesis.

e.g.  $\Sigma M(A, B, C, D, E) = (A + \bar{C}) \cdot (\bar{B} + E) \cdot (B + C)$

→ Each individual term in Canonical POS form is called Maxterm

→ POS forms are used to write logical expression for o/p becoming logic '0'.

→ In maxterm, we assign '0' to uncomplemented variable and '1' to complemented variables.

→ Maxterms are represented by  $\Pi M(-----)$

~~Q^M~~ Find the max term corresponding to decimal no. 5 and 13

~~sol<sup>M</sup>~~  $5 \rightarrow 101 \rightarrow (\bar{A} + B + \bar{C})$

~~answT x 011 + answT w/ 11 = answT so ans w/ 11~~  $13 \rightarrow 1101 \rightarrow (\bar{A} + \bar{B} + C + \bar{D})$

Principle of duality

Q^M

obtain the Canonical POS form for  
the given expression:-

$$Y(A, B, C) = (A + \bar{B})(B + C)(A + \bar{C})$$

Sol^n

$$(A + \bar{B} + 0)(0 + B + C)(A + 0 + \bar{C})$$

$$= (A + \bar{B} + C \cdot \bar{C})(A \cdot \bar{A} + B + C)(A + B \cdot \bar{B} + \bar{C})$$

$$= (A + \bar{B} + C \cdot \bar{C})(B + C + A \cdot \bar{A})(A + C + B \cdot \bar{B})$$

$$= (A + \bar{B} + C)(A + \bar{B} + \bar{C})(B + C + A)(B + C + \bar{A})$$

$$(A + C + B)(A + C + \bar{B})$$



$$= (A + \bar{B} + C)(A + \bar{B} + \bar{C})(A + B + C)(\bar{A} + B + C) + \\ (A + B + C)(A + \bar{B} + C)$$

$$= (A + \bar{B} + C)(A + \bar{B} + \bar{C})(A + B + C)(\bar{A} + B + C)$$

010            011            (000)            (100)

No. of Max Terms = 4

$$Y(A, B, C) = \prod M(2, 6, 0, 4)$$

$(\bar{A} + B + \bar{C}) \leftarrow 101$

Total no. of Terms = Min Terms + Max terms

$(\bar{A} + B + \bar{C} + \bar{A} + \bar{B}) \leftarrow 1011$

$$= \sum m(1, 3, 5, 7)$$

[�लन के लिए]

~~Q^M~~ Express the Boolean func<sup>n</sup>

$$Y(A, B, C) = A + \bar{B}C$$

in Canonical POS form

$$Y(A, B, C) = (A + 0 + 0) + (0 + \bar{B}C)$$

$$Y(A, B, C) = (A + B \cdot \bar{B} + C \cdot \bar{C}) + (A \cdot \bar{A} + \bar{B}C)$$

$$Y(A, B, C) = ((A+B)(A+\bar{B})(A+C)(A+\bar{C}))$$

$$Y(A, B, C) = A + \bar{B}C$$

$$= (A + \bar{B})(A + C)$$

$$Y = (A + \bar{B} + 0)(A + 0 + C)$$

$$Y = (A + \bar{B} + C \cdot \bar{C})(A + B \cdot \bar{B} + C)$$

$$Y = (A + \bar{B} + C)(A + \bar{B} + \bar{C})(A + B + C)$$

( $A + \bar{B} + C$ )

$$\tau(A, B, C) = \text{LTM}$$

$$(1, M, T) = (2, 0, A) Y$$

$$Y = (A + \bar{B} + C)(A + \bar{B} + \bar{C})(A + B + C)$$

$$Y = \text{LTM}(2, 3, 0)$$

010 011 000

$$(A + \bar{B} + C) \rightarrow \bar{A}BC$$

$$(A + \bar{B} + \bar{C}) \rightarrow (\bar{A}B\bar{C})$$

$$(A + B + C) \rightarrow (\bar{A}\bar{B}\bar{C})$$

Q3

For the given truth table, obtained the minimized expression

A	B	Y
0	0	1
0	1	0 ✓
1	1	0 ✓

$$(A+B) \cdot (B+\bar{A}) + (A\bar{B}) + (\bar{A}\bar{B}) = (A+B)(\bar{A}\bar{B})$$

Sol  $Y(A, B) = (A + \bar{B}) \cdot (\bar{A} + \bar{B})$

$$\bar{A}\bar{B} + \bar{B} = \cancel{A}\cancel{\bar{A}} + \bar{A}\bar{B} + \bar{A}\bar{B} + \bar{B}\bar{B}$$

$$(A+B)(\bar{B}+A) = A\bar{B} + \bar{A}\bar{B} + \bar{B}$$

$$= \bar{B}(\bar{A}+1) + AB$$

$$(A+B)(A+\bar{B}+A) = \bar{B} + A\bar{B}$$

$$= \bar{B}(1+A)$$

$$(A+\bar{B}+A)(\bar{A}+\bar{B}+A) = \bar{B}$$

$$(A+\bar{B}+A)(\bar{A}+\bar{B}+A)(A+\bar{B}+A) = Y$$

Q4 Find the no. of MAX Terms for the given Truth Table.

$$Y(A, B, C) = \prod M(?)$$

$$(A+B)(\bar{A}+\bar{B}+A)(\bar{A}\bar{B}+A)$$

$$(D, E, S) \in T = Y$$

000 110 010

$$SAA \leftarrow (A + \bar{B} + A)$$

$$(BA\bar{A}) \leftarrow (\bar{A} + \bar{B} + A)$$

$$(A\bar{B}\bar{A}) \leftarrow (A + B + A)$$


I/P			O/P
A	B	C	Y
0	0	0	0 ✓
0	0	1	0 ✓
0	1	0	0 ✓
0	1	1	1 ✓
1	0	0	0 ✓
1	0	1	1
1	1	1	1

$$Y(A, B, C) = (A + B + C)(A + B + \bar{C}) \\ (A + \bar{B} + C)(\bar{A} + B + C)$$

$$Y(A, B, C) = \pi M(0, 1, 2, 4)$$

∴ Specified function is

Dem-11

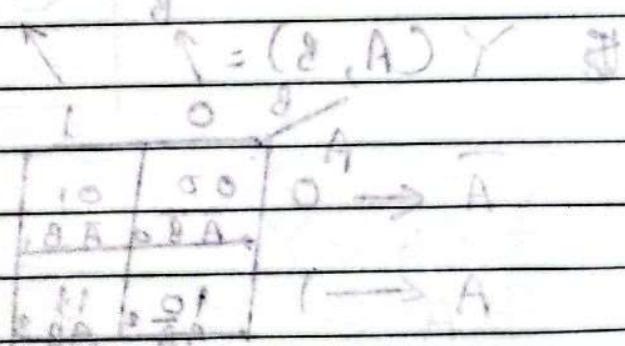

Ans

	Y	S	A
0	0	0	0
0	1	0	0

Ans Q/A  $\leftarrow$  83

Date \_\_\_\_\_

## K-Maps

- It is the graphical method for simplification of Boolean func.
- The func must be given in Canonical form to obtain the K-Map.
- K-Map can be constructed either for SOP or POS form.
- If a truth table is given then only those output will be considered for which the value is 1.
- For 'n' no. of variables, the no. of cells in the K-Map is always  $2^n$ .
- The value of each cell is obtained by gray code.


Two-variable K-Map

		$B$			
		0	1		
$\bar{A}$	0	00 AB <sub>0</sub>	01 AB <sub>1</sub>		
	1	10 AB <sub>2</sub>	11 AB <sub>3</sub>		

$2^n$

e.g. → AND Gate

A	B	Y
0	0	0
0	1	0

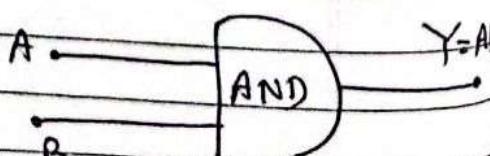

### Three - Variable K-Map

$$Y(A, B, C)$$

$$\text{No. of Cells} = 2^3 = 8$$

AB		C		0		1	
		00	01	00	01		
01	00	0	1				
	01	010	011				
11	00	2	3				
	11	110	111				
10	00	6	7				
	10	100	101	4	5		

e.g. → Minimize the given Boolean funcn using K-Map

$$Y(A, B, C) = A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}C + AB\bar{C}$$

$$(100 + 000 + 001 + 110)$$

AB		C		0		1	
		00	01	00	01		
01	00	1	1				
	01						
11	00	1	1				
	11						
10	00	1	1				
	10						

$$X = \bar{A}\bar{B} + A\bar{C}$$

Date \_\_\_\_\_

Q^n

Simplify the Boolean Expression -

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}Bc + A\bar{B}\bar{C}$$

AB	C	0	1
00		1	
01		1	1
10		1	0
11	1P		

$$\bar{A}\bar{C} + \bar{A}B +$$

AB	C	0	1
00	1P		
01		1	
10		1	
11		0	

$$\begin{array}{l} \cancel{\bar{A}\bar{C}} + \cancel{\bar{A}B} \\ \bar{A} + \bar{B} \end{array}$$

$$\bar{A}B + \bar{A}\bar{C} + \bar{B}\bar{C}$$

Four-Variable K-Map

$$Y(A, B, C, D)$$

$$\text{No. of cells} = 2^4 = 16$$

Date \_\_\_\_\_

Page no. \_\_\_\_\_

AB		00	01	11	10
		0000 0	0001 1	0011 3	0010 2
01		0100 4	0101 5	0111 7	0110 6
11		1100 12	1101 13	1111 15	1110 14
10		1000 8	1001 9	1011 11	1010 10

~~G'~~

Minimize the logic func' using K-Map

$$Y = ACD + ABD + B\bar{C}D$$

~~Soln~~ 
$$Y = A(B + \bar{B})CD + AB(C + \bar{C})D + (A + \bar{A})B\bar{C}D$$

$$= A(BCD + \bar{B}CD) + AB(CD + \bar{C}D) + AB\bar{C}D$$

$$+ \bar{A}B\bar{C}D$$

~~$$= ABCD + A\bar{B}CD + ABC\bar{D} + AB\bar{C}D + A\bar{B}\bar{C}D + \bar{A}B\bar{C}$$~~

$$Y = ABCD + A\bar{B}CD + AB\bar{C}D + \bar{A}B\bar{C}D$$

$$(1111) \quad (1011) \quad (1101) \quad (0101)$$

$$15 \qquad 11 \qquad 13 \qquad 5$$

$$Y = \sum m(5, 11, 13, 15)$$

$AB \backslash CD$	00	01	11	10
00	0	1	3	2
01	4	1	5	7
11	12	11	13	15
10	8	9	11	10

$$Y = B\bar{C}D + ABD + ACD$$

~~Q~~

Minimize the logic func

$$Y(A, B, C, D) = \sum m (0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$$

$$A\bar{B}\bar{C}D + A\bar{B}CD + AB\bar{C}D + ABCD = Y$$

$AB \backslash CD$	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1


$$A\bar{B}\bar{C}D + A\bar{B}CD + A\bar{B}C\bar{D} + A\bar{B}C\bar{D} + AB\bar{C}D + ABCD = Y$$

$$(1010) (1011) (1101) (1111) - Y$$

$$Z = E_1 \oplus E_2 \oplus E_3 \oplus E_4$$


$$(E_1, E_2, E_3, E_4) \in \Sigma^4 - Y$$

Date \_\_\_\_\_

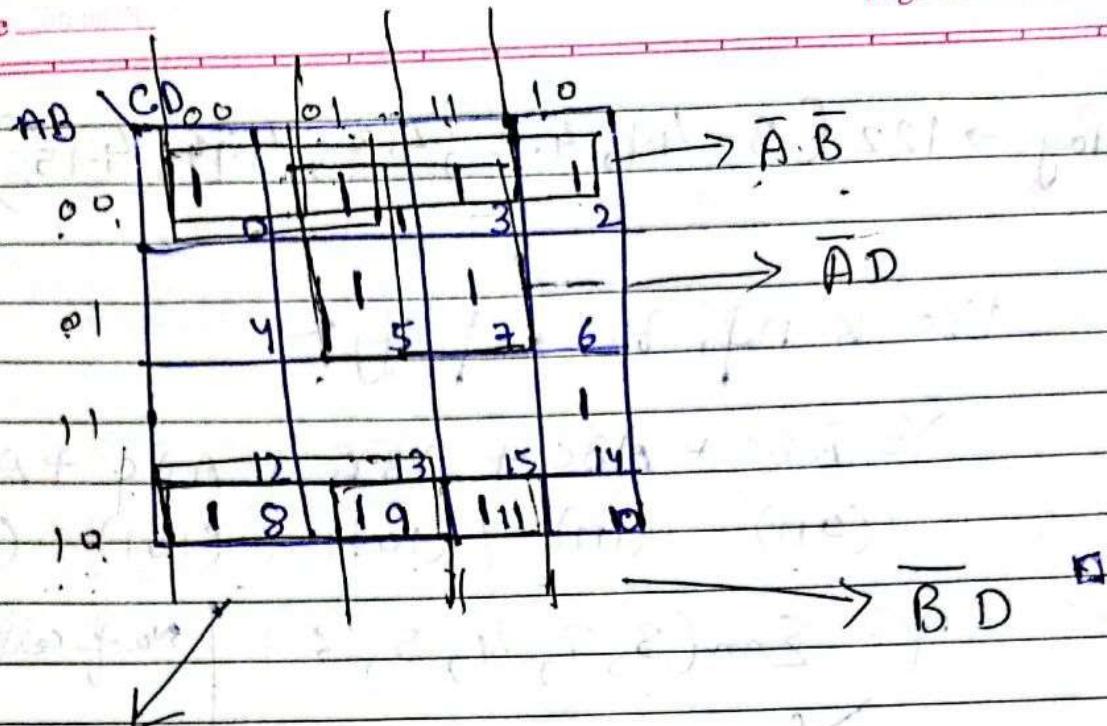

$$Y = \bar{A} \bar{B} + \bar{A}D + \bar{B}D + \bar{B}C$$

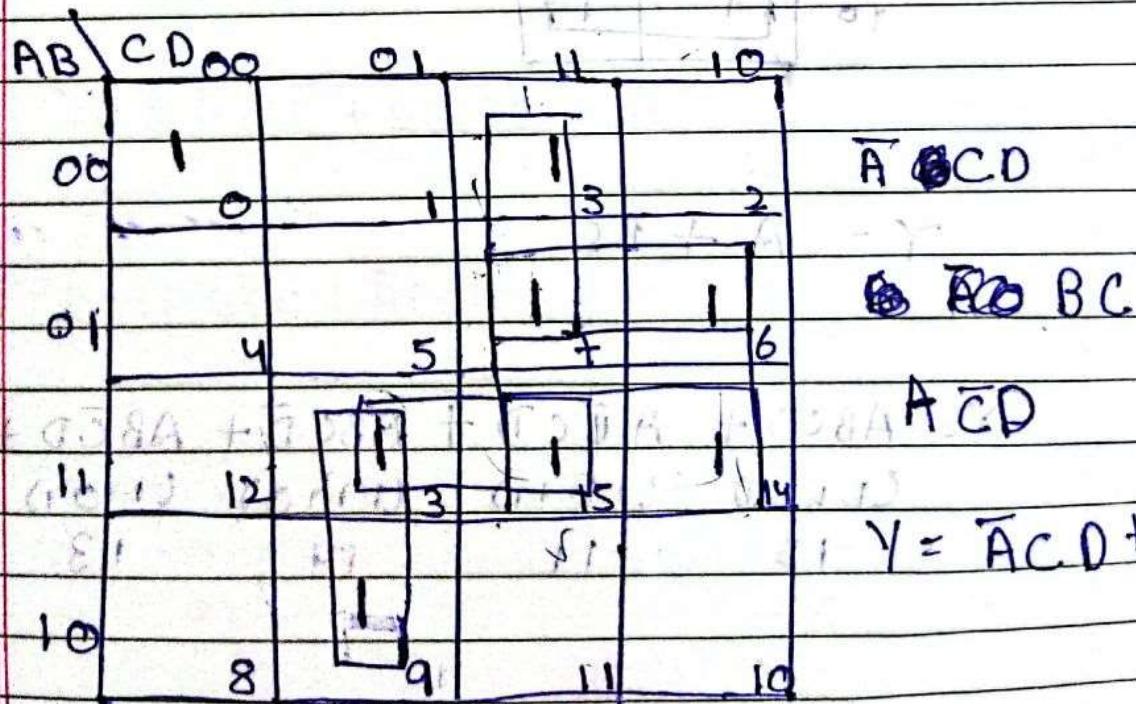(Q)  $f(A, B, C, D) = \sum m(0, 3, 6, 7, 9, 13, 14, 15)$



Page → 122 (Q - 4.1, 4.2, 4.3, 4.14, 4.15)

4.1


Use K-Map to simplify it

$$Y = \bar{A}BC + ABC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C}$$

(011)      (111)      (100)      (101)      (110)

~~f(x)~~

$$Y = \sum m(3, 7, 4, 5, 6) \quad \left| \begin{array}{l} \text{No. of cells} = 2^3 \\ = 8 \end{array} \right.$$

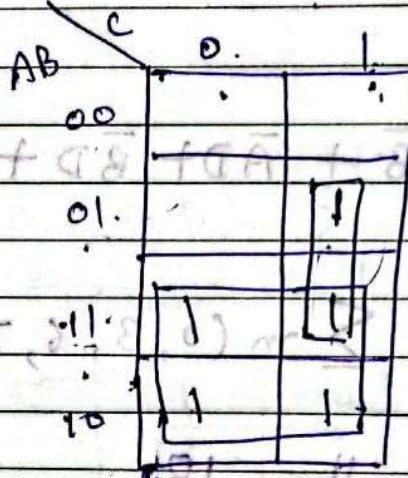

$$Y = A + BC$$

4.2

$$Y = ABCD + A\bar{B}CD + ABC\bar{D} + AB\bar{C}D + A\bar{B}\bar{C}D$$

(1, 1, 1, 1)      (1, 0, 1, 1)      (1, 1, 1, 0)      (1, 1, 0, 1)      (1, 1, 0, 0)

$$(1\bar{A} + 2A + 4\bar{A}) + 5\bar{A} = Y$$

$$15 = Y$$

$$\begin{matrix} 11 & 11 & 11 & 11 & 11 & 11 & 11 & 11 \\ 10 & 10 & 10 & 10 & 10 & 10 & 10 & 10 \\ 01 & 01 & 01 & 01 & 01 & 01 & 01 & 01 \end{matrix}$$

<del>AB</del>	<del>CD</del>	00	01	11	10	11
00	0	1	3	2		
01	4	5	7	6		
11	1	12	13	15	14	
10	8	9	11	10	Y	

$$Y = AB + AC \\ Y = AB + ACD$$

~~Q^2~~ Using Karnaugh map, simplify the given expression

$$Y = \bar{A} \bar{B} \bar{C} \bar{D} + A \bar{B} \bar{C} \bar{D} + \bar{A} B C + \bar{A} C \bar{D} \\ + \bar{A} \bar{C} \bar{D}$$

$$Y = \bar{A} \bar{B} \bar{C} \bar{D} + A \bar{B} \bar{C} \bar{D} + \bar{A} B C (D + \bar{D}) + \bar{A} (B + \bar{B}) C \bar{D} \\ + \bar{A} (B + \bar{B}) \bar{C} D$$

$$Y = \bar{A} \bar{B} \bar{C} \bar{D} + A \bar{B} \bar{C} \bar{D} + \bar{A} B C D + \bar{A} B C \bar{D} + \bar{A} B C \bar{D} + \bar{A} \bar{B} C \bar{D} + \bar{A} B \bar{C} \bar{D} \\ + \bar{A} \bar{B} \bar{C} \bar{D}$$

$$Y = \bar{A} \bar{B} \bar{C} \bar{D} + A \bar{B} \bar{C} \bar{D} + \bar{A} B C D + \bar{A} B C \bar{D} + \bar{A} \bar{B} C \bar{D} + \bar{A} B \bar{C} \bar{D} \\ (0000) (01000) (0111) (0110) (0010)$$

0      8      7      6      2

$$\bar{A} B \bar{C} D$$

$$(0100)$$

A	B	CD	00	01	11	10
00	0	0	1	2	1	2
01	1	4	5	1	1	6
11	12	13	15	14	1	1
10	1	8	9	11	10	1


$$Y = \bar{B}\bar{C}\bar{D} + \bar{A}BC + \bar{A}C\bar{D} + \bar{A}\bar{B}\bar{D}$$

Q

Find the minimized SOP expression for the given truth table :-

$$\bar{A}\bar{B}\bar{A} + \bar{A}\bar{B}A + \bar{A}\bar{B}\bar{A} = Y$$

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	0

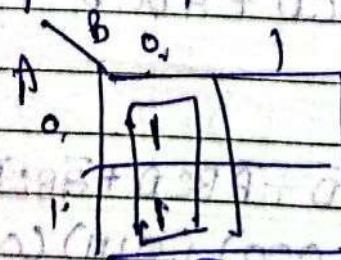

$$Y = \bar{B}$$

$$\bar{A}\bar{B}$$

$$(0010)$$

Date \_\_\_\_\_

$$Y = \sum m(3, 5, 6, 7)$$

Page no. \_\_\_\_\_


~~B'~~

Find the minimized SOP expression for the given truth table :-

Input (3 Variables)

Output

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

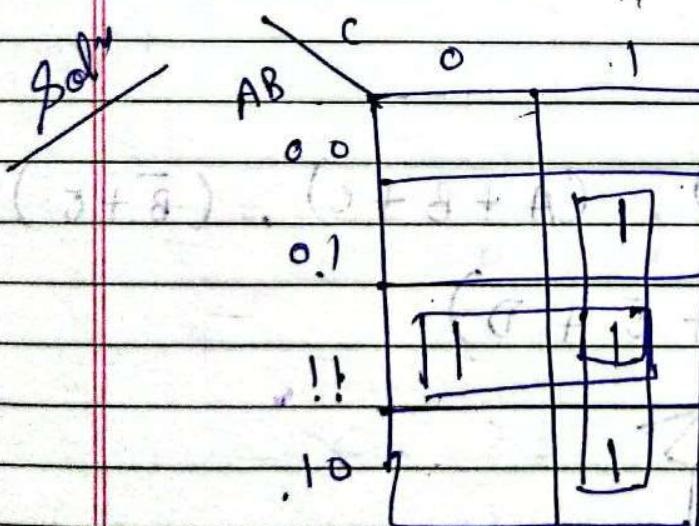

$$Y = (A+B)$$

$$Y = BC + A'B + AC$$

$$Y = (\bar{B}+\bar{C})(\bar{A}+\bar{B})(\bar{A}+\bar{C})$$

~~Q^M~~Simplify the Boolean func<sup>n</sup>

$$Y = \prod M (0, 1, 3, 5, 6, 7, 10, 14, 15)$$


$$= \cancel{\text{Sum}(0, 4, 8, 12, 13, 14, 15)} \rightarrow C(D)$$

AB

<del>CD</del>	00	01	11	10
<del>(A+B)</del>	0	0	0	1
<del>(A+\bar{B})</del>	1	0	1	0
<del>(\bar{A}+\bar{B})</del>	1	1	0	0
<del>(\bar{A}+B)</del>	0	1	1	1

$$Y = (A + \bar{D}) \cdot (A + B + C) \cdot (\bar{B} + \bar{C})$$

$$\cdot (\bar{A} + \bar{C} + D)$$

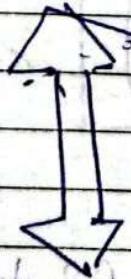

$$= \bar{A}D + \bar{A}\bar{B}\bar{C} + BC + ACD$$

the Boolean function

~~Q~~ Use K-Map to simplify ~~Y~~ using POS form.

$$Y = \overline{A}BC + ABC + A\overline{B}\overline{C} + A\overline{B}C + AB\overline{C}$$


3.      7.      4.      5.      6.

$$Y = (\underset{3}{A + \overline{B} + \overline{C}}) (\underset{7}{\overline{A} + \overline{B} + \overline{C}}) (\underset{4}{\overline{A} + B + C})$$

$$(\underset{5}{\overline{A} + B + \overline{C}}), (\underset{6}{\overline{A} + \overline{B} + C})$$

		C	$\overline{C}$
	AB	00	1
$(A+B)$	00	0	0
$(A+\overline{B})$	01	0	0
$(\overline{A}+B)$	11	0	0
$(\overline{A}+B)$	10	0	0

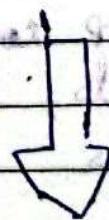So  $Y = (\overline{B} + \overline{C}) \cdot \overline{A}$



$$Y = BC + A$$

## Duality Theorem

- Any Boolean funcn can be represented either in SOP or POS form. If it is represented in SOP form, then each term is known as min-term and if it is represented in POS form, then each term is known as max-term.
- The POS form can be easily obtained with the help of SOP form by replacing complemented variables with uncomplemented variables and addition sign with multiplication sign and multiplication sign with add. It is known as duality property.

$$\sum m \text{ logically equiv. to } \prod M$$

## Don't care Conditions


- Some logic circuits can be designed so that there are certain i/p condns for which they are no specified levels, usually these i/p condns will never occur.
- A circuit designer is free to make the o/p for any don't care condn either a 0 or 1 in order to produce the simplest o/p expression.

Q3

Simplify - the given Boolean func<sup>n</sup>

$$F(A, B, C, D) = \sum_m(1, 3, 7, 11, 15)$$

$$+ \sum_d(0, 2, 5)$$

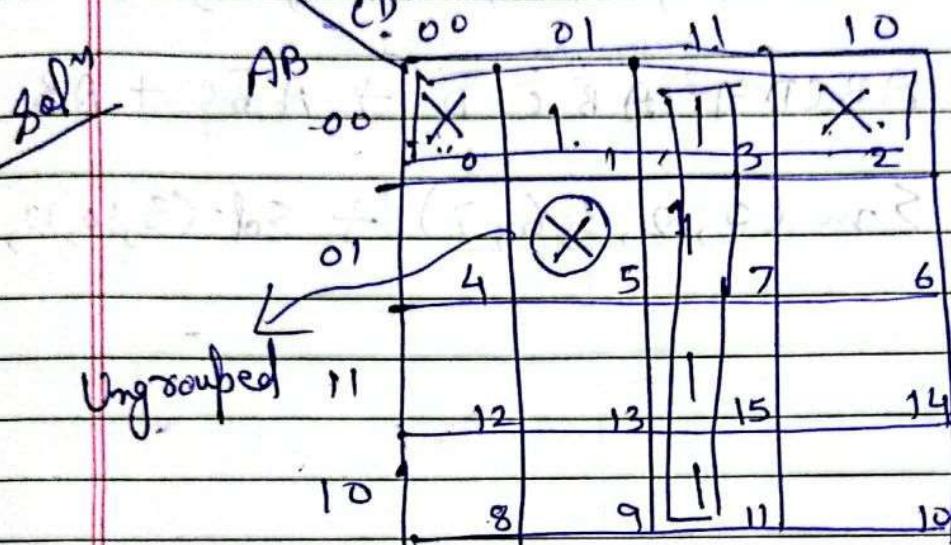

$$F = CD + \bar{A}\bar{B}$$

Note : → ① The don't care comb's are only used for simplification of K-Map by increasing '0's (for POS) and '1's (for SOP), ∵ we don't care the func's o/p for such combinations.

These comb's can be plotted on a map to provide further simplificn of the func<sup>n</sup>.

② Due to diff. groupings, the simplified expression for any given func<sup>n</sup> may not be unique but all the ~~from~~ expressions are logically equivalent since they have same value for every combination of Input Variable.

~~Q^M~~

Simplify the following expression:

$$(i) Y = \sum m (3, 4, 5, 7, 9, 13, 14, 15)$$

$$(ii) Y = \sum m (7, 9, 10, 11, 12, 13, 14, 15)$$

$$(iii) Y = ABCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}C + AB$$

$$(iv) Y = \sum m (0, 2, 3, 6, 7) + \sum d (8, 10, 11, 15)$$

$$\bar{A} + C = 1$$

Set how plus are 3 bits are each set of 3 bits

Final output for 3 bits to write 2 bits

set the first 3 bits of 4 bits in output

for one additional bit we have to take

one bit for shifting left by one bit

the last bit of 4 bits is shifting left by one bit

So we can get the required output


and so on and till we get the required output

thus we get the required output

## Logic Gates

- They are the most fundamental digital circuits that can be constructed from diodes, Transistors and Resistors.
- It is simply a device that has two or more inputs and one output.

### Logic Gates

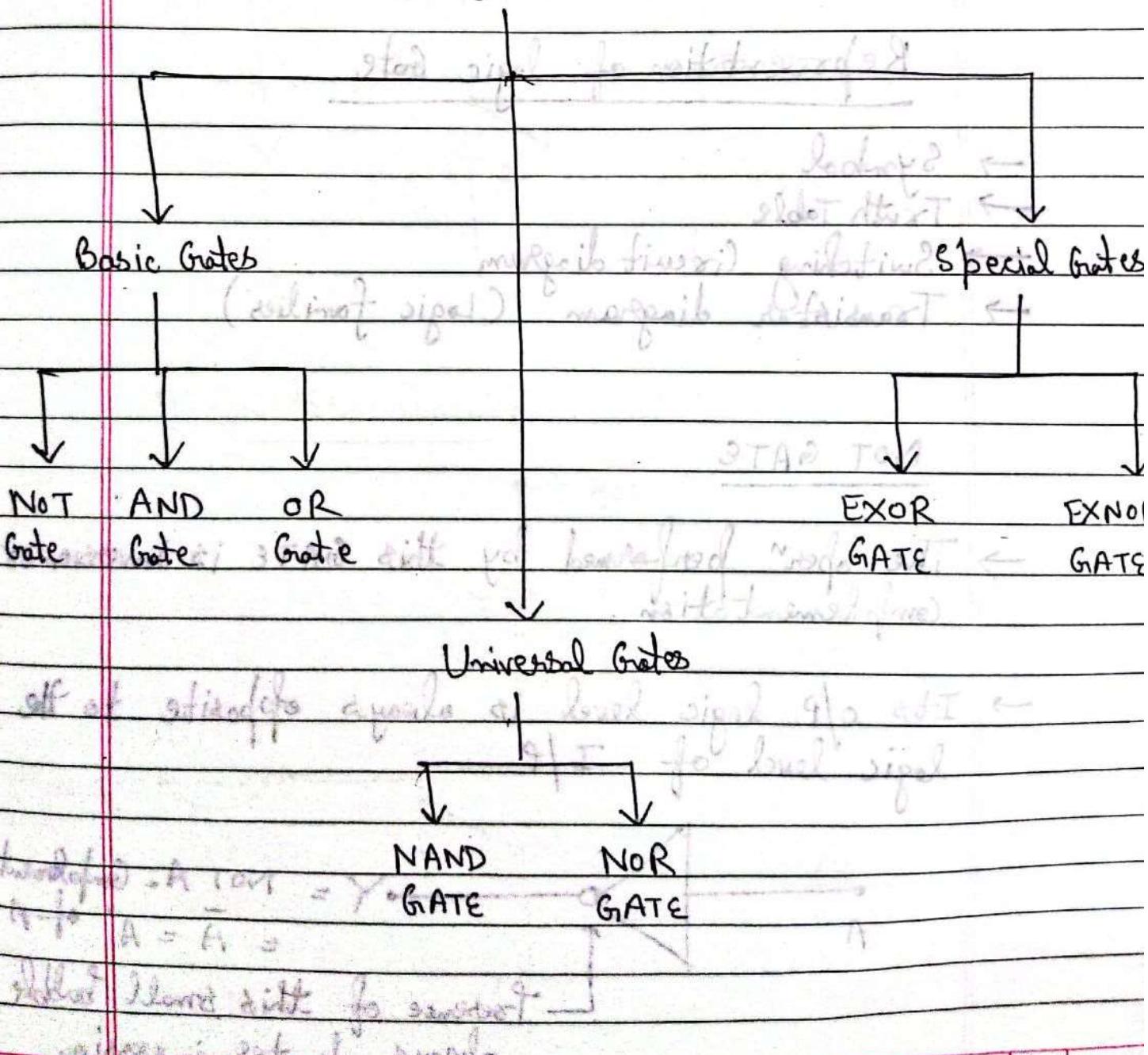

Boolean '0' and '1' represents the logic level.


<u>Logic '0'</u>	<u>Logic '1'</u>
FALSE	TRUE
OFF	ON
LOW	HIGH
No open Switch	YES closed switch

### Representation of logic Gate

- Symbol
- Truth Table
- Switching Circuit diagram
- Transistor diagram (Logic families)
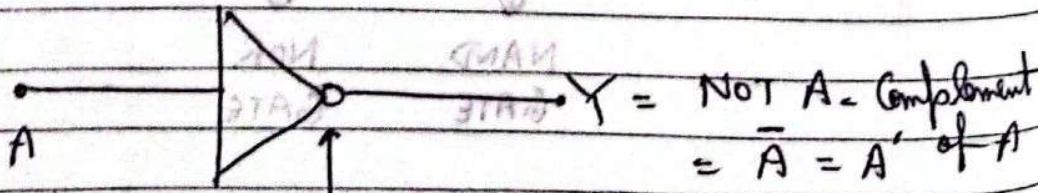
### NOT GATE



- The operation performed by this gate is inversion or complementation.
- Its o/p logic level is always opposite to the logic level of I/p




The presence of this small bubble always denotes inversion.

Truth Table


I/P	O/P
0	1
1	0

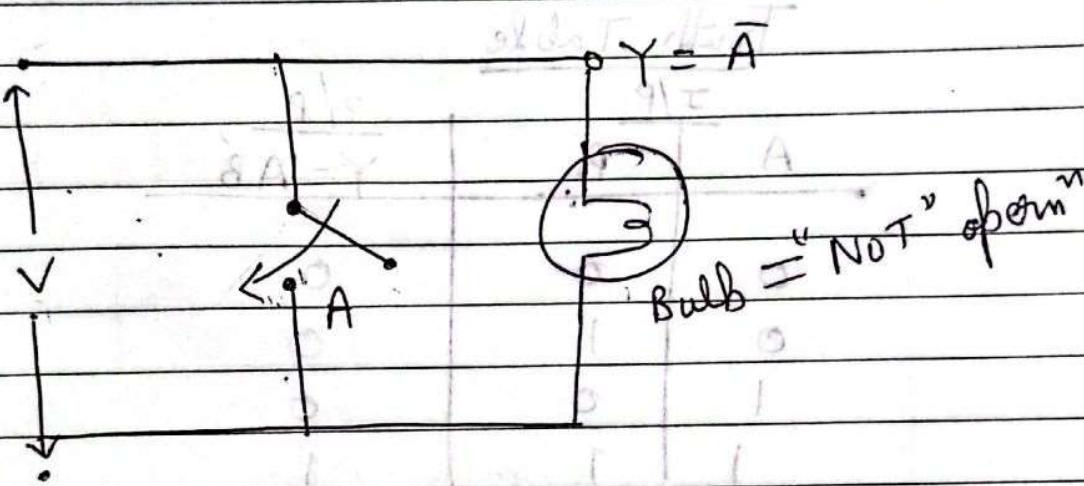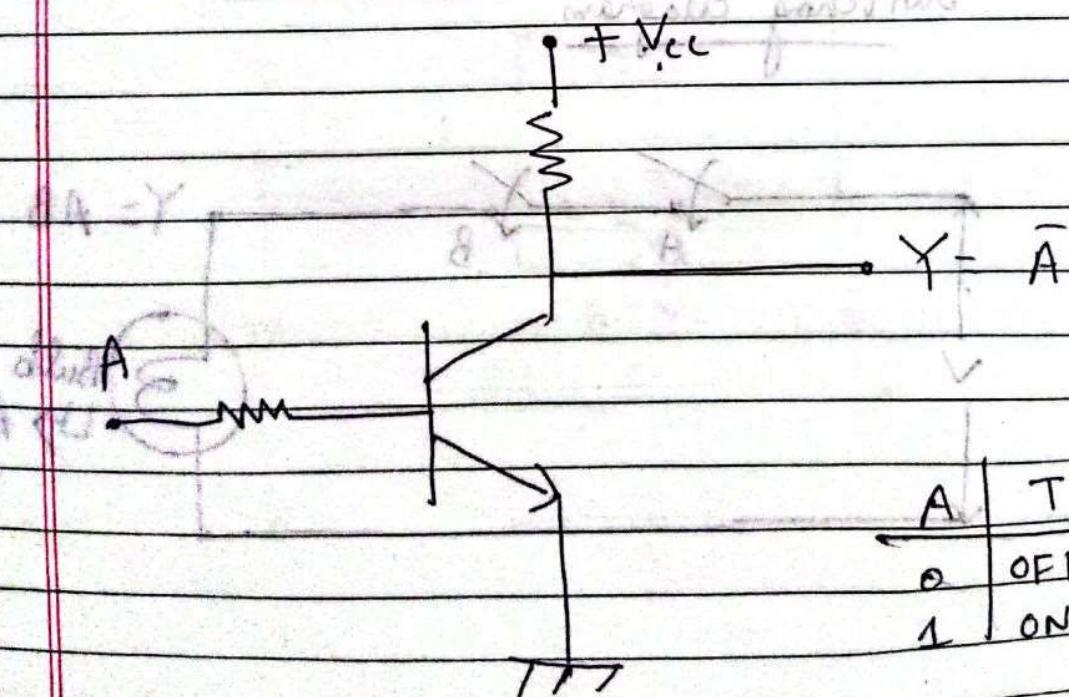
Switching Circuit diagram (Not Gate)Transistor Circuit

A	T	Y
0	OFF	V <sub>cc</sub> ≈ 1
1	ON	Ground = 0

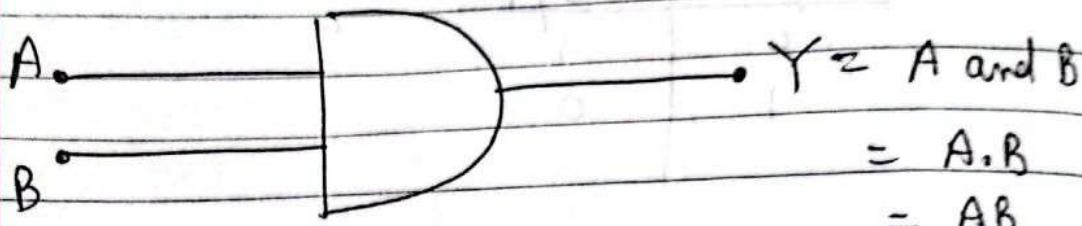AND GateSymbol :-Truth Table

I/P		O/P $Y = AB$
A	B	
0	0	0
0	1	0
1	0	0
1	1	1

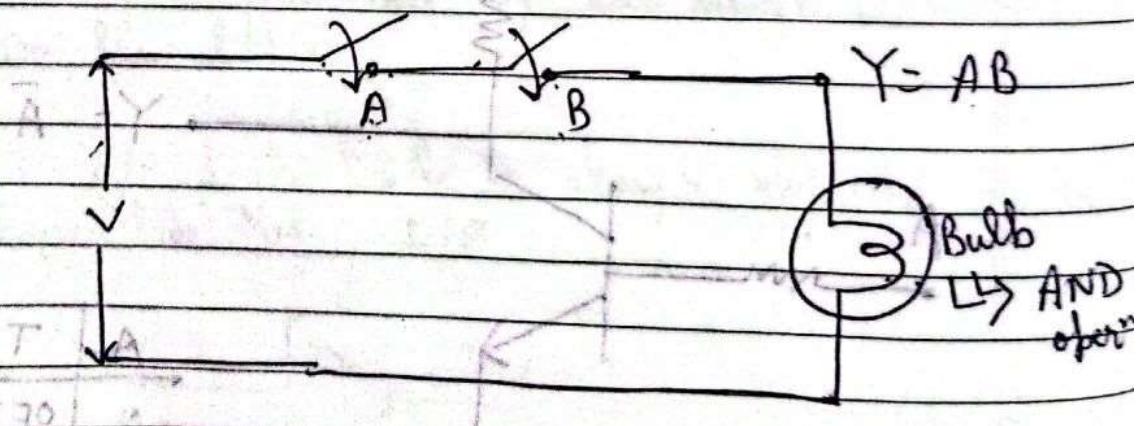
Switching diagram

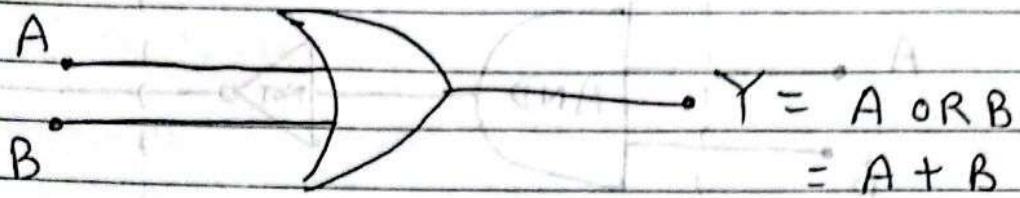OR GateSymbol :-InputsOutput


A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

A  $\oplus$  B = YSwitching diagram


(Bulb)

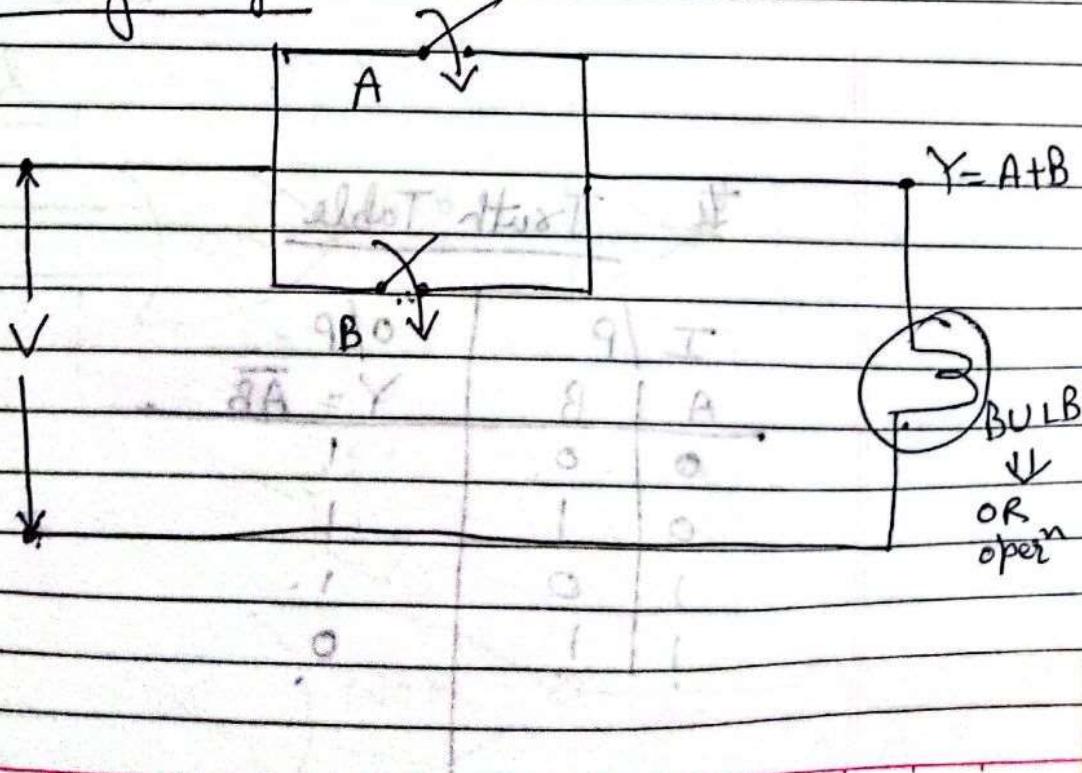

## 'NAND' GATE ("AND - NOT" oper)

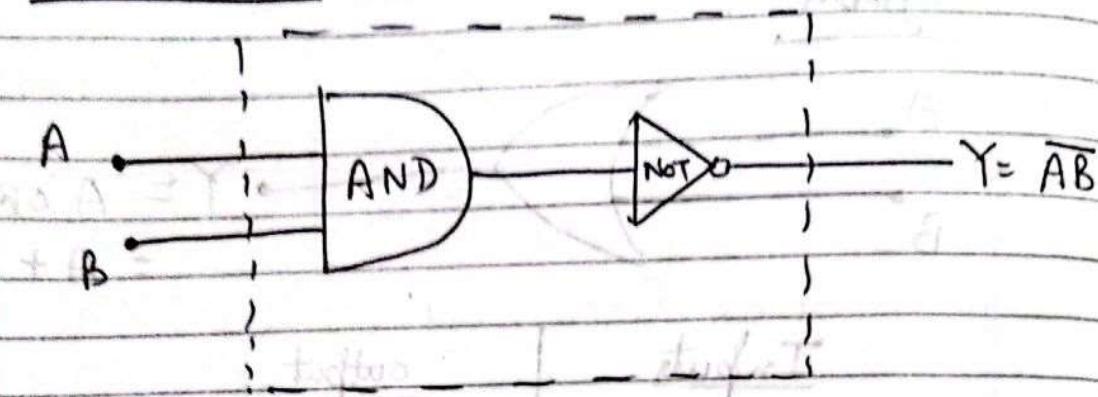

$\bar{A} + \bar{B} = Y$		$\bar{A}$	$\bar{B}$
0	1	1	0
1	0	0	1
0	0	1	1
1	1	0	0

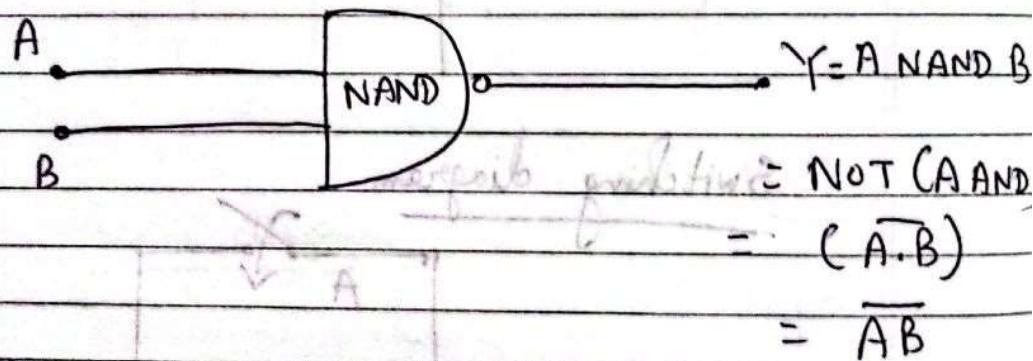

# Truth Table


I/P		O/P
A	B	$Y = \bar{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

→ "NAND gate" o/p goes low, when all of its inputs are high.

→ "NAND gate" o/p is the exact inverse of the AND gate for all possible i/p condns.


→ A single i/p "NAND gate" is equiv. to NOT gate.

### Switching Circuit diagram

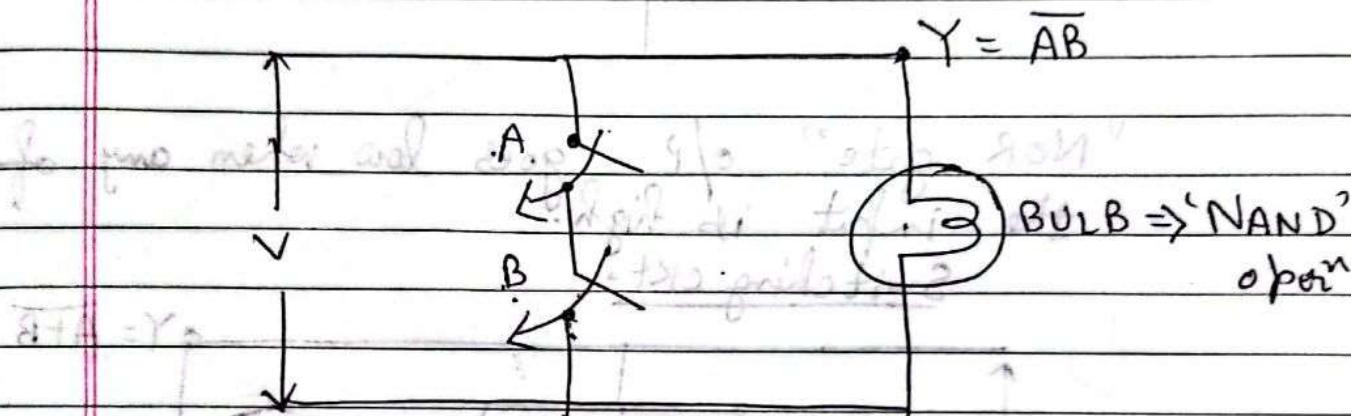


### NOR GATE

#### Symbol

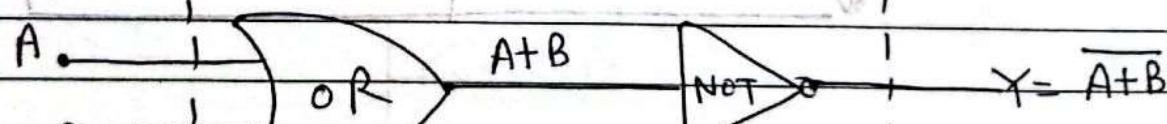

$$\bar{A} + \bar{B} + \bar{C} = Y$$

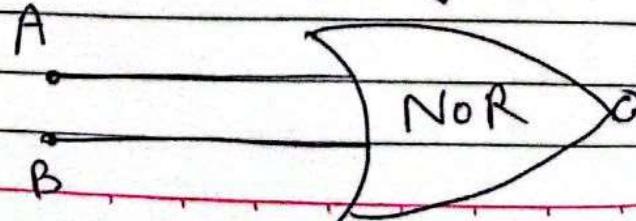

$$\begin{aligned}
 Y &= A \text{ NOR } B \\
 &= \text{NOT}(A \text{ OR } B) \\
 &= A + B
 \end{aligned}$$

# Truth Table

Date \_\_\_\_\_

Page no. \_\_\_\_\_


<u>I/P</u>		<u>O/P</u>
A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

$$\bar{A} \bar{B} = Y$$

"NOR gate" o/p goes low when any of the input is high.

Switching ckt.


$$Y = \bar{A} + \bar{B}$$

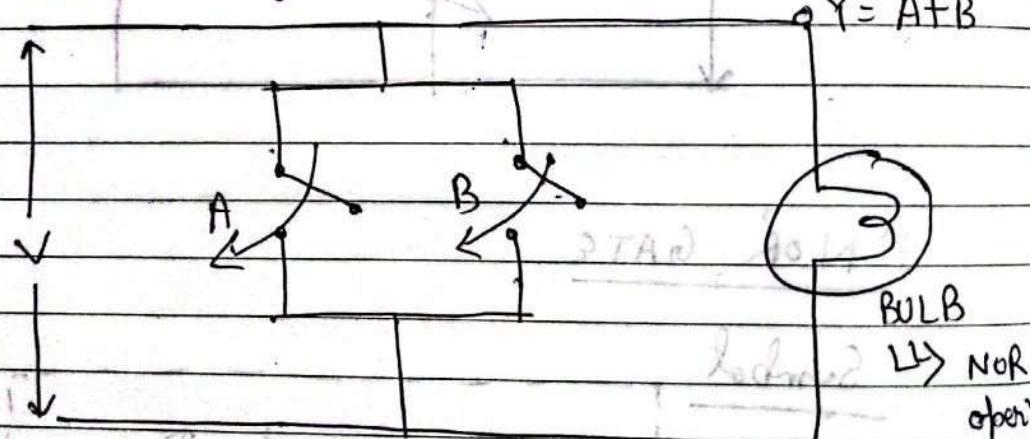


Q Realize the logic expression using basic gates

$$Y = \bar{B}\bar{C} + \bar{A}\bar{C} + \bar{A}\bar{B}$$

Date \_\_\_\_\_

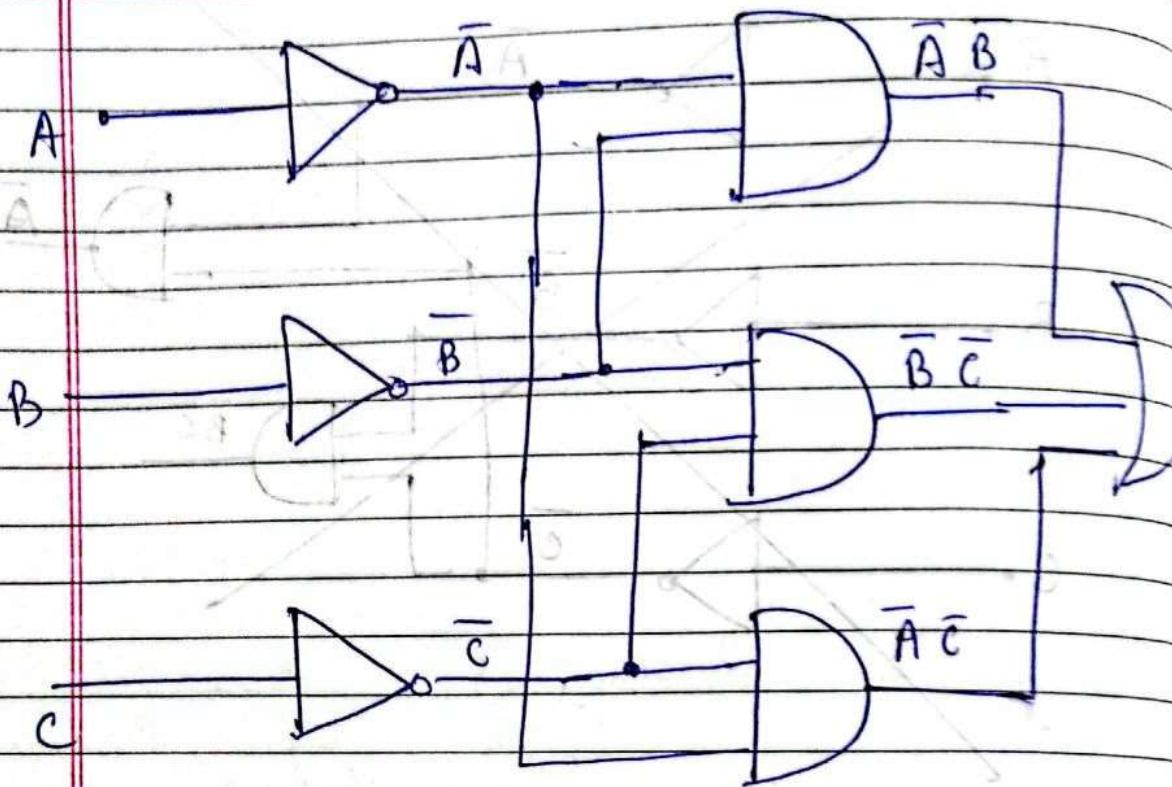

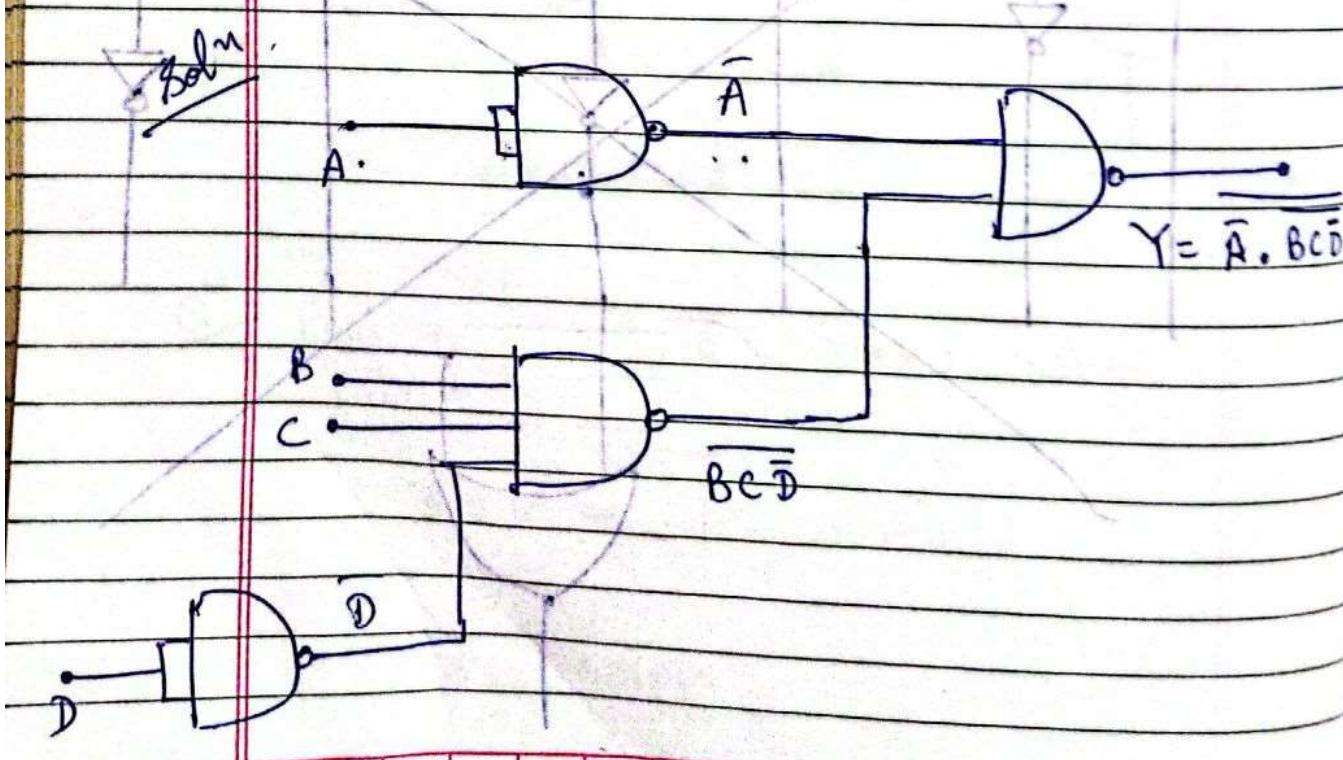~~B~~ Realise  $Y = A + BC\bar{D}$  using NAND gates only.




$$Y = \overline{\bar{A} \cdot BCD}$$

$$= \overline{\bar{A}} + \overline{BCD}$$

$$Y = \overline{\bar{A}} + \overline{BCD}$$

~~$$Y = \bar{A}\bar{B} + \bar{B}\bar{C} \\ + \bar{A}\bar{C}$$~~

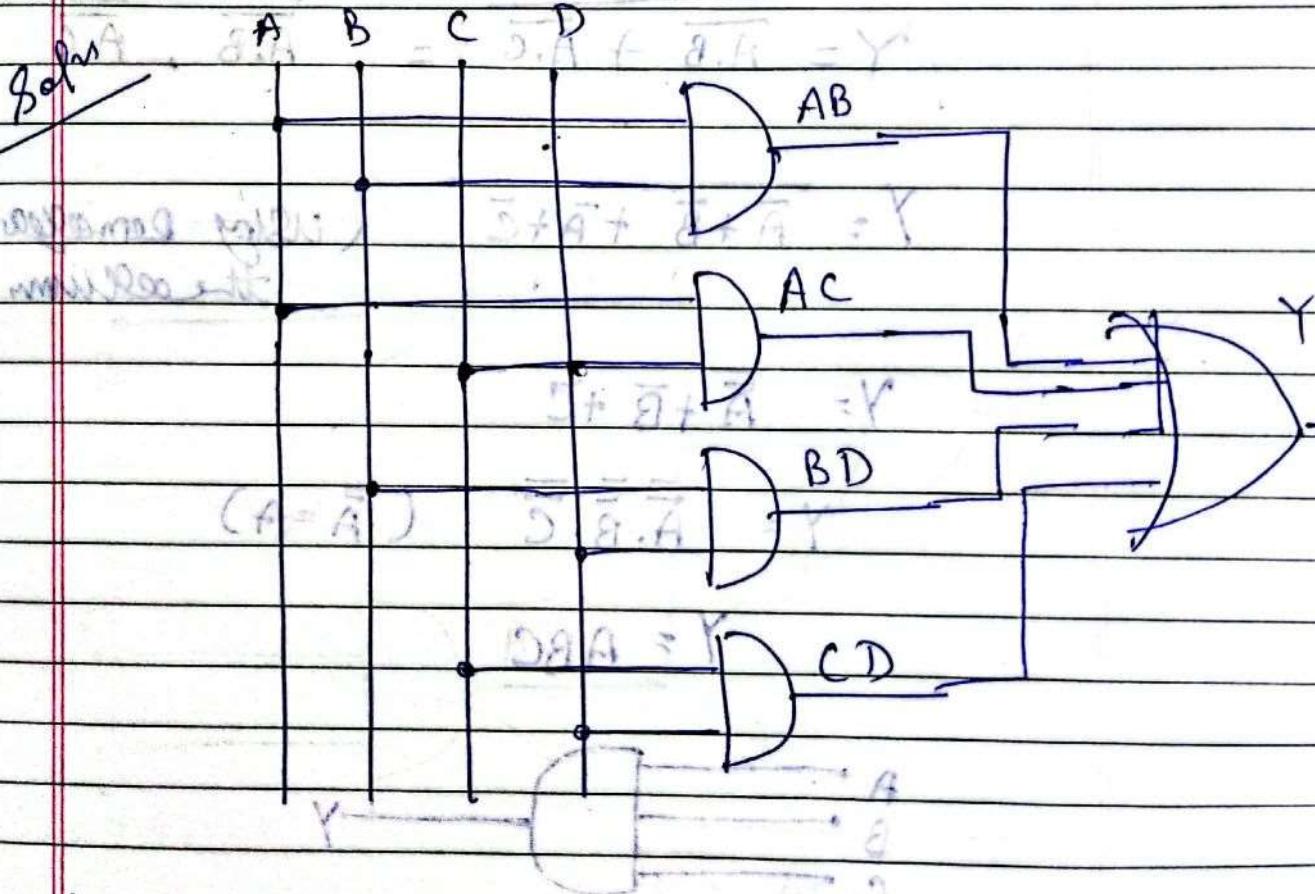Draw a logic circuit for the Boolean  
expr  $Y = AB + AC + BD + CD$



~~Q~~ Minimize the given expression and draw  
the logic circuit using basic gates.

$$Y = B \cdot (\bar{A} + \bar{C}) + \bar{A} \cdot \bar{B}$$

$$Y = \bar{A}B + B\bar{C} + \bar{A}\bar{B}$$


$$Y = \bar{A}(B + \bar{B}) + B\bar{C}$$

$$(A + \bar{A} = 1)$$

Date \_\_\_\_\_

$$Y = \bar{A} + BC$$

$$\bar{A} + \bar{B} \cdot \bar{C} = Y$$

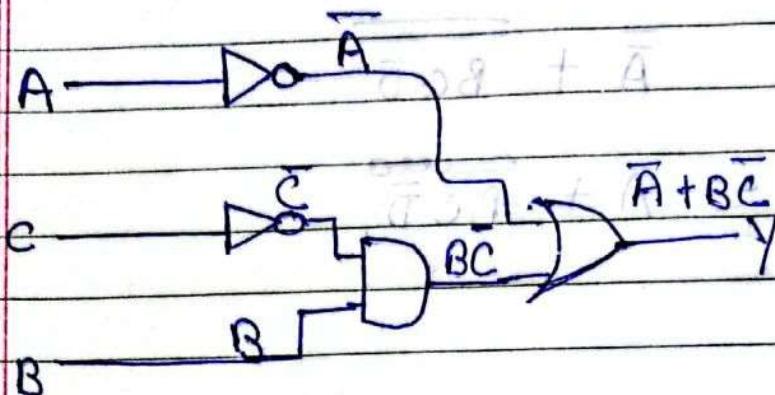~~B~~

~~Draw a circuit to realize the func-~~


$$Y = \overline{\overline{A} \cdot B} + \overline{\overline{A} \cdot C} = \overline{\overline{A} \cdot B} \cdot \overline{\overline{A} \cdot C}$$

$$Y = \bar{A} + \bar{B} + \bar{A} + \bar{C} \quad (\text{using DeMorgan's theorem})$$

$$Y = \bar{A} + \bar{B} + \bar{C}$$

$$Y = \overline{\overline{A} \cdot \overline{B} \cdot \overline{C}} \quad (\bar{A} = A)$$

$$Y = ABC$$

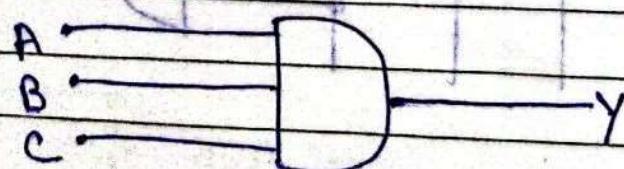

~~with help of DeMorgan's theorem with switching logic~~  
~~of logic gates guide this signal off~~



$$\bar{A} \cdot \bar{B} + (\bar{A} + \bar{B}) \cdot \bar{C} = Y$$

Date \_\_\_\_\_

8


$$A + (\bar{A} + B)A = Y$$

$$A + BA + \bar{A}A$$

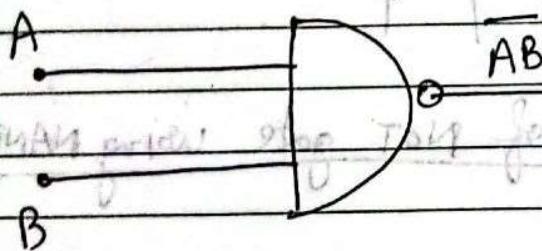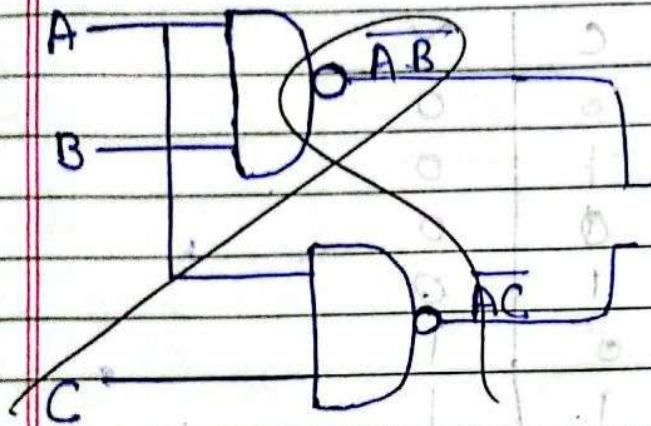

~~$\bar{A}B \cdot \bar{A}C$~~

$$\bar{A}B + \bar{A}C$$

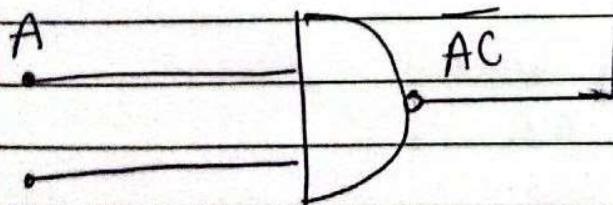

$$AC + A = A$$

$$\bar{A}B \cdot \bar{A}C = \bar{A}B + \bar{A}C$$

$$A \cdot A = B \cdot A$$

 $\bar{A}$

Date \_\_\_\_\_


Q3

Before Draw T.T for the following:-

$$Y = A(CB + C) + A \\ = AB + AC + A$$

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

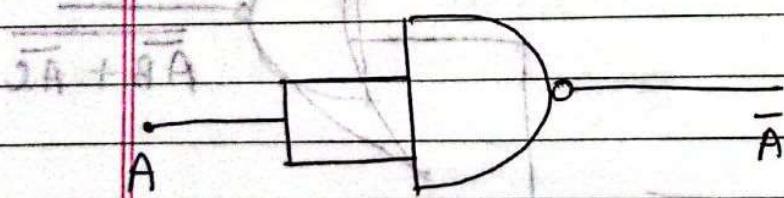Implementation of NOT gate using NAND gate



$$A = B = A$$

$$\bar{A} + \bar{A}A = \bar{A} \cdot \bar{A}$$


$$A \cdot B = \bar{A} \cdot A \\ = \bar{A}$$

Date \_\_\_\_\_

Q.

$$Y = \overline{AB} + A + (B+C)$$

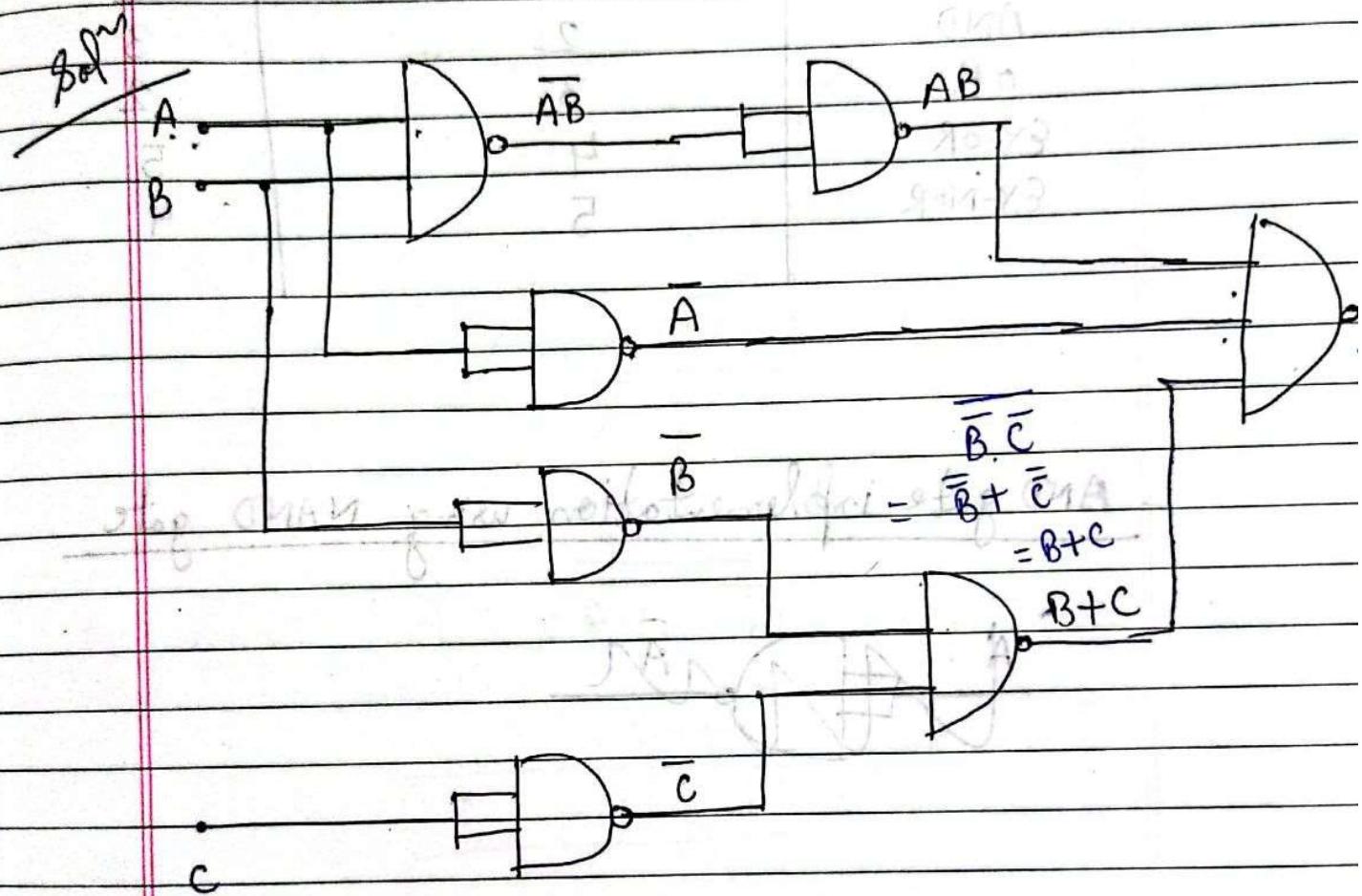Implement the above Boolean func<sup>n</sup> using NAND gates only.



$$Y = AB \cdot \bar{A} \cdot (B+C)$$

$$= \overline{AB} + \bar{A} \cdot (B+C)$$

$$= \overline{AB} + \bar{A} + \overline{B+C}$$

$$= \overline{AB} + A + (B+C)$$

\* Single i/p NAND or NOR gate cannot be considered as two i/p NAND or NOR gate. Page no. \_\_\_\_\_

Date \_\_\_\_\_


\* For inverter, we connect both the inputs.

NAND and NOR GATE AS Universal GATE


(Min. No. of two-input NAND and NOR gates reqd.)



<u>Logic Gates</u>	<u>No. of NAND gates reqd.</u>	<u>No. of NOR gates</u>
NOT	1	1
AND	2	3
OR	3	2
EX-OR	4	5
EX-NOR	5	4

AND gate implementation using NAND gate

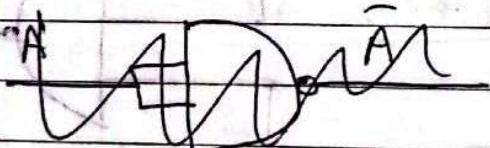


$$(A \bar{+} B) \bar{+} \bar{A} = AB$$

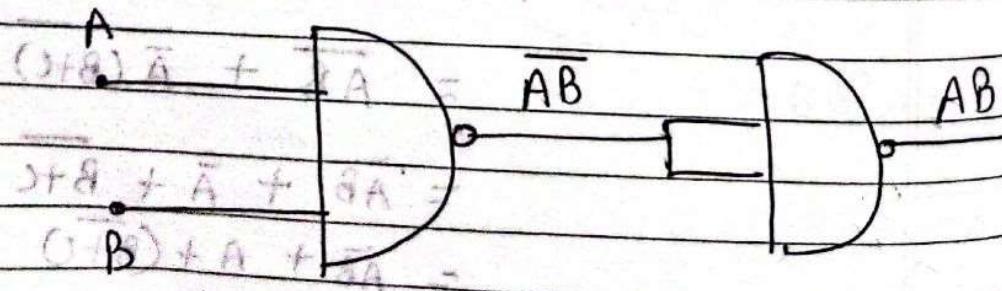

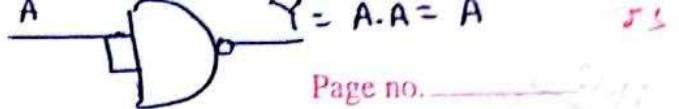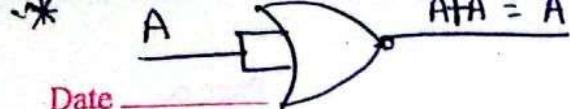

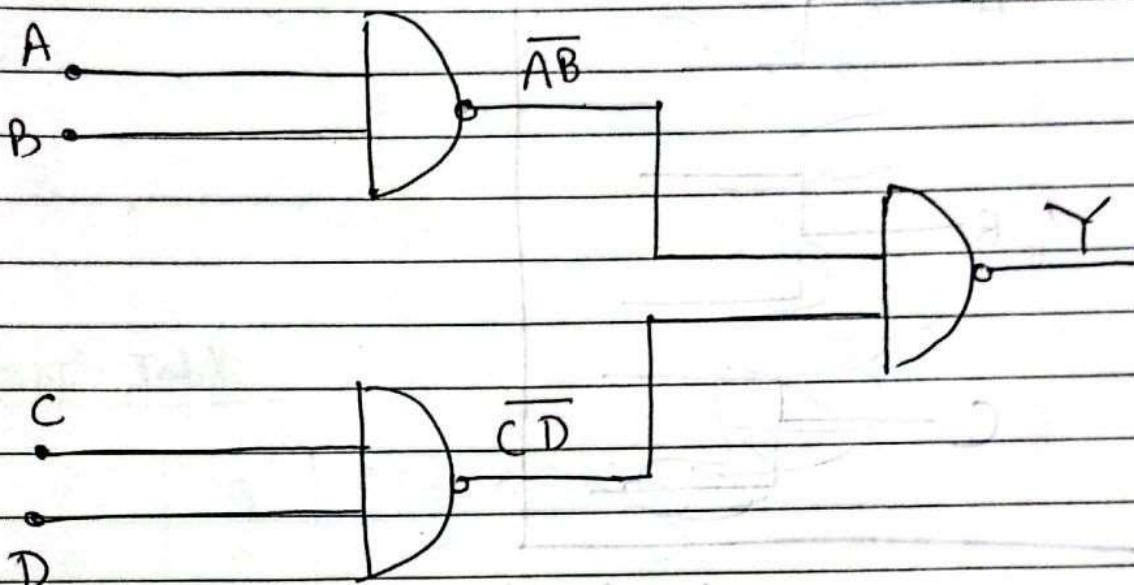~~Q^n~~ Find the min<sup>n</sup> no. of two input NAND gates reqd. to be realized for implementing the boolean func<sup>n</sup>,  $Y = AB + CD$ .




actual logic

$$Y = \overline{AB} \cdot \overline{CD}$$

$$= \overline{AB} + \overline{CD}$$

$Y = AB + CD$

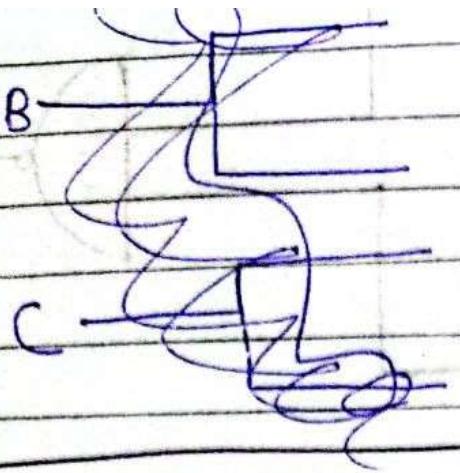$\therefore$  No. of NAND gates reqd. = 3



### Special Gates

Special gates are those gates which are used for special purpose like arithmetic and logical operations.

It is of two types:-

1. EX-OR Gate


2. EX-NOR Gate

### EXOR Gate (Exclusive OR)


→ EXOR oper is not a basic oper and can be performed using the basic gates (AND, OR, NOT) or universal gates (NAND, NOR)

~~Imp~~ → It acts like an "odd no. of 1's detector" in the i/p.

- It is also called "stair Case switch".
- It is mostly used in "parity generation and detection".

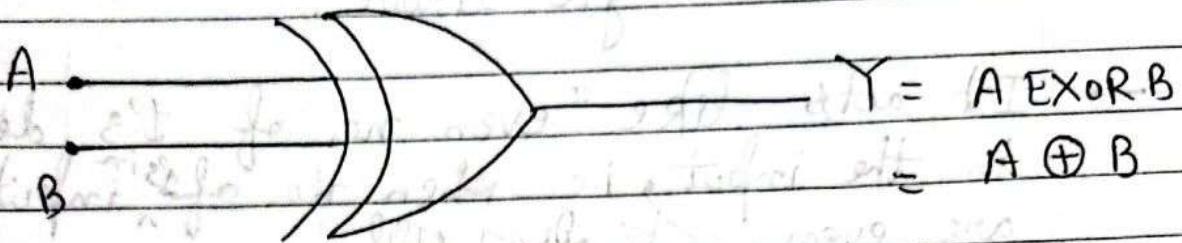Truth Table

A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

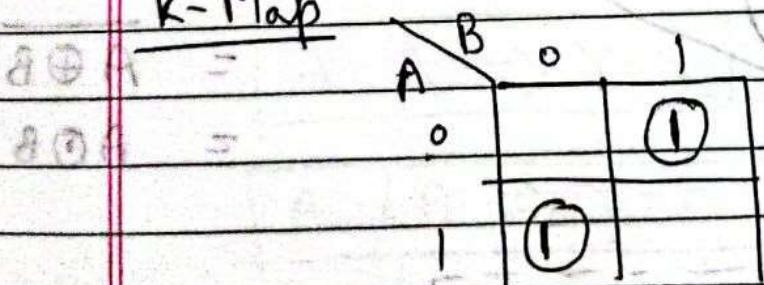K-Map

$$\boxed{\begin{array}{l} A=B, Y=0 \\ A \neq B, Y=1 \end{array}}$$

$$Y = \bar{A}B + A\bar{B}$$

$$\therefore Y = A \oplus B = \bar{A}B + A\bar{B}$$



## 'EX NOR gate'

→ It is also called "Equivalence gate" or "coincidence logic circuit".

→ It acts like "even no. of 1's detector" in the input, i.e. when no. of <sup>1's in</sup> input variables are even.

→ EX NOR oper<sup>n</sup> is equal to the EXOR oper<sup>n</sup> followed by NOT gate.

### Logic circuit

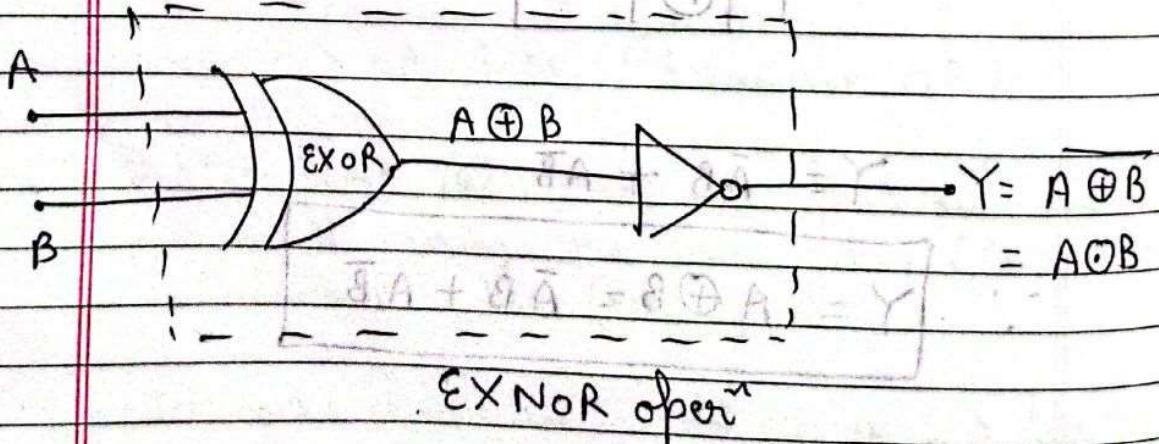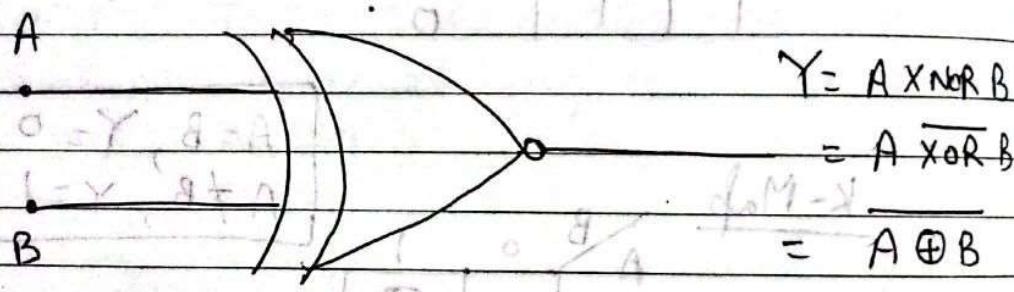

Truth Table

I/Ps		O/Ps
A	B	$Y = A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	1

K-Map

	B	0	1
A	0	(1)	
	1	(1)	

$$Y = \overline{A} \overline{B} + AB$$

$$A = B \Rightarrow Y = 1$$

$$A \neq B \Rightarrow Y = 0$$

NOTE :  $\rightarrow$  The output of "EXNOR" gate is exactly inverse of "EXOR" gate for all input conditions.

## Combinational Circuits

- Combinational circuits are those circuits which depends only on present values of inputs.
- They are memoryless circuits.
- It consists of logic gates whose output at any time are determined directly from the present combination of inputs without regard to previous inputs and previous outputs.

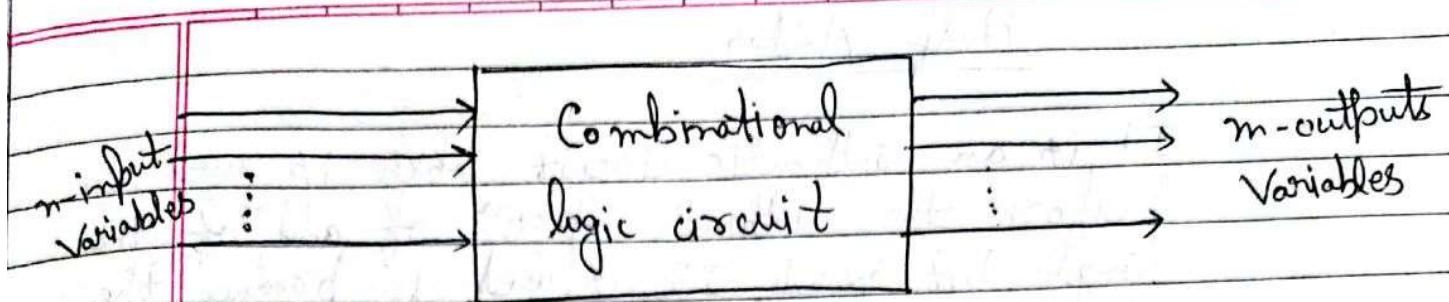


Fig.- Block diagram of combinational logic circuit

### Design Procedure

The procedure involves the following steps:-

- (1) The problem is stated.
- (2) The no. of available input variables and reqd. output variables is determined.
- (3) The input and output variables are assigned letter symbols.
- (4) The truth-table is used to define the reqd. relationship between Inputs and outputs.
- (5) The simplified Boolean func<sup>n</sup> for each output is obtained.
- (6) The logic diagram is drawn.

### Types of Combinational Circuits

1. Adders (Half adder, Full Adder, Parallel Adder, CLA)
2. Subtractor (Half-subtractor, Full Subtractor)
3. Multiplexer
4. De-Multiplexer
5. DECODER
6. ENCODER
7. Comparator
8. 7-segment display