

Emitter: Supplies majority charge carrier i.e. e^- or holes
 Base: Transfer majority charge carriers from emitter to collector
 Collector: Moderately doped. Large amount of heat is liberated & so provided with large area to dissipate heat
 Date: _____


$BJT = \text{Bipolar Junction Transistor}$




Transistor \Rightarrow Transfer of Resistor J_1, J_2, N

$J_1 = FB$] Low Resist.

$J_2 = RB$] High Resist

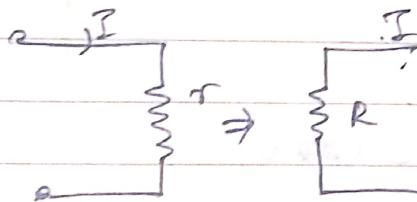

$$V_i = I R \quad V_o = IR$$

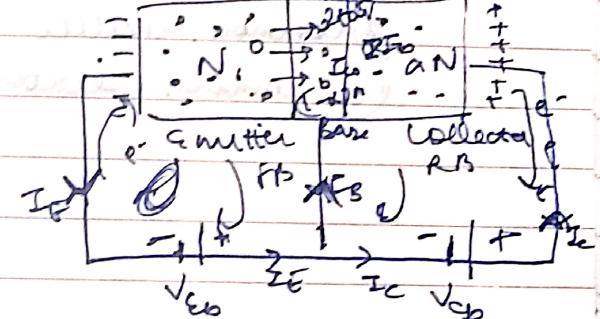

$$N \times N = (1-\alpha)N$$

$$V_i < V_o$$


Amplification

$$A = \frac{V_o}{V_i}$$

$$I_E = I_B + I_C$$

by KCL

$V_b = 0$ bias condition

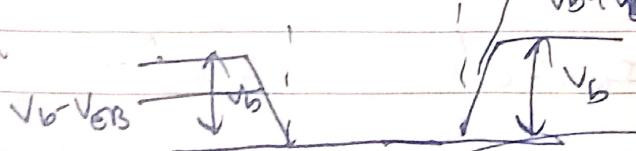



$$I_C = \alpha I_E + I_{C0} \rightarrow \text{leakage or current reverse saturation current}$$

$$I_E = I_B + I_C$$

$$I_B = (1-\alpha) I_E$$

Emitter:

Common base configuration

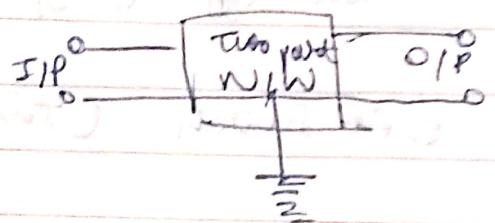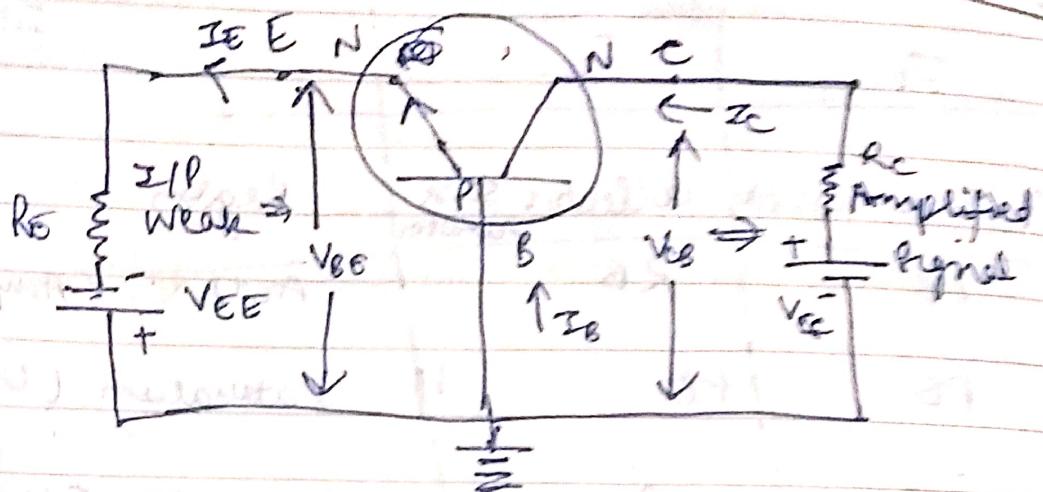


Active Region

$$J_1 = F_B$$

$$J_2 = R_E$$

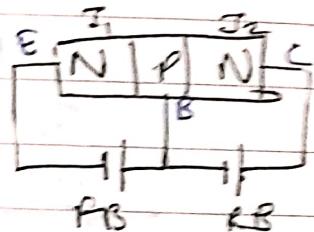- ① Common Base config
- ② Common Emitter config
- ③ common Collector config



Node Gain

Transistor


B/w I/P volt & I/P curr \leftarrow I/P char

B/w O/P curr & O/P voltage \leftarrow O/P char

KCL

$$I_E = I_B + I_C$$

$$I_C = \alpha I_E + I_{CBO}$$

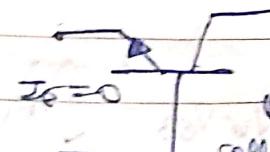

$I_{CBO} \rightarrow 0$
Collector bias (Emitter)

$I_C = \alpha I_E + I_{CBO}$ (current produced when emitter terminal is left open)

$$I_C = \alpha I_E$$


$$\alpha = 0.95 \text{ to } 0.98$$

$$\alpha = \frac{I_C}{I_E}$$

$\alpha =$ current amplification factor of common base config

Date _____ / _____ / _____

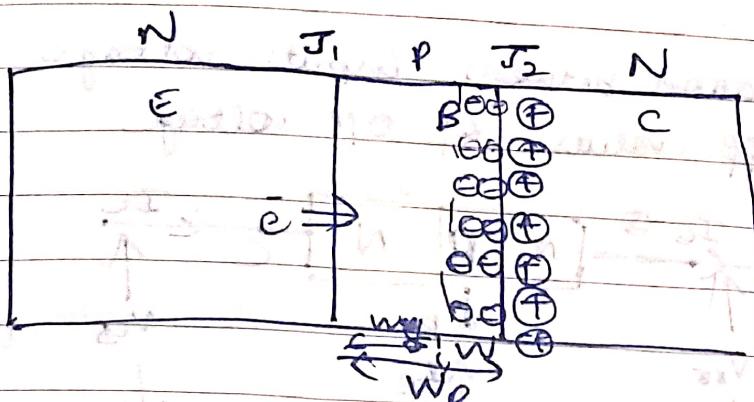Width Early Effect on Base with Modulation



$$J_1 = P_B$$

$$\underline{J_2 = R_B}$$

$$V_{EB} \rightarrow \uparrow$$

$$R_B \rightarrow \uparrow$$

$$\text{Doping : } E > C > B$$

Base is lightly doped as the depletion layer formed will deeply penetrate in base region

$$W_B = \text{width of Base} / \cancel{\text{metallurgical}} \text{ Base width}$$

$$W_B = W_{eff} + W$$

$$\frac{V_{CB} \uparrow}{\cancel{W_B}} \quad \frac{R_B \uparrow}{\cancel{W_B}} \quad \frac{W \uparrow}{\cancel{W_B}}$$

Reverse Bias increase \Rightarrow Depletion Layer increase ($W \uparrow$)

$$W_{eff} = W_B - W \uparrow$$

$$W_{eff} = \downarrow$$

$$\textcircled{1} \quad W_{eff} \Rightarrow \downarrow$$

less recombination

α = increase

$$R_B \uparrow \downarrow \Rightarrow W_B \uparrow \downarrow$$

Base Modulation

$$I_C = \alpha I_E + I_{CBO}$$

$$\alpha \uparrow$$


$$\boxed{I_C \uparrow}$$

$$\textcircled{2} \quad \text{conc. gradient will increase}$$

$$\boxed{I_E \uparrow}$$

Common Base Input Characteristic

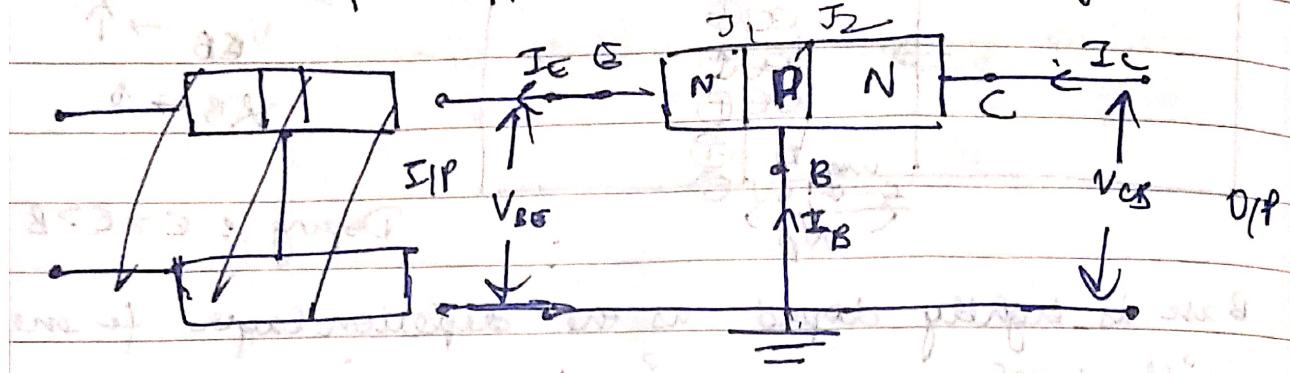It is graphical relation between input voltage & current for diff values of O/P voltage




D/I/P char

② O/P Char

curve

I/P vs I/P curr

O/P voltage = constant

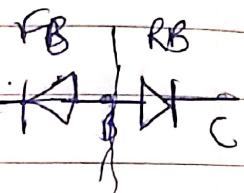

I/P voltage = V_{BE}

I/P

O/P

I/P current = I_E


O/P voltage = V_{CB}

$$\left\{ \begin{array}{l} V_{BE} \quad I_E \\ \end{array} \right\} \quad \left\{ \begin{array}{l} V_{CB} \quad I_C \\ \end{array} \right\}$$

O/P current = I_E

I_E (mA)

$$V_{CB} = 1V$$

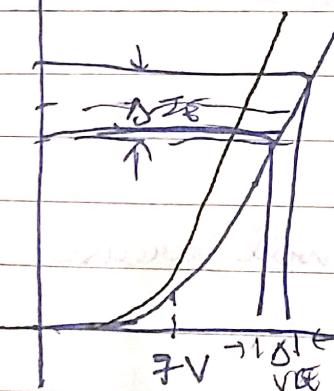

Q Trans

V_{CB} ↑
w_{eff} ↓

I_E ↑

$$\text{slope} = \frac{1}{r_i}$$

$$m = \frac{\Delta V_{BE}}{\Delta I_E} / V_{CB} = \text{const}$$

$$r_i = 20\Omega \text{ to } 100\Omega$$

Date - / /

Dynamic I/P resistance (R_d) = $\frac{\text{Change in } I/P \text{ voltage}}{\text{change in } I/P \text{ current}} / \text{Op voltage} = \text{constant}$

Common Base Output Characteristics

BJT \rightarrow Current Controlled device V_{CB}, V_B, I_C ($I_E = \text{const}$)

$$I_E = \text{Fix}$$

$$V_{CB} \rightarrow \text{vary}$$

$$I_C \rightarrow \text{Node}$$

$$I_E = 0 \text{ mA}$$

$$I_C = \alpha I_E + I_{CBO}$$


$$= 0 + I_{CBO}$$

$$I_C = I_{CBO} \text{ mA}$$


$$I_E \gg I_{CBO}$$

$$\alpha < 1$$

$$I_C \approx I_E$$

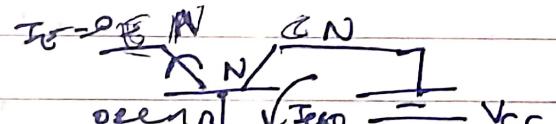

Off-Switch (Volts)

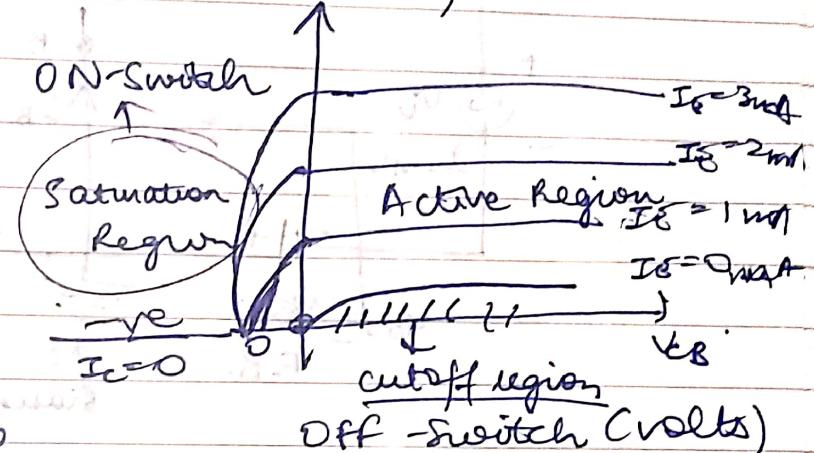

cutoff region

Off-Switch (Volts)

open B open E

open N

base

open emitter

Border line
Active Region
& Saturation
Region

$I_C = 0 \rightarrow$ Active Region & cut-off region

Op dynamic resistance

$$r_o = \frac{\Delta V_{CB}}{\Delta I_C} / I_E = \text{constant}$$

$$r_o = 1 \text{ M}\Omega$$

slope ① \Rightarrow
 $r_o \uparrow$


very high resistance

Date _____

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

low freq current gain of CB config

Transistor Amplifying Action

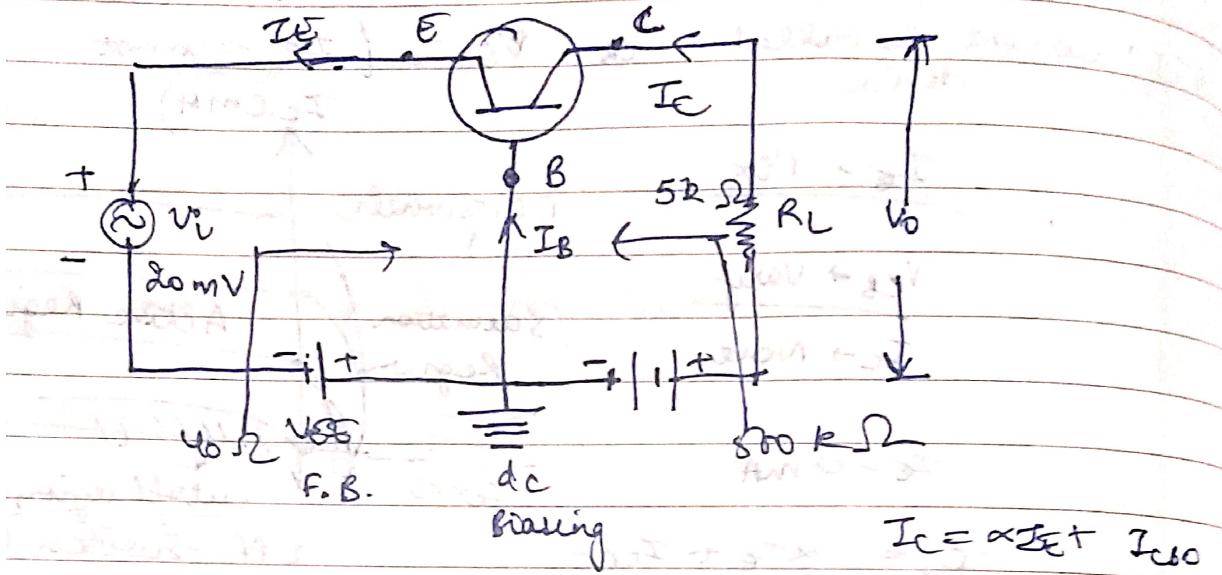

$$V_i = 20 \text{ mV}$$

$$V_E = I_E R_E$$

$$V_E = I_E \cdot 40 \Omega$$

$$I_E = \frac{V_i}{R_E} = \frac{20 \text{ mV}}{40 \Omega} = 0.5 \text{ mA}$$

$$I_E \gg I_{CBO}$$

$$(I_C \approx I_E)$$

$$I_E = 0.5 \text{ mA}$$

$$I_C = 0.5 \text{ mA}$$

$$\alpha < 1$$

$$0.95 \cdot 500 \cdot 10^3$$

$$V_o = I_C \cdot R_L$$

$$= 0.5 \text{ mA} \times 5 \text{ k}\Omega$$

$$= (0.5 \times 10^{-3}) (5 \times 10^3)$$

$$V_o = 2.5 \text{ V}$$

$A_v = \text{Voltage Amplification factor}$

$$= \frac{\text{Output Voltage}}{\text{Input Voltage}} = \frac{2.5 \text{ V}}{20 \text{ mV}} = 125$$

Date _____ / _____ / _____

$$\begin{aligned} V_o &= A_v \times V_i \\ &= 125 \times 20 \text{ mV} \\ &= 125 \times 20 \text{ mV} \end{aligned}$$

① Voltage amplification factor


$$A_v \neq 50 \text{ to } 300$$

② Current Amplification factor

$$\alpha \rightarrow < 1$$

$$0.95 \text{ to } 0.98$$

Common emitter configuration

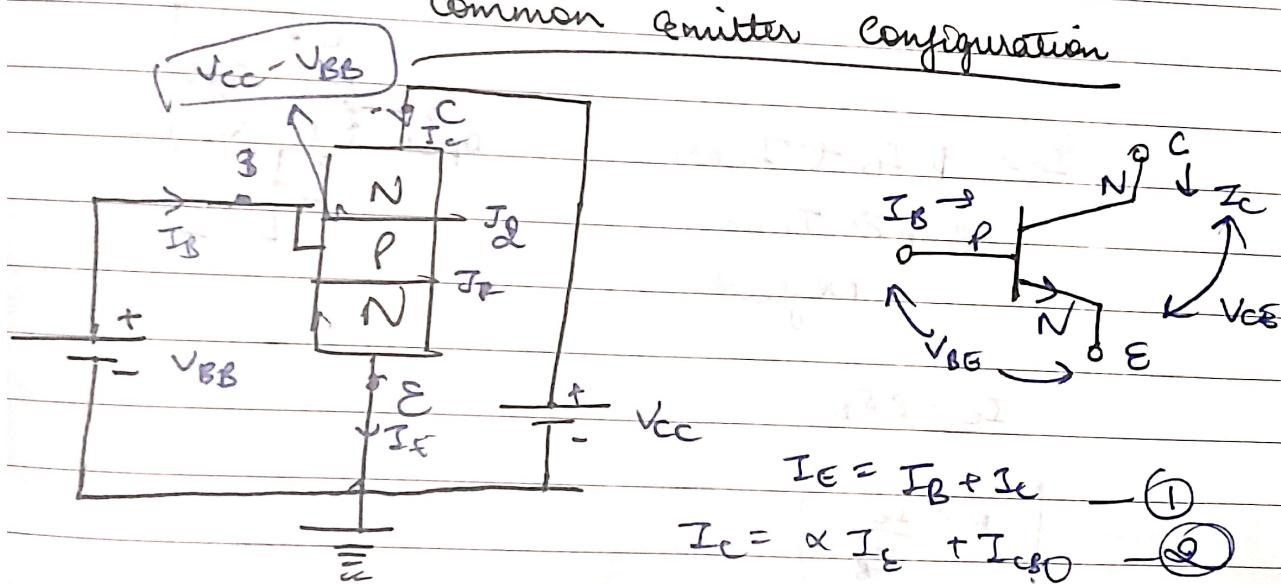

I/P current = I_B

I/P voltage = V_{BE}

O/P current = I_C

O/P voltage = V_{CE}

$$I_C = f(I_B)$$

Put value of I_E from eqn ① in eqn ②

$$I_C = \alpha (I_B + I_C) + I_{CBO}$$

$$I_C = \alpha I_B + \alpha I_C + I_{CBO}$$

$$I_C(1-\alpha) = \alpha I_B + I_{CBO}$$

Divide both sides by $(1-\alpha)$

$$I_C = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$$

$$I_E = I_B + I_C$$

$$I_E = I_B + I_C$$

$$\boxed{\alpha = \frac{I_C}{I_E}}$$

$$\frac{I_E}{I_C} = \frac{I_B}{I_C} + 1$$

$$\frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\boxed{\beta = \frac{\alpha}{1-\alpha}}$$


$$I_C = \beta I_B + (\beta + 1) I_{CBO}$$

$$\boxed{I_C = \beta I_B + I_{CBO}}$$

$$I_C = \beta I_B + I_{CBO}$$

$$\beta I_B \gg I_{CBO}$$

Neglect

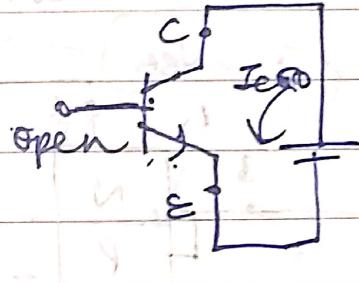

$$I_C = \beta I_B$$

$$\boxed{\beta = \frac{I_C}{I_B}}$$

Current gain of CE configuration $\beta \approx 50$ to 400

" " " " CB configuration $\alpha < 1$

Common emitter \rightarrow Current Amplifier


$$I_B = 5 \text{ mA}$$

$$\beta = 200$$

$$\boxed{I_C = 1000 \text{ mA}}$$

Date _____


CE Input Characteristics

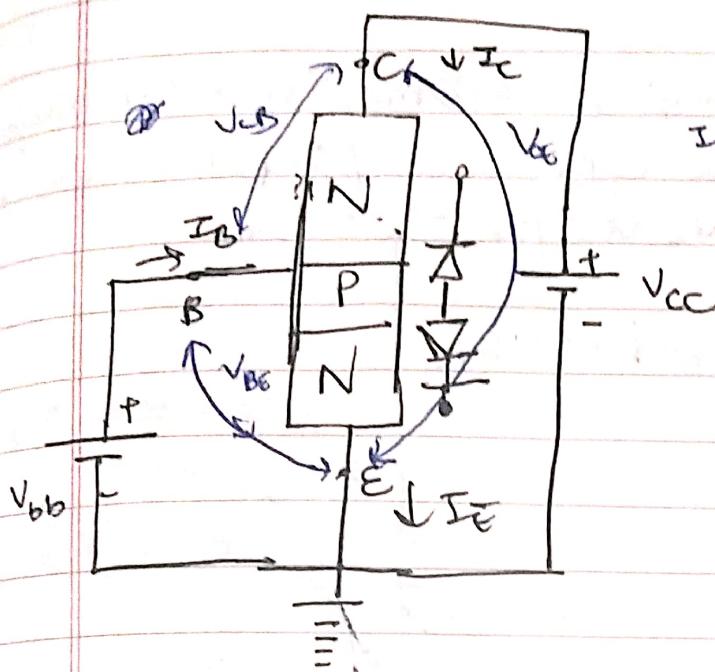


curve bath

I_OP & I_OP curv/O/P voltage constant


V_{BE} vs I_B/V_{CE}

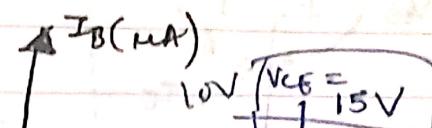

V_{BE} vs I_B/V_{CE}

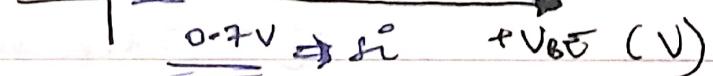

W_B = Base width
Knee Voltage

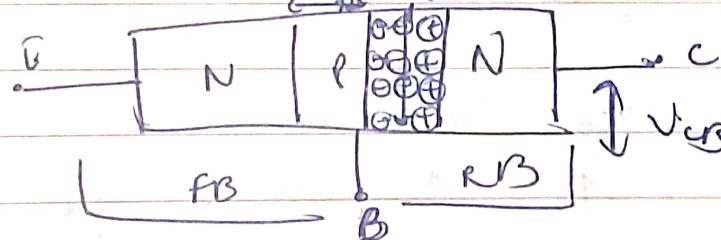

V_{CB}↑ W↑ W_{eff}↑ I_B↑

Base width modulation \rightarrow (W_{eff} = W_B - W)


V_{CB}↓ W↓ W_{eff}↑ I_B↑

$$V_{CB} = V_{CB} + V_{BE}$$

V_{CE}↑ V_{CB}↑ I_B↓

V_{CE}↓ V_{CB}↓ I_B↑

$$\Delta \alpha_i^\circ = \frac{\Delta V_{BE}}{\Delta I_B} / V_{CE} = \text{constant}$$

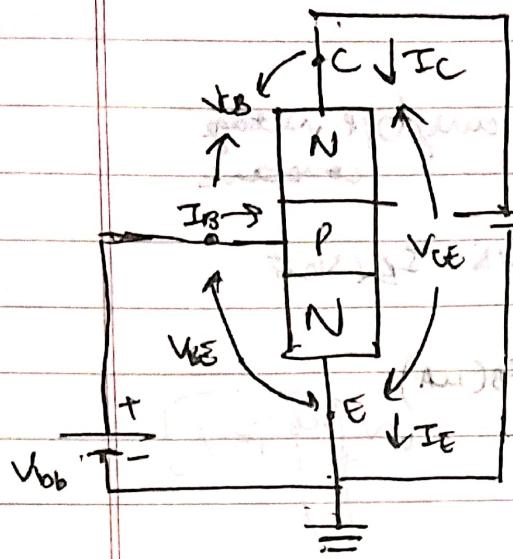BJT Output Characteristics

Graphical relation b/w O/P voltage

& O/P current / Input current


$V_{CE} \propto I_C / I_B = \text{const}$ $I_C (\text{max})$

$$I_C = \beta I_B + (\beta + 1) I_{CBO}$$

$$I_B = 0$$

$$I_C = (\beta + 1) I_{CBO}$$

= leakage
current

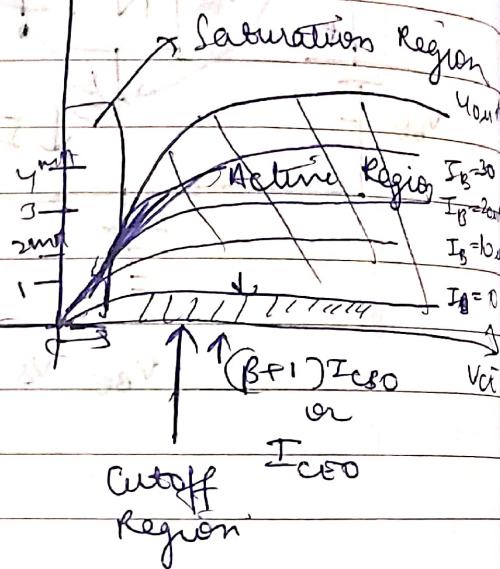

$I_E \Rightarrow$ Independent of V_{CE}

Early Effect

$$V_{CE} = V_{CB} + V_{BE}$$

$\uparrow \quad \uparrow \quad W_{eff} \downarrow I_B \downarrow I_c \uparrow$

Dynamic O/P resistance

$$r_{oD} = \frac{\Delta V_{CE}}{\Delta I_C} \quad | I_B = \text{constant}$$

Relation b/w α , β , γ

$\alpha \rightarrow$ Amplification factor of CB configuration

$$\alpha_{dc} = \frac{I_C}{I_E}$$

$$\alpha_{ac} = \frac{\Delta I_C}{\Delta I_E} \quad | V_{CB} = \text{const}$$

Date ___ / ___ / ___

→ $\beta \rightarrow$ Current amplification factor of CE configuration

$$\beta_{dc} = \frac{I_c}{I_B} \quad A_{ac} = \frac{\Delta I_c}{\Delta I_B} \quad | \quad V_{CE} = \text{constant}$$

→ $\gamma \rightarrow$ amplification factor of CC config

$$\gamma_{dc} = \frac{I_E}{I_B} \quad A_{ac} = \frac{\Delta I_E}{\Delta I_B} \quad | \quad V_{EC} = \text{const}$$

$$I_E = I_C + I_B$$

divide both sides by I_B

$$\frac{I_E}{I_B} = \frac{I_C}{I_B} + 1$$

$$y = \beta + 1$$

We know that


$$\beta = \frac{\alpha}{1-\alpha}$$

$$y = \frac{\alpha}{1-\alpha} + 1$$

$$y = \frac{1}{1-\alpha}$$

$$y = \beta + 1 = \frac{1}{1-\alpha}$$

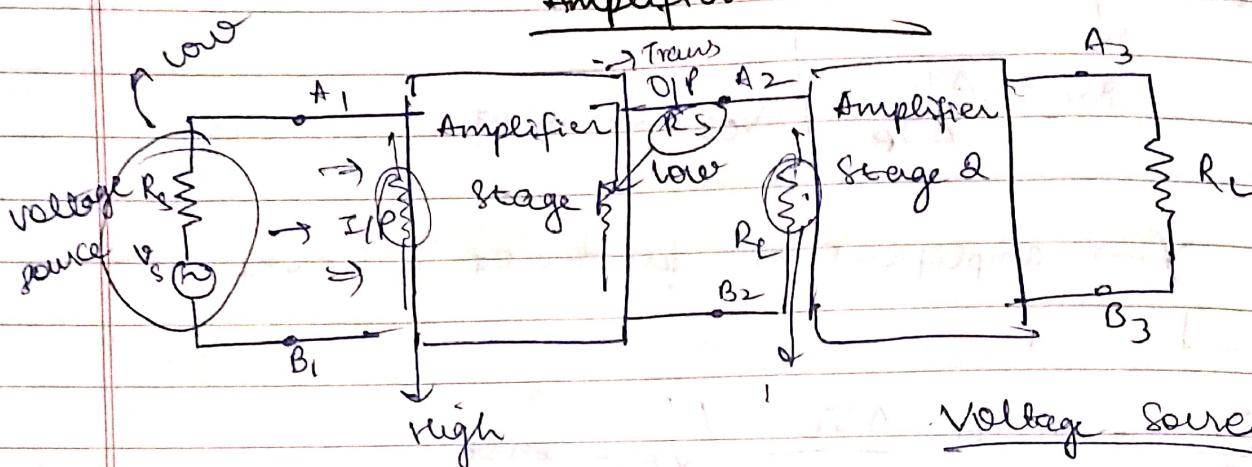Why CE configuration is widely used in Amplifier Circuits




Voltage Source

$$V_T = \frac{R_L}{R_S + R_L} \times V_s$$

$$V_T \approx V_s = \frac{V_s}{R_L}$$

if $R_S \gg R_L$

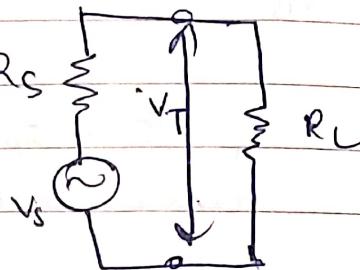

$$V_s \approx V_T \text{ (good voltage source)}$$

$$C_B = I/P \Rightarrow 20 \Omega$$

$$= 0.1 P \Rightarrow 1 M\Omega$$

I/P resist (R_S) \Rightarrow low
 O/P resist (R_L) \Rightarrow High

$$C_E \Rightarrow I/P = 1 k\Omega$$


$$O/P = 10 k\Omega$$

$$C_C \Rightarrow I/P = 150 k\Omega$$

$$O/P = 800 \Omega$$

Coupling
crossover

Basic CE Amplifier and DC load line

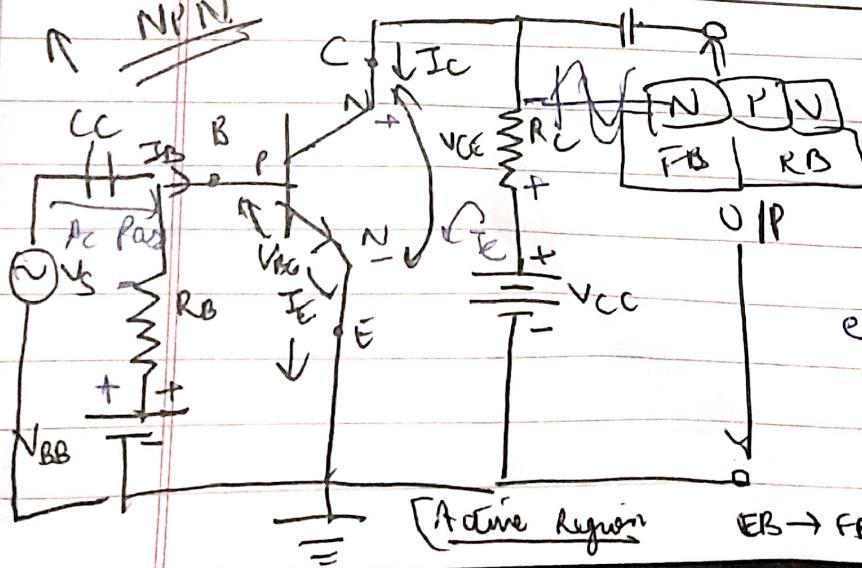

$$I_c = B I_B$$

O/P section eqn

$$V_{CE} - I_c R_C - V_{CE} = 0$$

eqn of straight line

$$Y = mx + c$$


$$I_c = \frac{V_{CC} - V_{CE}}{R_C} = \frac{V_{CC} - V_{CE}}{R_C} \cdot \frac{1}{R_L}$$

const

x

y

CB \rightarrow RB

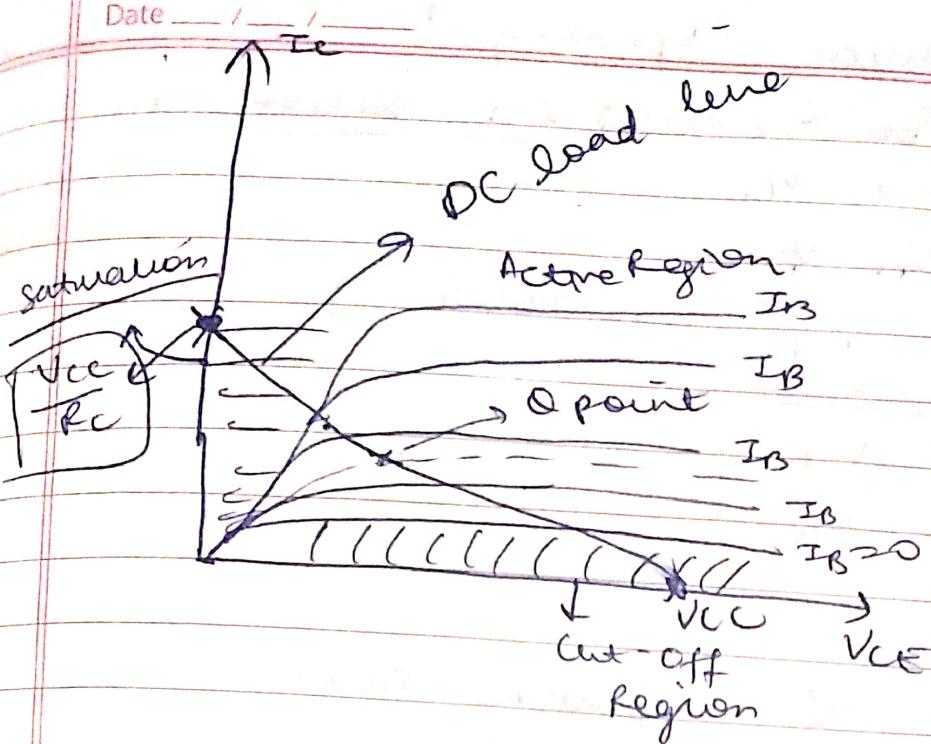

Quiescent condition

When no signal on the base

$$I_c = \cancel{V_B} \left(-\frac{1}{R_C} \right) V_{CE} + \frac{V_{CE}}{R_C}$$

$$y = \cancel{m} + c$$

slope of line = $-\frac{1}{R_C}$

On Y-axis

$$V_{CE} = 0$$

$$V_{CC} - I_c R_C - 0 = 0$$

$$I_c = \frac{V_{CC}}{R_C}$$

On X-axis

$$I_c = 0$$

$$\boxed{V_{CC} = V_{CE}}$$

DC load line is formed when we join I_c & V_{CC}

Date

Quiescent Condition (Operating point)


$$V_{BB} - I_B R_B - V_{BE} = 0 \rightarrow \text{I/P section eqn}$$

$$I_B R_B = V_{BB} - V_{BE}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

[0.7 V_{BE} si]

$$I_B \approx \frac{V_{BB}}{R_B}$$

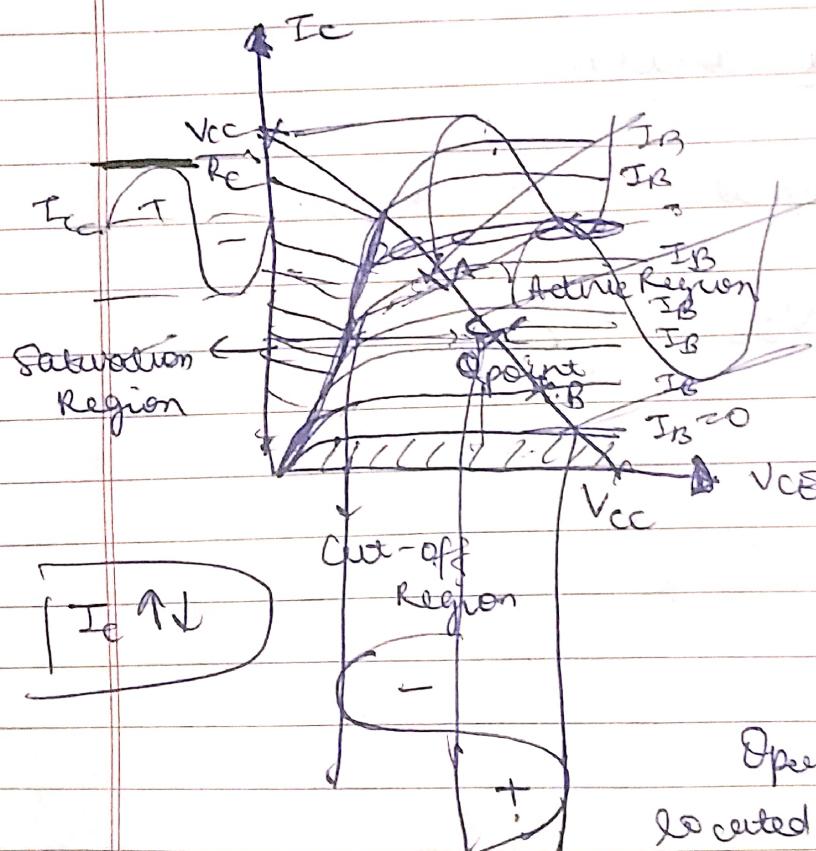Selection of Operating Point

$$I_C \uparrow \downarrow$$

① Transistor parameter

$\beta \rightarrow$ Current gain

$$\uparrow \downarrow I_C = \beta I_B + (\beta + 1) I_S$$

② Temp $(I_C) \uparrow \downarrow$

Operating point should be located in middle of DC load line

so we get the same output as the input given & This is known as faithful amplification

Bias Stabilization & Stability Factor

Stabilization :- The process of making operating point independent of temperature changes and variations in transistor parameters is known as stabilization.

Causes of Instabilization

① Temperature changes.

$$T \uparrow \downarrow$$

$$I_c = \beta I_B + (\beta + 1) I_{CBO}$$



Reverse leakage current


10°C Rise in Temperature

$$I_{CBO} = \text{Double}$$

↓ Minority charge carriers

$T \uparrow I_{CBO} \uparrow \rightarrow I_c \uparrow$. $T \uparrow \rightarrow V_{be}$ (2-5 mV decrease / °C ↑)

$$I_c \propto T$$

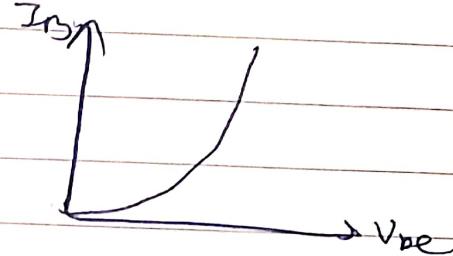

② Current gain $\rightarrow I_c \uparrow \downarrow$ (β)

Stability Factor - The ratio of change of collector current over reverse leakage current at constant input voltage and amplification factor is called stability factor.

(β)

Lower the value of S, system will be more stable

$$S = \frac{dI_c}{dI_{CBO}} \quad | \text{ const } V_{BE} \& \beta$$

$$S' = \frac{dI_c}{dV_{BE}} \quad | \text{ const } I_{CBO} \& \beta$$

$$S'' = \frac{dI_c}{d\beta} \quad | \text{ const } V_{BE} \& I_{CBO}$$


Date _____ / _____ / _____

Requirement for Biasing Circuit


- ① Selection of operating point - Middle of load line
- ② Stabilization against temp variations of I_C

(B) free from transistor parameter variations


fixed bias circuit

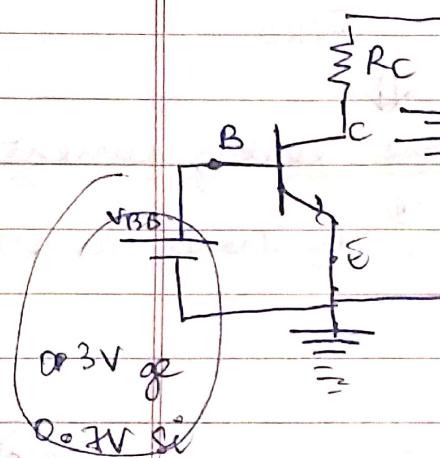




Base Bias Circ.

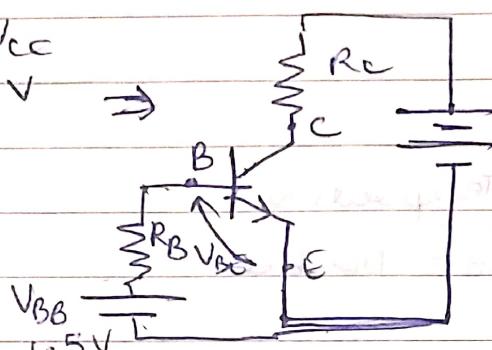


Base Bias Circ.

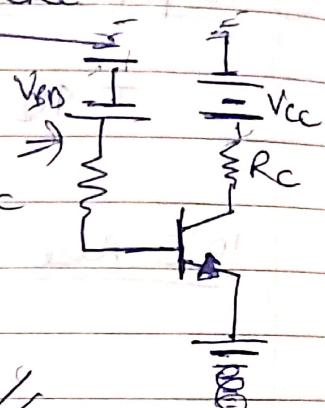

Potential diff

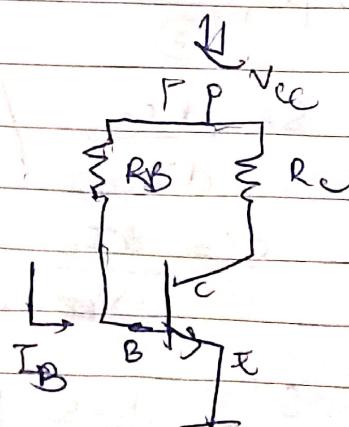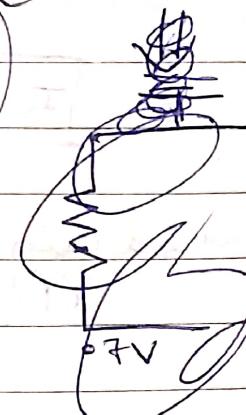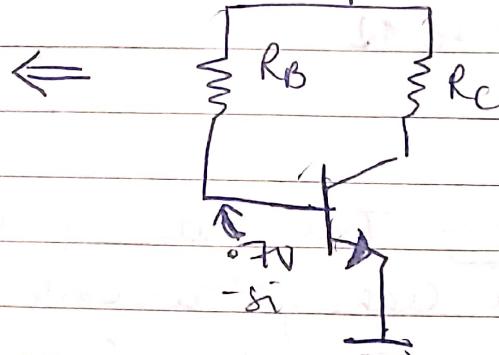

Date / /

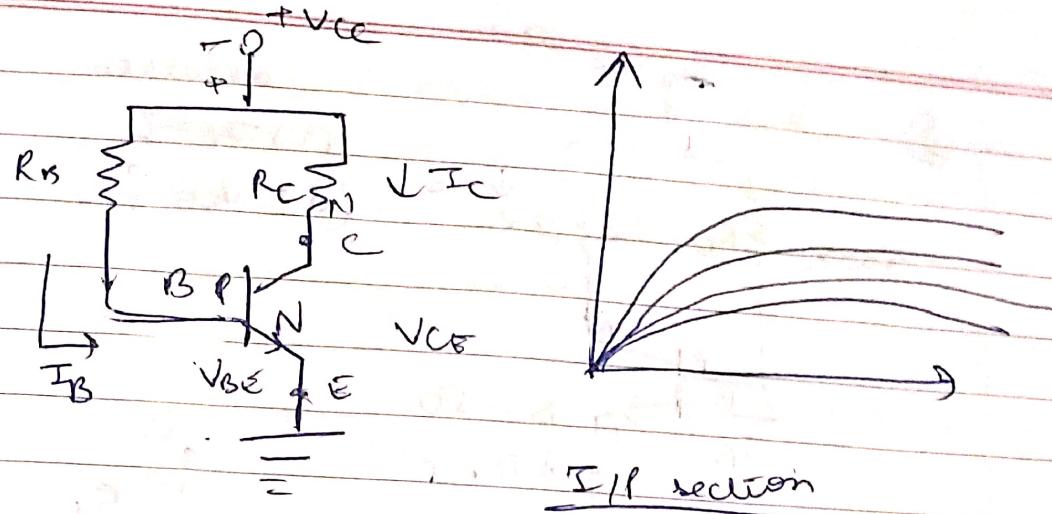

$$V_B \approx 0.7V$$

$$+V_{CC} - I_B R_B - V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_B \approx \frac{V_{CC}}{R_B}$$

$$I_C = \beta I_B + (\beta + 1) I_{CEO}$$

$$I_{CEO} = (\beta + 1) I_{CEO}$$

$$I_C = \beta I_B + I_{CEO}$$

$$I_C \approx \beta I_B$$

$$I_C = \beta \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$

QP section


$$+V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

- ① operating point in the middle - R_B (design flex)

Date _____

\equiv

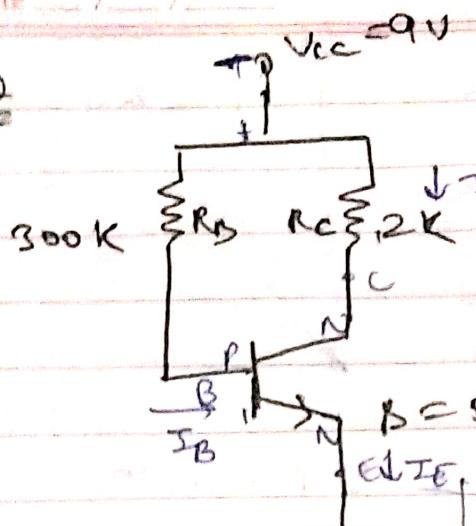

$$I_C = \beta I_B$$

I/P section

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_B \approx \frac{V_{CC}}{R_B}$$

$$= \frac{9V}{300k\Omega} = \frac{9}{300 \times 10^3} = \frac{3}{10^5} = 3 \times 10^{-5} A$$

$\boxed{I_B = 30 \mu A}$

$$\begin{aligned} I_C &= \beta I_B \\ &= 50 \times 30 \times 10^{-6} \\ &= 1500 \times 10^{-6} \end{aligned}$$

$$\boxed{(I_C = 1.5mA)}$$

O/P section

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = 9 - (1.5 \times 2k\Omega)$$


$$= 9 - 3$$

$$\boxed{(V_{CE} = 6V)}$$

Calculate

(i) $I_C = ?$


(ii) $V_{CE} = ?$

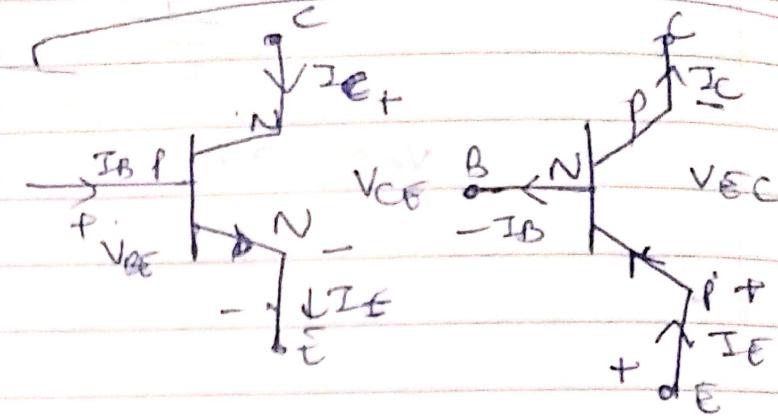

$$f = \beta_{dc} = \frac{I_C}{I_B}$$

$$\alpha = \alpha_{dc} = \frac{I_C}{I_E}$$

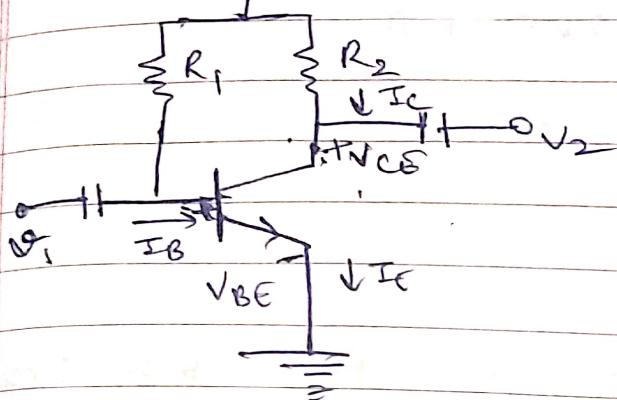In amplifier circuit shows value of R_1 & R_2 are such that the transistor is operating at $V_{CE} = 3V$ & $I_C = 1.5\text{mA}$ when $\beta = 150$. For a transistor with $\beta = 200$, calculate the operating point



$$V_{CE} = 3V \quad I_C = 1.5\text{mA} \quad \beta = 150$$

$$I_C = \beta I_B$$

$$\frac{1.5}{150} = I_B$$

$$I_B = 10\mu\text{A}$$

$$Z_L = \frac{1}{2\pi f C} = \frac{1}{0} = \infty$$

$$\text{dc } f = 0$$

Hence dc analysis

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B}$$

$$R_B = \frac{6 - 0.7}{10\mu\text{A}} = 530 \times 10^3 \Omega$$

D/P section

$$V_{CC} - I_C R_Q - V_{CE} = 0$$

$$R_Q = \frac{V_{CC} - V_{CE}}{I_C}$$

$$= \frac{6 - 3}{1.5\text{mA}} = 2k\Omega$$

$$R_2 = 2k\Omega$$

$$(iii) V_{CC} = 6V, R_1 = 530k\Omega, R_2 = 2k\Omega, \beta = 200$$

$$I_C = \beta I_B$$

$$V_{CE} - I_B R_B - V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_1} = \frac{6V - 0.7V}{530k\Omega} = \frac{5.3}{530} k\Omega$$

$$I_B = 10\mu\text{A}$$

O/P section

$$V_{CC} - I_C R_2 - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_2$$

$$= 6V - 2mA \cdot 2k\Omega$$

$$= 6 - 4 = 2$$

$$\boxed{V_{CC} = 2V}$$


Stability factor for fixed bias circuit

$$S = \frac{dI_C}{dI_{CBO}} / \text{const } V_{BE} \& \beta$$

Step I

$$V_{CC} - I_B R_B - V_{BE} = 0$$
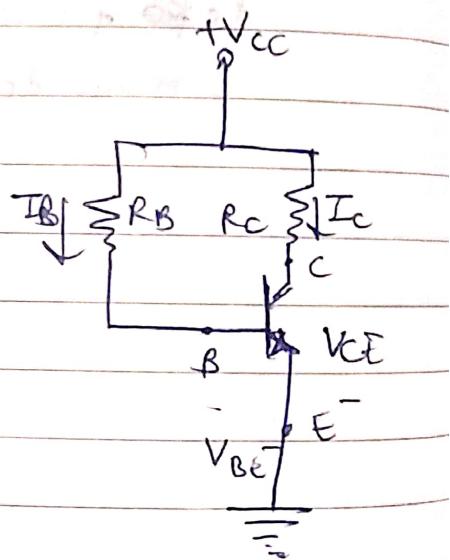
$$\boxed{I_B = \frac{V_{CC} - V_{BE}}{R_B}}$$



Step II

$$I_C = \beta I_B + (\beta + 1) I_{CBO} \rightarrow \textcircled{O}$$

$$I_C = \beta I_B + (\beta + 1) I_{CBO} \rightarrow \textcircled{1}$$

$$= \beta \left(\frac{V_{CC} - V_{BE}}{R_B} \right) + (\beta + 1) I_{CBO} \rightarrow \textcircled{2}$$

Differentiate wrt I_C with const V_{BE} & β

$$\frac{dI_C}{dI_C} = \frac{\beta}{R_B} \frac{d}{dI_C} (V_{CC} - V_{BE}) + (\beta + 1) \frac{dI_{CBO}}{dI_C}$$

$$I = \frac{\beta}{R_B} (0 - 0) + (\beta + 1) \frac{1}{S}$$

$$I = (\beta + 1) \frac{1}{S} \Rightarrow S = \beta + 1$$

General Eqn for Stability Factor

$$\frac{dI_C}{dI_C} = \beta \frac{dI_B}{dI_C} + (\beta + 1) \frac{dI_{CBO}}{dI_C}$$

$$1 = \beta \frac{dI_B}{dI_C} + (\beta + 1) \frac{1}{S}$$

$$(\beta + 1) \frac{1}{S} = 1 - \beta \frac{dI_B}{dI_C}$$

$$S = \frac{\beta + 1}{1 - \beta \frac{dI_B}{dI_C}}$$

→ generalised eqn


Collector to Base Bias Circuit

Input Section (KVL)

$$V_{CC} - R_C (I_C + I_B) - I_B R_B - V_{BE} = 0$$

$$-I_C R_C - I_B R_C - I_B R_B - V_{BE} = 0$$
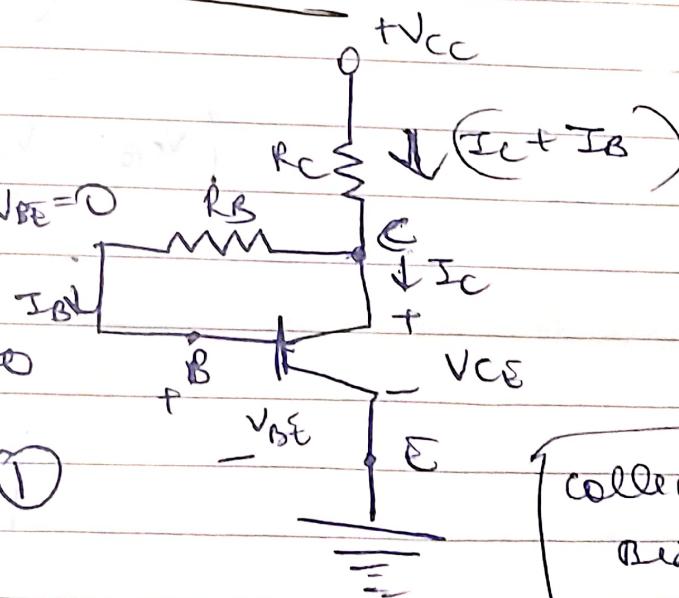
$$B = \frac{V_{CC} - I_C R_C - V_{BE}}{R_C + R_B} - ①$$



Collector feed
back
Bias Ckt
Voltage
F/B ckt

Output Section

$$V_{CC} - R_C (I_C + I_B) - V_{CE} = 0$$

$$V_{CC} - I_C R_C - V_{CE} = 0 \quad I_B \ll I_C$$

$$V_{CE} = V_{CC} - I_C R_C \quad \text{--- (2)}$$

Put eqn (2) in eqn (1)

$$I_B = \frac{V_{CE} - V_{BE}}{R_C + R_B}$$

$\uparrow I_{CBO}$, \uparrow

$$I_C = \beta I_B (\beta + 1) I_{CBO}$$

$I_C \downarrow$, $I_B \downarrow$

$V_{CE} \downarrow$

$$V_{CC} - \beta I_B R_C - I_B (R_C + R_B) - V_{BE} = 0 \quad (\text{eqn 1})$$

$$V_{CC} - I_B [(\beta + 1) R_C + R_B] - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{(\beta + 1) R_C + R_B}$$

$$I_C = \beta I_B = \frac{\beta (V_{CC} - V_{BE})}{(\beta + 1) R_C + R_B}$$

$\beta + 1 \approx \beta$

$$V_{CE} = V_{CC} - I_C R_C$$

$$I_C = \frac{\beta (V_{CC} - V_{BE})}{\beta R_C + R_B} = \frac{\beta' (V_{CC} - V_{BE})}{\beta' R_C + R_B}$$

$\beta' R_C \gg R_B$

$$I_C = \frac{V_{CC} - V_{BE}}{R_C}$$

free from β