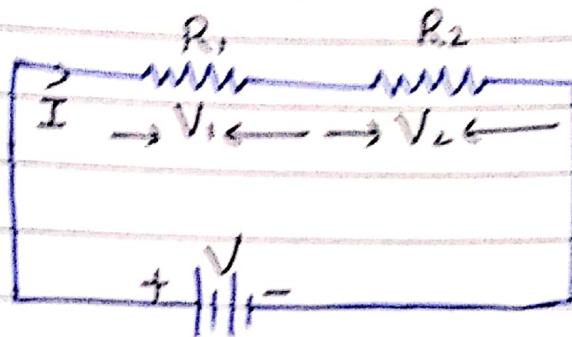


ELECTRONICS & ELECTRICAL ENGINEERING

Voltage Divider Rule




$$I = \frac{V}{R}$$

$$V_1 = IR_1$$

$$V_1 = \frac{R_1}{R_1 + R_2} V$$

$$V_2 = \frac{R_2}{R_1 + R_2} V$$

Current Divider Rule

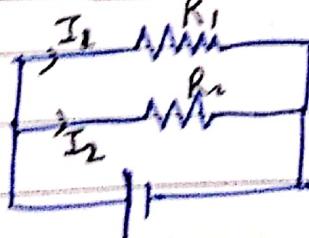

$$I = \frac{V}{R}$$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 R_1 = I_2 R_2 = I R$$

$$I_1 R_1 = I R$$


$$I_1 = \frac{I R_1 R_2}{R_1 (R_1 + R_2)}$$

$$I_1 = \frac{I R_2}{R_1 + R_2}$$

DOMS

$$I_2 = \frac{I R_1}{R_1 + R_2}$$

11

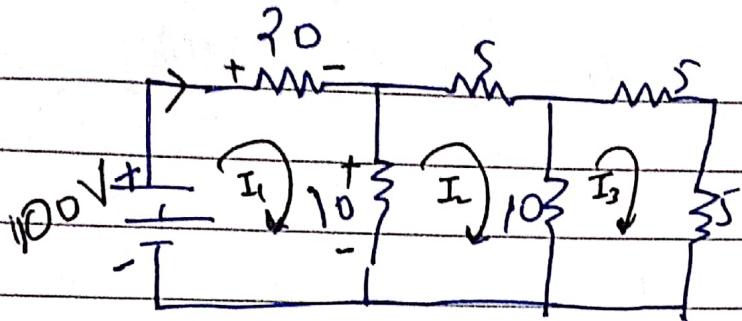


Every mesh is a loop but every loop ^{not} is a mesh

Voltage - to + +ve
+ to - -ve

Current entering +ve
exit -ve

A Loop currents will be taken as maximum for a loop

$$100 - 20I_1 - 10(I_1 - I_2) = 0$$

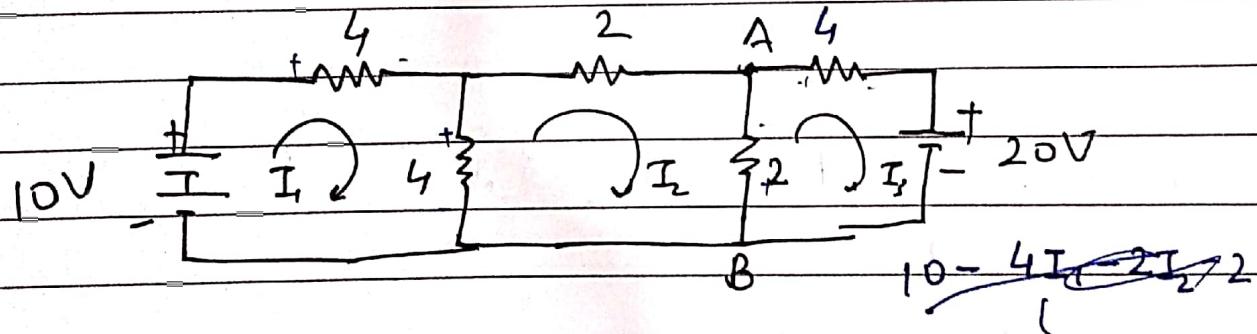

$$10 - 4I_1 - 4(I_1 - I_2) = 0$$

$$10 = 4I_1 + 4I_1 - 4I_2$$

~~$$I_2 = 8I_1 - 4I_2 = 10 \quad (1)$$~~

$$-20 - 2(I_3 - I_2) - 4I_3 = 0$$

~~$$20 = -2I_3 + 2I_2 - 6I_3$$~~

~~$$20 + 8I_3 = 2(2S) = 5$$~~

~~$$I_3 = 1.8$$~~

ANS

$$-2I_2 - 2(I_2 - I_3) - 4(I_2 - I_1) = 0 \quad \text{--- (2)}$$


$$-8I_2 + 2I_3 - 4I_1 = 0$$

$$-20 - 2(I_3 - I_2) - 4I_3 = 0 \quad \text{--- (3)}$$

$$-20 = -2I_3 - 2I_2$$

$$I_1 = 1.0937, \quad I_2 = -0.3125, \quad I_3 = -3.4375$$

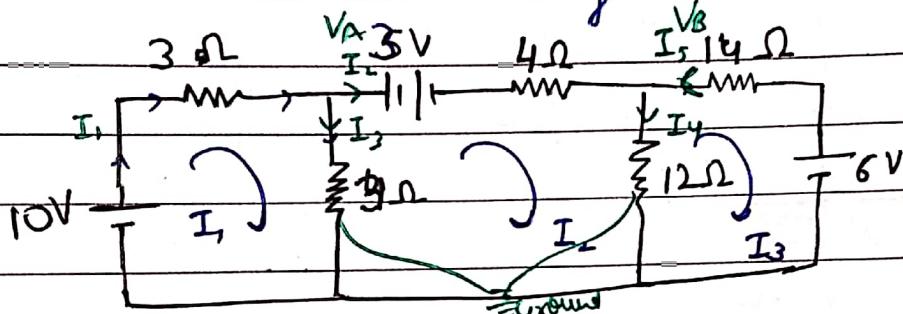Current through AB = $I_2 - I_3$ or $I_3 - I_2$



$$10 - 3I_1 - 3(I_1 - I_2) = 0$$

$$10 = 6I_1 - 3I_2 + 0I_3$$

$$-5 - 4I_2 - 12(I_2 - I_3) - 3(I_2 - I_1) = 0$$

$$5 = -19I_2 + 12I_3 + 3I_1$$

$$-6 - 12(I_3 - I_2) - 14I_3 = 0$$

$$6 = -26I_3 + 12I_2 + 0I_1$$

$$\begin{vmatrix} A_1x + B_1y + C_1z \\ A_2x + B_2y + C_2z \\ A_3x + B_3y + C_3z \end{vmatrix} = \begin{vmatrix} d_1 \\ d_2 \\ d_3 \end{vmatrix}$$

$$\begin{vmatrix} 6 & -3 & 0 \\ 3 & -19 & 12 \\ 0 & 12 & -26 \end{vmatrix} = \begin{vmatrix} d_{10} \\ d_{15} \\ d_{18} \end{vmatrix} \begin{vmatrix} 10 \\ 5 \\ 3 \end{vmatrix}$$

$$\Delta = 6(19 \times 26 - 144) + 3(-98 - 0)$$

$$= 6(350) - 294 = 1806$$

DOMS

$$5 = -19I_2 + 12\left(\frac{12I_2 - 6}{26}\right) + 3\left(\frac{10 + 3I_2}{12}\right)$$

$$5 = -19I$$

$$\begin{array}{r} 19 \\ 26 \\ \hline 41 \end{array} \begin{array}{r} 32 \\ 52 \\ \hline 84 \end{array} \begin{array}{r} 38 \\ 49 \\ \hline 87 \end{array} \begin{array}{r} 14 \\ 29 \\ \hline 43 \end{array} \begin{array}{r} 9 \\ 18 \\ \hline 27 \end{array} \begin{array}{r} 3 \\ 6 \\ \hline 9 \end{array} \begin{array}{r} 3 \\ 6 \\ \hline 9 \end{array} \begin{array}{r} 3 \\ 6 \\ \hline 9 \end{array}$$

$$I_1 = I_2 + I_3 \quad \text{--- (1)}$$


$$I_2 + I_5 = I_4 \quad \text{--- (2)}$$

$$\textcircled{1} \quad \frac{10 - V_A}{3} = \frac{V_A - V_B - 3}{4} + \frac{V_A - 0}{8}$$

$$\frac{3 + 10}{4} = \frac{V_A}{3} + \frac{V_A}{4} + \frac{V_A - V_B}{8} + \frac{3}{4}$$


$$\textcircled{2} \quad \frac{V_A - V_B - 3}{4} + \frac{6 - V_B}{14} = \frac{V_B - 0}{12}$$
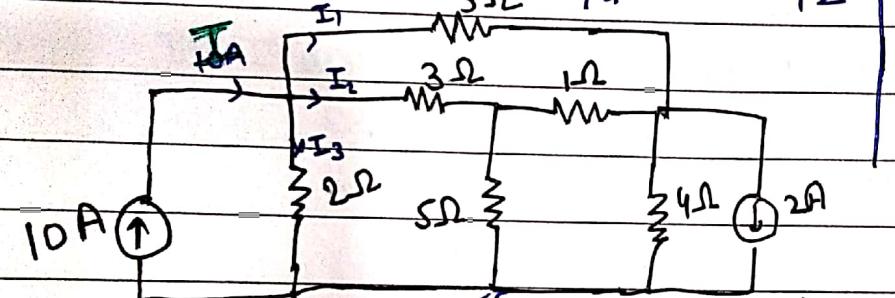
$$\frac{V_A - V_B - 3}{8} - \frac{V_B - 6}{14} - \frac{V_B}{12} = \frac{3}{4} - \frac{6}{14}$$



$$\frac{17}{24} V_A = \frac{\sqrt{3}}{4}$$

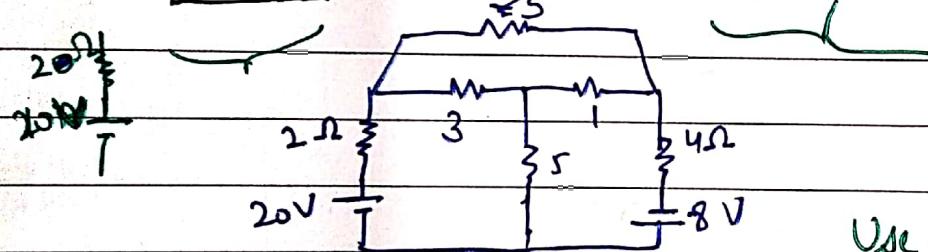for Conv. of Current source to V source
in Parallel
I source with load



$$\frac{1}{4} \frac{1}{8} V$$

Use Nodal analysis where Current Source is given

$$I = 10 = I_1 + I_2 + I_3$$

& Loop analysis where Voltage Source is given

Thevenin theorem: Any 2 terminal bilateral linear DC circuit can be replaced by an equivalent circuit consisting of voltage source with series resistance

Steps -


- (1) Remove the load resistance & find the open

DCM5

(2) circuit voltage across the open circuited terminals
 deactivate the constant sources (for voltage source remove it by internal resistance and for current source, replace it with open source) and find the total internal resistance of the source side looking through open circuited load terminal


(3) obtain thevenin equivalent circuit by placing eq. res. with open source in series.

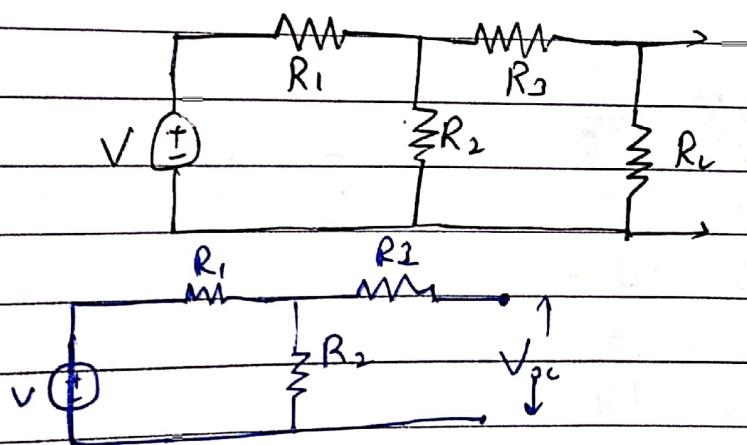(4) Reconnect the load resistance across the load terminals





$$V_{oc} = \frac{VR_2}{R_1 + R_2}$$

$$\begin{aligned} R_{th} &= R_3 + (R_1 || R_2) \\ &= R_3 + \frac{R_1 R_2}{R_1 + R_2} \end{aligned}$$

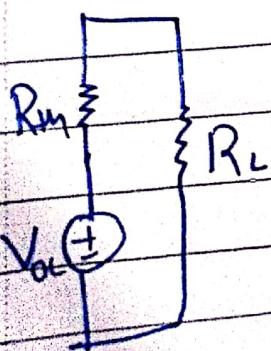

$$I = \frac{V_{oc}}{R + R_{th}}$$

DOMS

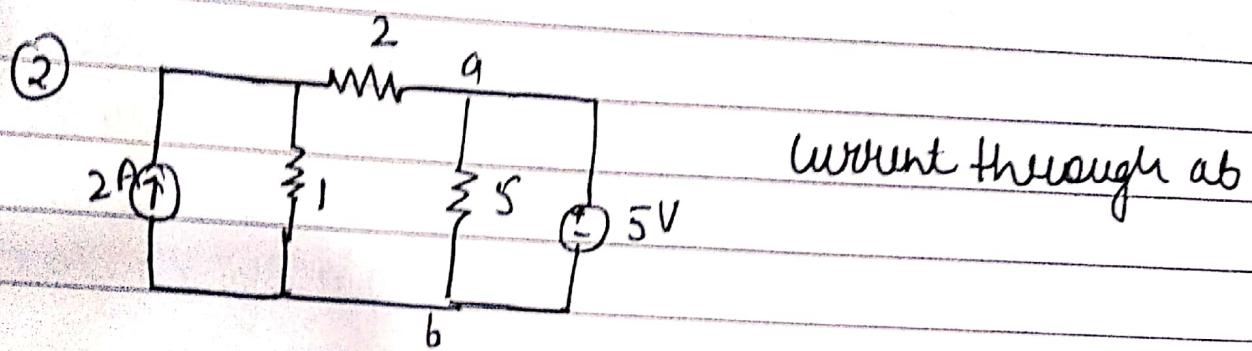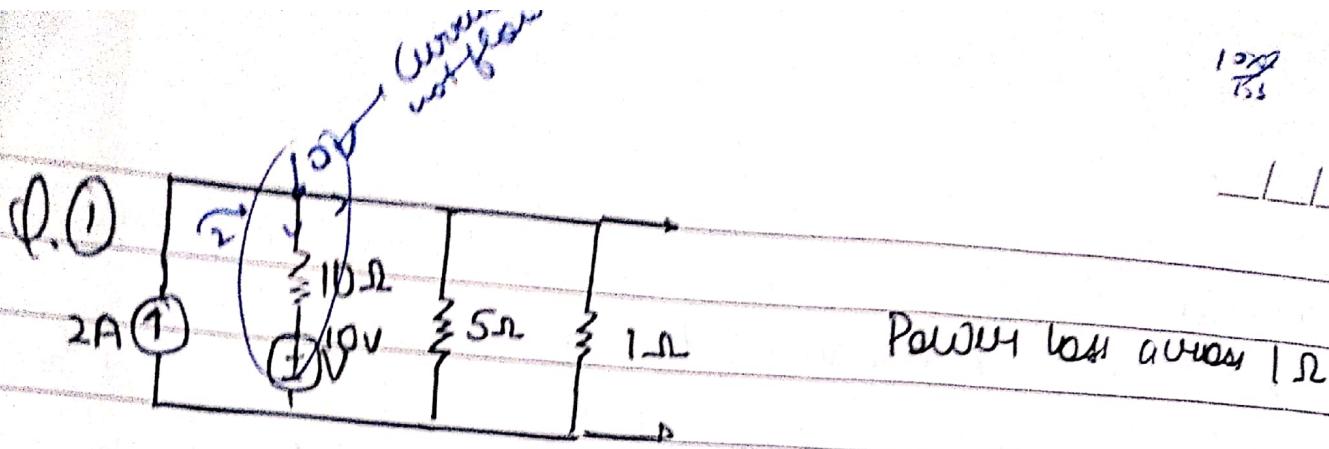

①

$$I = \frac{10}{10+3} = \frac{10}{13}$$

$$V_{oc} = 10V$$


$$3V_{oc} = 30$$

$$V_{oc} = 10V$$

②

$$I = \frac{5}{3+1} = 1A$$

DOMS

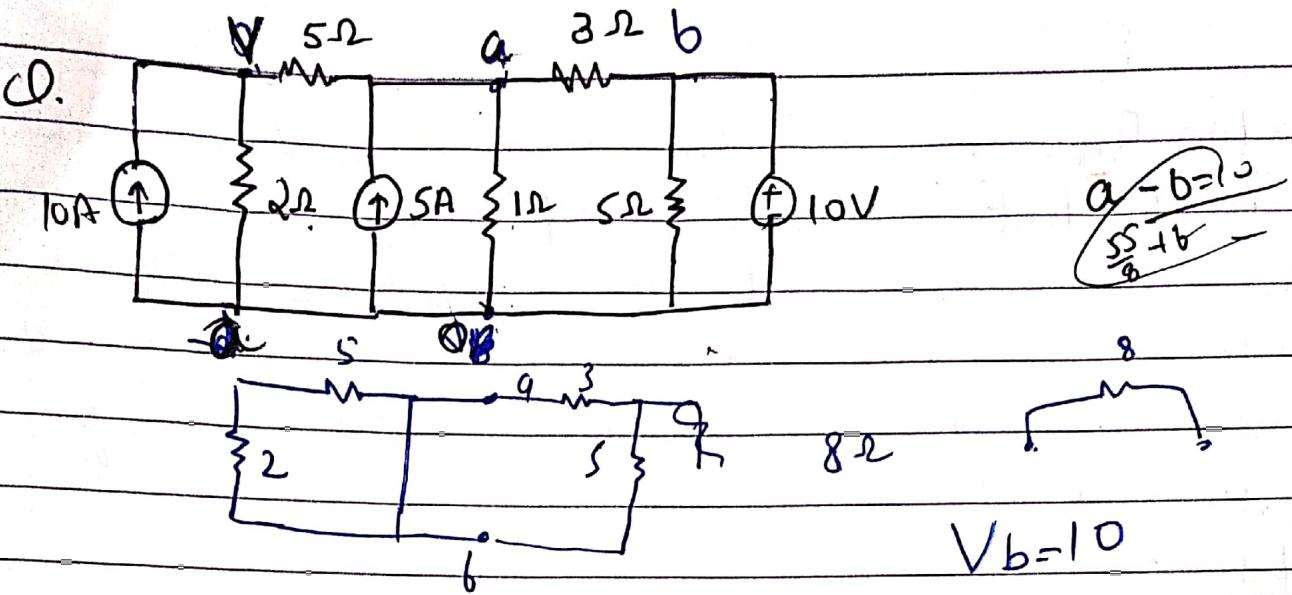

$$\frac{V}{2} + \frac{V-a}{5} = 10 \quad 7V - 2a = 100$$

$$3.125$$

$$\frac{V-a}{5} + \frac{5}{1} = a$$

$$V_{th} = 10 - \frac{55}{8} = 3.125$$

$$V-a+25=5a$$

$$V+25=6a$$

$$7V + 25 \times 7 = 42a$$

$$a = \frac{55}{8}$$

$$= \frac{165-100}{4} - \frac{65}{4}$$

$$7V - 2a = 100$$

$$42a - 175 = 100 + 2a$$

$$40a = 275$$

$$a = \frac{275}{400} = \frac{25}{4} \frac{55}{8}$$

$$V = 6a - 25$$

$$= \frac{3}{4} \times \left(\frac{55}{8} \right) - 25$$

$$= 6 \therefore$$


$$= \frac{165-100}{4} = 65$$

$$16.25$$


Norton Theorem :- A linear active network consisting of independent or and/or dependent voltage and current sources and linear bilateral network elements can be replaced by an equivalent circuit consisting of a current source in parallel way equivalent resistance.

Steps →

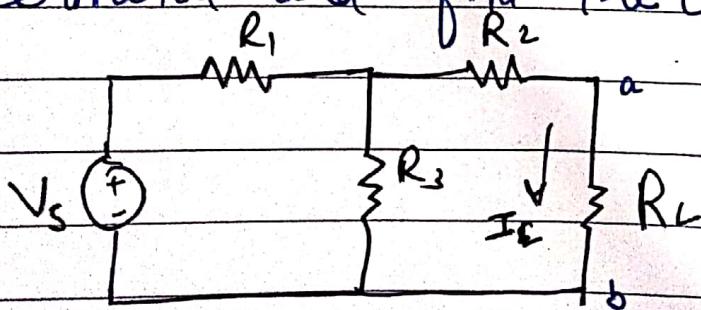- (1) Short the load terminal and find the short circuit current flowing through the shorted load terminal using conventional network analysis
- (2) Remove the load resistance and find the internal equivalent resistance of the source network after deactivating the current and voltage sources
- (3) Draw norton equivalent circuit by keeping short circuit current in parallel way the equivalent resistance and
- (4) Reconnect the load resistance across the load terminal and find the current through it.



DOMS

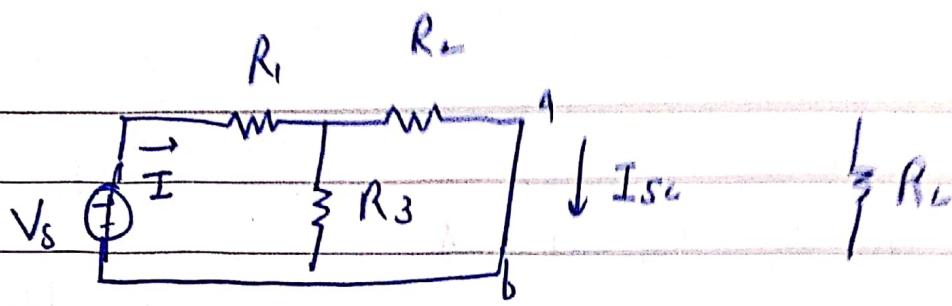


$$I = \frac{V}{R_1 + R_2 + R_3}$$


$$I_{sc} = \frac{IR_3}{R_2 + R_3}$$

$$R_{eq} = R_2 + R_1 || R_3 = \frac{R_2 + R_1 R_3}{R_1 + R_3}$$

Norton circuit

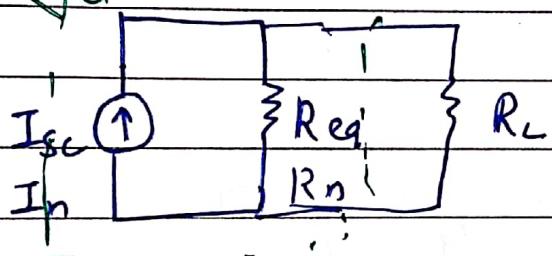
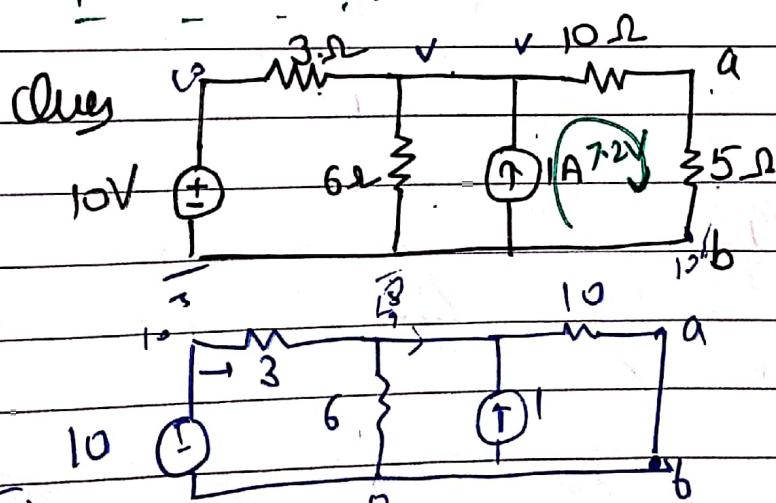
$$I_L = \frac{I_{sc} R_{eq}}{R_{eq} + R_L} \frac{V_o}{10}$$



$$I_{sc} = \frac{V}{10} \quad V = 10V$$

$$\frac{10-V}{3} + \frac{0-V}{6} + 1 = I_{sc}$$

$$I_{sc} = \frac{10-V}{3} - \frac{V}{6} + 1$$

$$I_{sc} = \frac{13-V}{3}$$

$$I_{sc} + \frac{16I_{sc}}{2} = \frac{13}{3}$$

$$I = \frac{10}{9} \quad I_{sc} = \frac{10+1}{9} = \frac{19}{9}$$

$$I_{sc} = \frac{13}{6 \times 3} = \frac{13}{18}$$

$$R_{eq} = 10 + \frac{8}{8+2} = \frac{12}{9} \Omega = R_n$$

Let V be highest potential

$$\frac{V-10}{3} + \frac{V-0}{6} + \frac{V-0}{10} - 1 = 0 \quad \frac{10V - 100 + 5V - 10}{30} = 1$$

DOMS

$$16V = 30 + 10 \\ V = \frac{30}{10} + \frac{65}{9} = 7\frac{1}{2} V$$

Jawab

$$V - I_{sc} \cdot 10 = 0$$


$$I_{sc} = \frac{V}{10} = \frac{7.2}{10} = 0.72 \text{ A}$$

$$I_L = \frac{I_{sc} R_n}{R_n + R_L}$$

$$= \frac{0.72 \times 12}{12 + 5}$$

$$= 0.72 \times \frac{12}{17}$$

$$= 0.508 \text{ A}$$

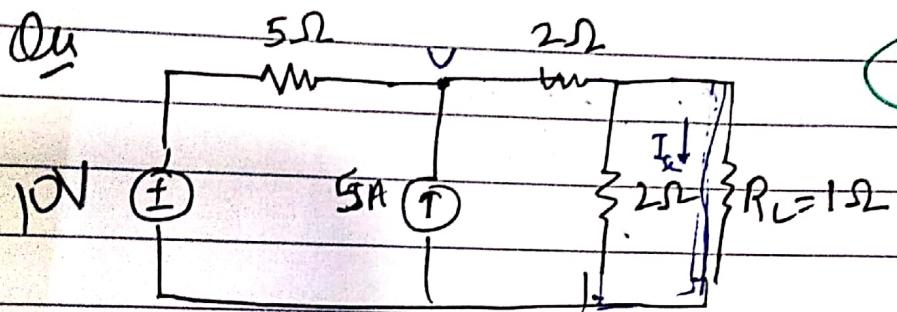

$$\frac{V - 10}{5} + \frac{-5}{9} + \frac{V - 0}{1} = 0$$

$$4V - 40 - 10 + 10V = 0$$

$$14V = 40$$

$$V = \frac{40}{14} = 10 \text{ V}$$

$$V - I_{sc}(1) = 0$$

$$I_{sc} = \frac{140}{9}$$

$$R_n = 6 \Omega$$

$$V - I_{sc}(2) = 0$$


$$I_{sc} = \frac{10}{2} = 5 \text{ A}$$

$$I_L = \frac{140/9 \times 6}{6+1} = \frac{140}{7} \times \frac{6}{7} = \frac{40}{3}$$

$$I_L = \frac{5 \times 9}{9+1} = \frac{30}{10} = \frac{30}{8} = 4$$

DOMS

Equivalent Resistance for dependent Sources

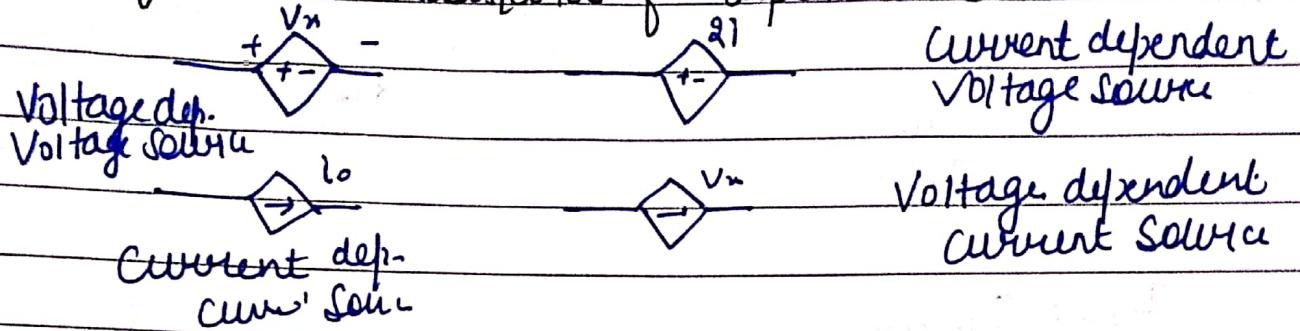

Method I. Find V_{oc} across open circuited load terminal by conventional network analysis

2. Short the load terminal and find the short circuit current through the shorted terminal.

$$R_{th} = \frac{V_{oc}}{I_{sc}}$$

Method II

Remove the load resistance & apply the DC voltage V_{dc} at open circuited load terminals


Keep the other independent sources deactivated during this time. So, due to V_{dc} , the driving current I_{dc} will flow in the circuit from the load terminal. So, the equivalent terminal

$$\text{resistance is } R_{th} = \frac{V_{dc}}{I_{dc}}$$

$$R_{th} = R_N = \underline{V_{oc}}$$

I_{sc}

$$\Rightarrow \frac{V_{dc}}{I_{dc}}$$

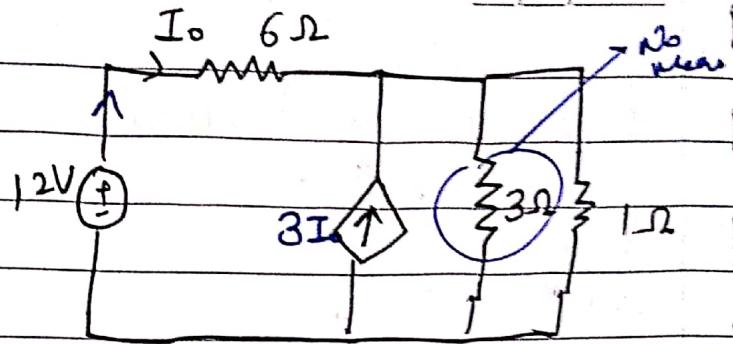

$$I_{sc} = \frac{3I_0 \times 3}{3+6}$$

$$3I_0 = \frac{12}{6+3}$$

$$I_0 = \frac{4}{9}$$

$$\frac{12-0}{6} = 2A = I_0$$

$$I_0 + 3I_0 = I_{sc}$$

$$4I_0 = I_{sc}$$

$$\boxed{I_{sc} = 8A}$$

$$\frac{V_{oc}-12}{6} + 3I_0 = \frac{V_{oc}-0}{3}$$

$$I_0 + 3I_0 = \frac{V_{oc}}{3}$$

$$\frac{V_{oc}-12}{6} - \frac{V_{oc}}{3} = -6$$


$$\frac{V_{oc}-12-2V_{oc}}{6} = -36$$

$$4I_0 = \frac{V_{oc}(12-V_{oc})}{6}$$


$$R_N = \frac{V_{oc}}{I_{sc}} = \frac{8}{8} = 1\Omega$$

$$V_{oc} = 24 - 2V_{oc}$$

$$V_{oc} = 8V$$

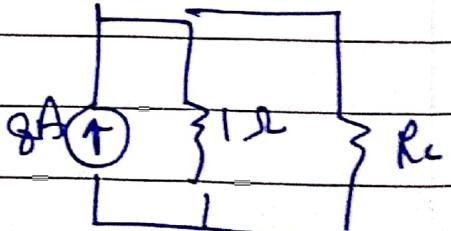

Next Method

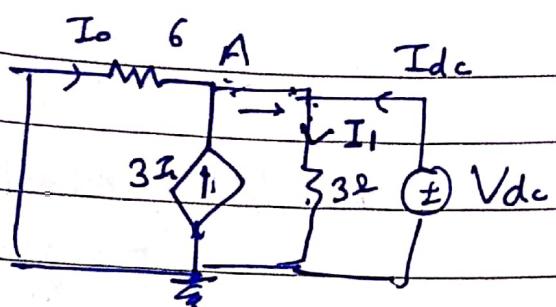

$$I_{dc} = I_1 - 3I_o - I_o$$

$$I_{dc} = I_1 - 4I_o$$

$$I_{dc} = \frac{V_{dc} - 4I_o}{3}$$

$$I_{dc} = \frac{V_{dc}}{3} - \left(\frac{4}{3} \frac{V_{dc}}{6} \right).$$

$$I_{dc} = +\frac{V_{dc}}{3}$$

$$\boxed{\frac{V_{dc}}{I_{dc}} = 1}$$

Superposition theorem

If a number of voltage and current sources are acting simultaneously in a linear network

The resultant current in any branch is algebraic sum of the currents that would be produced in it when each source acts alone replacing all other independent sources by their internal resistance


V_2 short circuit

$$I'_1 = \frac{V_1}{R_1 + R_2 R_3 / (R_2 + R_3)}$$

$$R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

$$I'_2 = \frac{I'_1 R_3}{R_2 + R_3}$$

DOMS

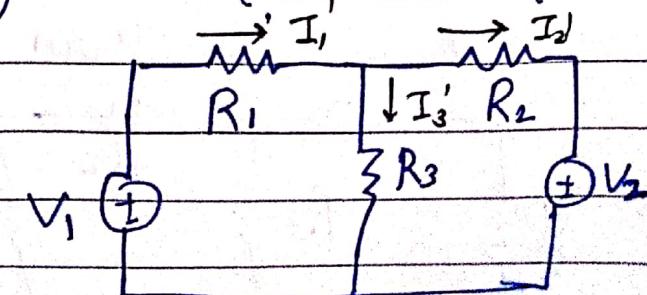

$$I_3' = I_1' - I_2'$$

Now take effect of 2nd voltage source

$$I_2'' = \frac{V_2}{R_2 + R_1 R_3}$$

$$\frac{R_2 + R_1 R_3}{R_1 + R_3}$$


$$I_1'' = \frac{I_2'' R_3}{R_1 + R_3}$$

$$I_3'' = I_2'' - I_1''$$


$$I_1 = I_1' - I_1''$$

$$I_2 = I_2' - I_2''$$

$$I_3 = I_3' + I_3''$$

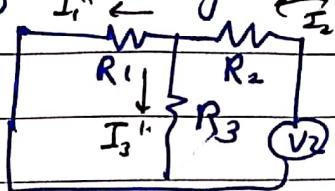


Ans

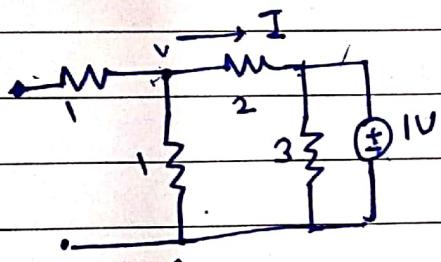


$$I' = 1/3 \quad I'' = 1/3$$
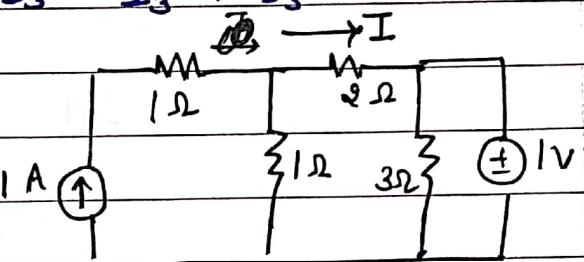
$$I = I' - I'' = \frac{1}{3} - \frac{1}{3} = 0$$




Max. Power Transfer theorem

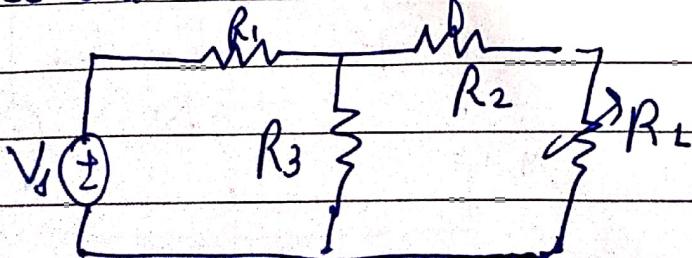A resistive load being connected to DC circuit receives the max. power when the load resistance = Internal equivalent resistance of the source network as seen from the load terminal



DOMS

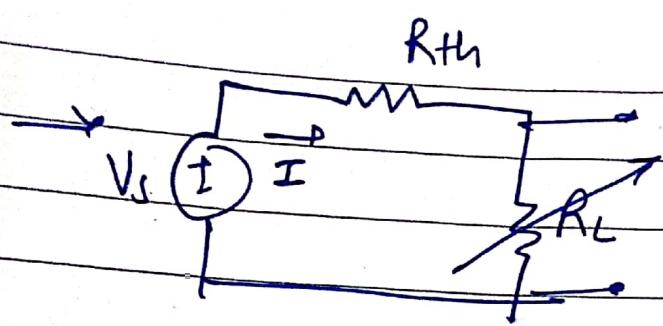

$$I = \frac{V_s}{R_{th} + R_L}$$

$$V_o = \frac{V_s}{R_{th} + R_L} \times R_L$$

$$P = VI$$

$$P = \frac{V_s^2}{(R_{th} + R_L)^2} \times R_L$$

for maxima $\frac{dP}{dR_L} = 0$

$$\frac{dP}{dR_L} = \frac{V_s^2}{R_{th} + R_L} \cdot \frac{\cancel{(R_{th} + R_L)^2} \cdot 1 - R_L \cdot 2(R_{th} + R_L)}{\cancel{(R_{th} + R_L)^2}}$$

$$= \frac{V_s^2 (R_{th} + R_L) (R_{th} + R_L - 2R_L)}{(R_{th} + R_L)^2}$$


$$R_{th} + R_L - 2R_L = 0$$

$$R_{th} - R_L = 0$$

$$\underline{[R_{th} = R_L]}$$

$$\text{Power} = \frac{V_s^2 R_L}{4R_L^2}$$

$$\boxed{P = \frac{V_s^2}{4R_L}}$$

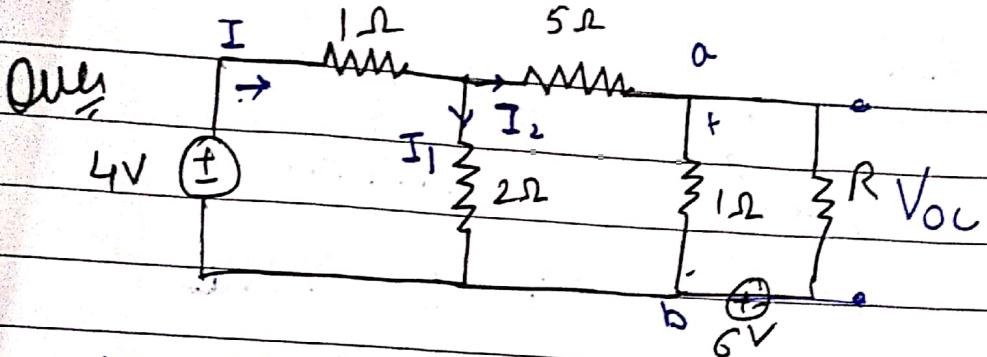

$$I = \frac{V}{R_{eq}} = \frac{4}{1} = \frac{8}{5} = 1.6$$


$$I_1 = \frac{V}{R_{eq}} = \frac{8}{5} \times \frac{2}{9} = \frac{16}{45}$$

$$V_{ab} = \frac{16}{5} V$$

$$V_{ab} - V_{bc} + 6 = 0$$

$$V_{oc} = 6 + \frac{16}{5} = \frac{32}{5} = 6.4 V$$

$$R_{th} = 1 \Omega$$

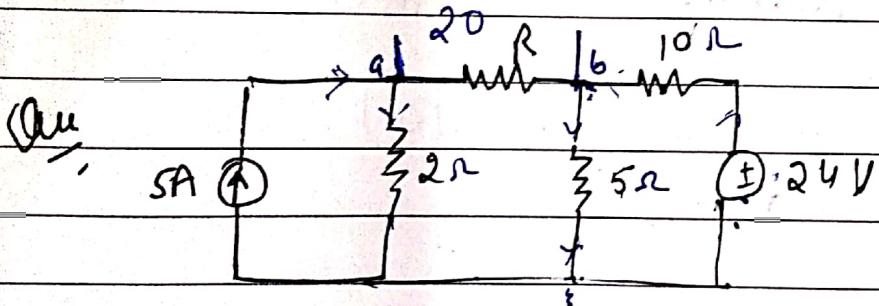

$$\frac{V_a}{2} = 5$$

$$V_a = 10$$

$$\frac{V_b - 24}{10} + \frac{V_b}{5} = 0$$

$$V_b - 24 + 2V_b = 0$$


$$3V_b = 24$$

$$V_b = 8$$

~~$$R_{th} = \frac{10 \times 2}{10 + 2} = 7 \Omega$$~~

~~$$R_{th} = \frac{10 \times 2}{10 + 2} = 7 \Omega$$~~

$$R_{th} = \frac{16}{3}$$

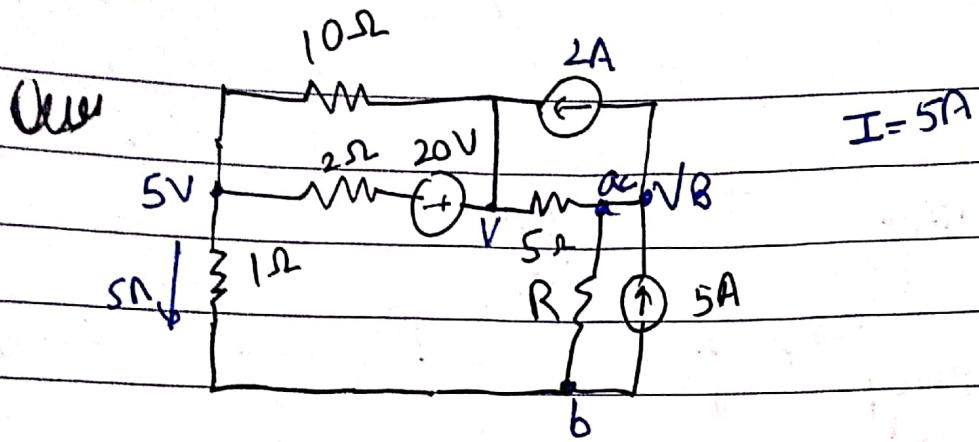

$$\frac{V - 5}{10} + \frac{V - 5 - 20}{2} + \frac{V_B - V_{oc}}{5} = 0$$

$$V - 5 + 5V - 125 + 2V - 2V_{oc} = 0$$

$$8V - 2V_{oc} = 130$$

$$4V - V_{oc} = 65$$


$$\frac{V_B - V_{oc}}{5}$$

$$\frac{45 - V_{oc}}{R} = \frac{23}{3}$$

166 Watt-Power

UNIT-2

A.C.

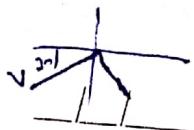


Steady State Analysis of AC Circuits

$$V(t) = V_m \sin(\omega t + \phi)$$

Amplitude Nature of signal Phase angle

$$\omega = 2\pi f = \frac{2\pi}{T}$$

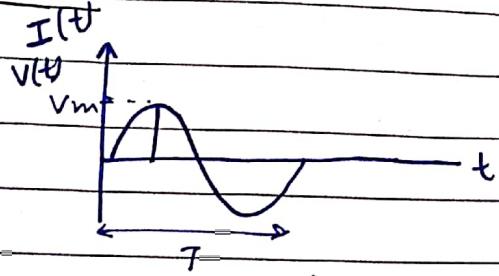

Polar & Rectangular Comp.

$$A \angle \theta = (a + jb)$$

$$A = \sqrt{a^2 + b^2}$$


$$\theta = \tan^{-1}\left(\frac{b}{a}\right)$$

$$a = A \cos \theta$$

$$b = A \sin \theta$$

$$V(t) = -5 \sin(100t - 30^\circ)$$

$$i(t) = 8 \cos(100t - 60^\circ)$$

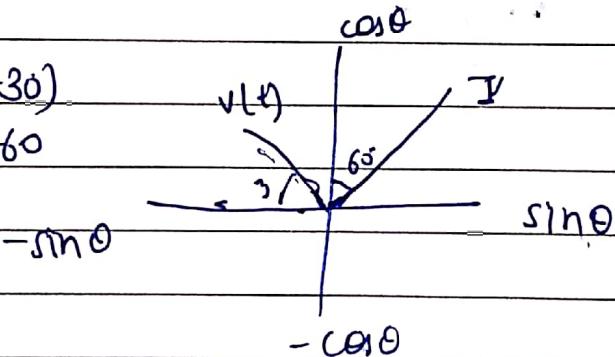

—mm— Resistor

—mm— } Reactance

} Impedance

$I(t) \rightarrow DC$

$V_{BE} - DC$

$V_{BE} \rightarrow DC + AC$

$i(t) \rightarrow AC$

$V_{BE} - AC$

$$V = IR$$

$$V_2 = L \frac{dI(t)}{dt}$$

$$V = \frac{1}{L} \int I(t) dt$$

$$I(t) = \frac{1}{L} \int V(t) dt$$

CIVIL

(m.v. I leading to V and in L, V in leading)

DOMS

$$X_L = \frac{1}{j\omega L} = \frac{-j}{\omega L}$$

Angles in
fraction
are added or
N & negative
and subtracted by
 $\frac{1}{2}\pi$ ve

$$X_L = \frac{1}{L}$$

$$V_m = 5 \sin(100t + 30^\circ)$$

$$5 < 30^\circ$$

$$\frac{V - 5 \angle 30^\circ}{2} + \frac{V_0}{2} + \frac{V}{2j} = 0$$

$$\frac{V + V}{2j} = \frac{5 \angle 30^\circ}{2}$$

$$V \left(1 + \frac{1}{2j}\right) = \frac{5 \angle 30^\circ}{2}$$

$$V \left(1 - \frac{1}{2j}\right) = \frac{5 \angle 30^\circ}{2}$$

$$V = \frac{5 \angle 30^\circ}{2 \left(1 + \frac{1}{2j}\right)} = \frac{5 \angle 30^\circ}{2 \left(\frac{2+2j}{2j}\right)}$$

$$V \left(\frac{2-j}{2}\right) = 5 \angle 30^\circ$$


$$V = \frac{5 \angle 30^\circ}{\left(\frac{2-j}{2}\right)} = \frac{5 \angle 30^\circ}{2-j}$$

$$\sqrt{5} \tan^{-1}\left(\frac{1}{2}\right)$$

$$\frac{\sqrt{5} \angle 30^\circ}{\angle 26.5^\circ} = \frac{\sqrt{5} \angle 30^\circ}{\angle 26.5^\circ}$$

$$V = \sqrt{5} \angle 56.5^\circ$$
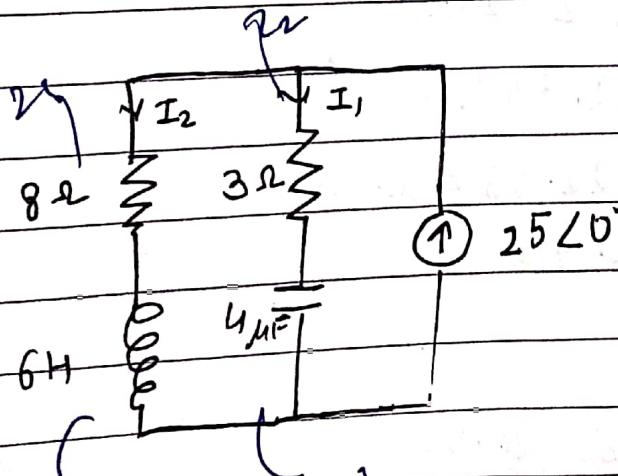
$$i = \frac{V}{2} = \frac{\sqrt{5}}{2} \angle 56.5^\circ = 1.118 \angle 56.5^\circ$$



$$8 + 6j \quad 3 - 4j$$

$$10 \tan^{-1}\left(\frac{3}{4}\right)$$

$$10 \angle 36.87^\circ$$

$$5 \angle 53.13^\circ$$

$$5 \angle -53.13^\circ$$

$$Z_1 \parallel Z_2$$

$$Z_1 + Z_2$$

$$10 \angle 36.87^\circ * 5 \angle -53.13^\circ$$

$$10 \angle 36.87^\circ + 5 \angle -53.13^\circ$$

$$50 \angle -16.26^\circ$$

$$\sqrt{125} \angle 10^\circ 30'$$

$$Z = 4.47 \angle -26.56^\circ$$

$$20 \Omega \text{MS}$$

$$I_1 = 22.36 \angle 26.5^\circ$$

$$I_2 = 11.18 \angle -63.43^\circ$$

$$I_T 10 \angle 36.87^\circ = I_1 5 \angle -53.13^\circ$$

$$\frac{I_4}{I_T} = \frac{5 \angle -53.13^\circ}{10 \angle 36.87^\circ}$$

$$\frac{I_2}{I_T} = 0.5 \angle -90.00^\circ$$

$$I_1 + I_2 = 25 \angle 0^\circ$$

$$(0.5 \angle -90 + 1) I_2 = 25 \angle 0^\circ$$

$$25 \angle 0^\circ - I_2 = 0.5 \angle -90^\circ I_2$$

$$\frac{25 \angle 0^\circ}{(0.5 \angle -90 + 1)} = I_2$$

$$I_T = \frac{25 \angle 0^\circ}{1 - 0.5j}$$

$$I_T \frac{25 \angle 0^\circ}{\sqrt{1.25}} = 22.36 \angle 26.5^\circ$$

$$I_1 = 22.36 \angle 26.5^\circ$$

$$I_2 = 0.5 \angle -90^\circ \times 22.36 \angle 26.5^\circ$$
$$= 11.18 \angle -63.43^\circ$$

$$V = IZ$$

$$= 25 \angle 0^\circ \times 4.47 \angle -26.56^\circ$$

$$= 111.75 \angle \cancel{62.44} - 26.56^\circ$$

63.43
26.56
37.07

DOMS

Inductor



$$i(t) = I_m \cos(\omega t + \phi) \quad I_m' < \phi$$

$$V_L = L \frac{di(t)}{dt}$$

$$= L \frac{d}{dt} I_m \cos(\omega t + \phi)$$

$$= -L I_m \omega \sin(\omega t + \phi)$$
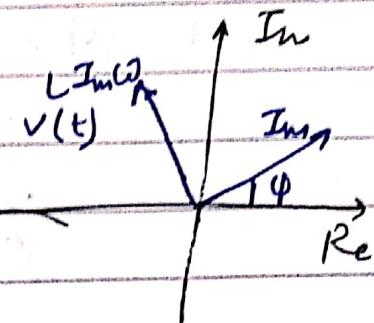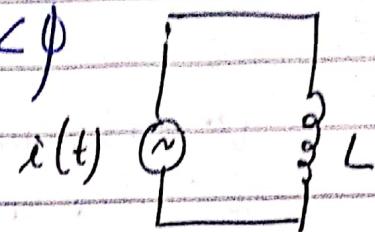
$$V_L = L I_m \omega \cos(\omega t + 90^\circ + \phi)$$




Capacitor

$$i(t) = I_m \cos(\omega t + \phi)$$

$$V = \frac{\phi}{C} = \frac{i dt}{C}$$
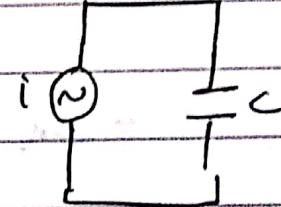
$$V = \int_C I_m \cos(\omega t + \phi) dt$$




$$Q = CV$$

$$V_c(\phi) = \frac{1}{2\pi\omega C}$$

$$= \frac{1}{\omega C} I_m \sin(\omega t + \phi)$$

$$= \frac{1}{\omega C} I_m \cos(90^\circ - (\omega t + \phi))$$
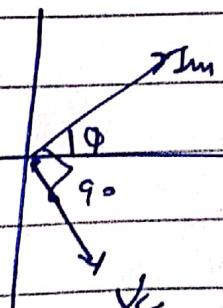
$$\therefore V_c = \frac{I_m}{\omega C} \cos(90^\circ - (\omega t + \phi))$$



Power \rightarrow

$$V = V_m \sin \omega t$$

$$i = I_m \sin(\omega t + \phi)$$

?

$$P = Vi = V_m I_m \sin(\omega t) \sin(\omega t + \phi)$$

$$= \frac{V_m I_m}{2} [\cos(\omega t - \omega t + \phi) - \cos(\omega t + \omega t + \phi)]$$

$$= \frac{V_m I_m}{2} \cos \phi - \frac{I_m V_m}{2} \cos(2\omega t + \phi)$$

Constant power

Pulsating Power

$$= \frac{V_m}{\sqrt{2}} \frac{I_m \cos \phi}{\sqrt{2}} \Rightarrow [VI \cos \phi = P_{avg}]$$

$$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} V_m I_m \sin(\omega t) \sin(\omega t + \frac{\pi}{2}) d\omega t$$


$$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} V_m I_m \sin(\omega t) \sin(\omega t) d\omega t$$


$$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} V_m I_m \sin(\omega t) \sin(\omega t - \frac{\pi}{2}) d\omega t$$

$VI \cos \phi$ = True Power / Active / Simple

$VI \sin \phi$ = Reactive Power

DOMS

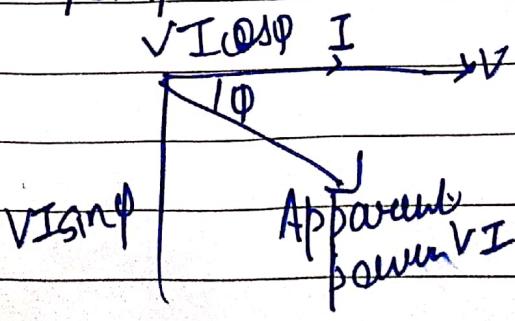

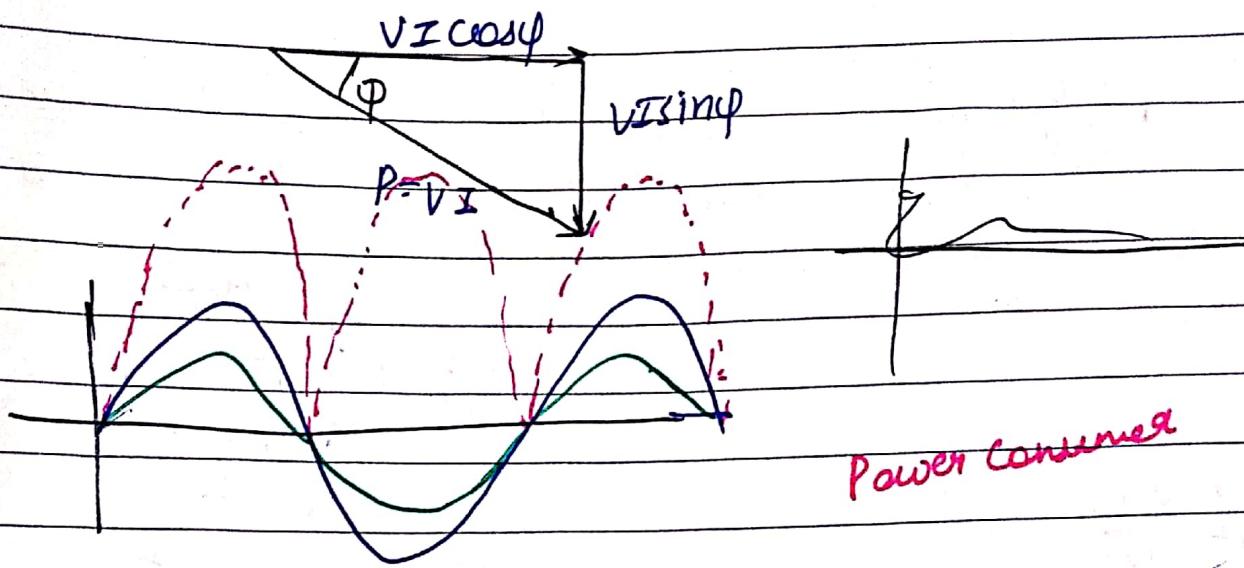

Power factor

$$\cos\phi = \frac{P}{VI} = \frac{V_R I}{VI} = \frac{IR}{I Z} = \frac{R}{Z}$$

$$I = P/V\cos\phi$$

$$kVA = \frac{kW}{\cos\phi}$$


Active Power - Power which is rarely consumed or utilised in AC circuit or power consumed in resistive circuit called Active Power.

$$P = VI\cos\phi$$

Reactive Power - Power which flows back and forth or reacts itself is called Reactive power or whenever the current is not in the phase with voltage will produce reactive power

Ques

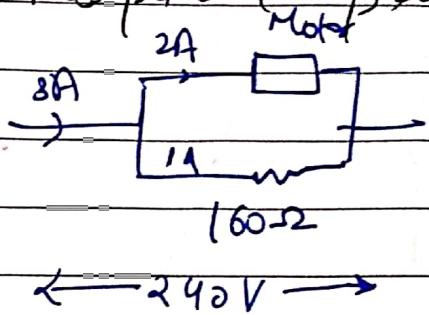A single phase 240 Volt induction motor runs balanced with 160Ω resistor. If motor takes 2A and the total current is 3A. So find the power & power factor of motor.



$$\frac{240^2}{160} = 1.5$$

$$I_m = 2A, I_H = 1.5A$$

$$I_m = I_w - j I_u$$

$$2 = I_w - j I_u$$

$$4 = I_w^2 + I_u^2 \quad \text{--- (1)}$$

$$I_m + I_H = 3A$$

$$I_w - j I_u + I_H = 3$$

$$(I_w + I_H) - j I_u = 3$$

$$(I_w + 1.5) - j I_u = 3 \quad \text{---}$$

$$(I_w + 1.5)^2 + (I_u)^2 = 9 \quad \text{--- (2)}$$

$$4 - I_w^2 = 9 - I_w^2 - 2.25 - 3 I_w$$

$$3 I_w = 9 - 4 - 2.25 = 9 - 6.25$$

$$I_w = \frac{9.75}{3} = 0.916$$

$$I_u = \sqrt{4 - (0.916)^2} = \sqrt{4 - 3.161} = 1.771$$

DOMS

$$I_m = 6.917 - j1.78$$

Power factor
if w = 0 and 1

Resonance in RLC N/W

Whenever natural frequency of oscillation of a system coincide with frequency of driving force, the two system resonate wrt each other, and system has the maximum response to a fixed magnitude. So, the phenomena by virtue of which the resulting current of an AC circuit is in the phase of the sinusoidal excitation even in the due presence of reactive components called Resonance.


The frequency at which resonance occurs is called Resonant frequency.

It is of 2 types—

→ Series Resonance (Voltage)

→ ~~Parallel~~ Parallel Resonance (Current)
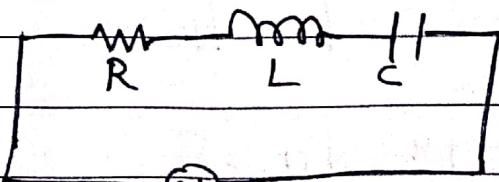
$$Z = R + j\omega L - \frac{j}{\omega C}$$



$$Z = R + j(\omega L - \frac{1}{\omega C})$$

$$\omega L - \frac{1}{\omega C} = 0$$

DOMS

$$\omega^2 = \frac{1}{LC} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$


$$f_R = \frac{1}{2\pi\sqrt{LC}}$$

With this freq.
current will be

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L = \omega L = 2\pi f L$$
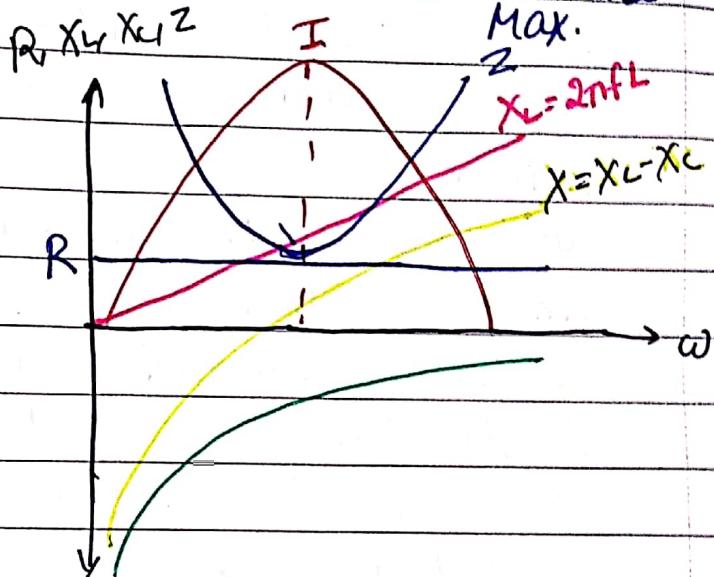
$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$




Band Width

The Range of frequencies over which the circuit current is equal to or more than 70.7% of the Max. current is known as Band Width.

$$\text{Band Width} = f_2 - f_1$$

$$f_R = \sqrt{f_1 f_2}$$

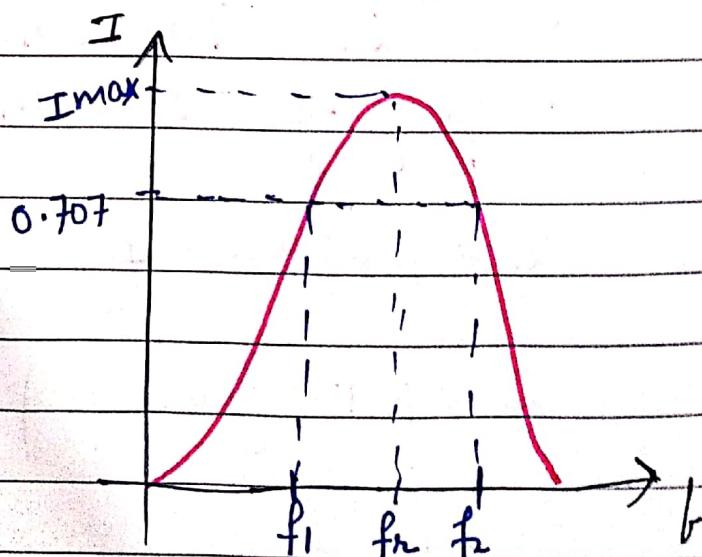

$$\frac{f_{r2}^2 - f_1}{f_1}$$

11

$$f_{r2}^2 = f_1 (f_1 + BW)$$

$$f_{r2}^2 = f_1^2 + f_1 BW$$

$$f_1^2 + f_1 BW - f_{r2}^2 = 0$$

$$f_1 = \frac{-BW \pm \sqrt{(BW)^2 + 4f_{r2}^2}}{2}$$

$$f_1 = \frac{-BW \pm 2f_{r2}}{2}$$

BW Neglect

$$f_1 = \frac{-BW}{2} + f_{r2} = \boxed{f_1 = f_{r2} - \frac{BW}{2}}$$

$$f_2 = BW + f_1 = BW + f_{r2} - \frac{BW}{2}$$

$$\boxed{f_2 = f_{r2} + \frac{BW}{2}}$$

Quality factor It is the Ratio of voltage across L or C and applied voltage

$$Q = \frac{IX_L}{IR} \text{ or } \frac{IX_C}{IR}$$

$$Q = \frac{\omega L}{R}$$

$$f_{r2} = \frac{1}{2\pi\sqrt{LC}}$$

$$\omega = \frac{2\pi}{2\pi\sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

DOMS

$$\varphi = \omega \frac{l}{R} = \frac{l}{R\sqrt{LC}}$$

$$\Phi = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Relationship b/w Quality factor and Band Width

$$\text{Ansatz: } x = \pm(x_L - x_C) = R$$

Let f_1 is the frequency when net Resistance = -ve
 f_2 " " " " + " " " " = +ve

$$\left(\omega_2 L - \frac{1}{\omega_2 c} \right) = R \quad \text{--- ①}$$

$$\left(\omega_{1L} - \frac{1}{\omega_{1C}}\right) > -R \quad \text{--- (2)}$$

① + ②

$$(\omega_1 + \omega_2)L - \left(\frac{1}{\omega_1} + \frac{1}{\omega_2}\right)\frac{l}{c} = \cancel{\infty} 0$$

$$(w_1 + w_2)L - \frac{1}{c} \left(\frac{w_1 + w_2}{w_1 w_2} \right) = 0$$

$$L = \frac{1}{\omega_1 \omega_L c}$$

$$\omega_1 \omega_2 = \frac{1}{LC}$$

$$\textcircled{1} - \textcircled{2} \quad (\omega_2 - \omega_1)L - \frac{1}{C} \left(\frac{1}{\omega_2} - \frac{1}{\omega_1} \right) = QR$$

DOMS

$$(\omega_2 - \omega_1)L + \frac{1}{C} \frac{(\omega_2 - \omega_1)}{\omega_1 \omega_2} = 2R$$

$$\cancel{L} = \frac{1}{C \omega_1 \omega_2}$$

~~$\omega_1 \omega_2 = -1$~~

$$(\omega_2 - \omega_1) \left(L + \frac{1}{C \omega_1 \omega_2} \right) = 2R$$

$$L + \frac{1}{C \omega_1 \omega_2} = \frac{2R}{\omega_2 - \omega_1}$$

$$[\omega_1 \omega_2 = \frac{1}{LC}]$$

$$L + \cancel{LC} = \frac{2R}{\omega_2 - \omega_1}$$

$$\cancel{L} = \frac{2R}{\omega_2 - \omega_1}$$

$$R = L (\omega_2 - \omega_1) \quad \text{or} \quad [\omega_2 - \omega_1 = \frac{R}{L}]$$

$$[\Phi = \frac{\omega L}{R}] \Rightarrow \frac{R}{L} = \frac{\omega}{\Phi}$$

$$\text{Now } \frac{\omega_2 - \omega_1}{\Phi}$$

Bandwidth

$$B.W = \frac{\omega_2}{\Phi}$$

Resonating frequency
quality factor

Amittance = $\frac{1}{Z}$

Conductance = $\frac{1}{R}$


Susceptance = $\frac{1}{X_L}$

PARALLEL RESONANCE

$$Z_1 = R + jX_L$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{R + jX_L} \times \frac{R - jX_L}{R - jX_L} = \frac{R - jX_L}{R^2 + X_L^2}$$

$$Y_1 = \frac{R - jX_L}{R^2 + X_L^2}$$

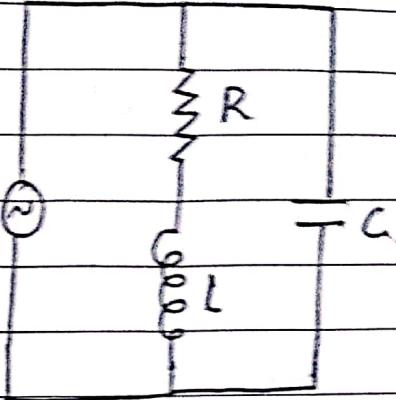

$$Z_2 = -jX_C$$

$$\therefore Y_2 = \frac{1}{Z_2} = \frac{-1}{jX_C} = \frac{j}{X_C}$$

$$Y = Y_1 + Y_2$$

$$= \frac{R - jX_L}{R^2 + X_L^2} + \frac{j}{X_C} = \frac{R}{R^2 + X_L^2} + j \left(\frac{1}{X_C} - \frac{X_L}{R^2 + X_L^2} \right)$$

Imaginary term = 0

$$\frac{1}{X_C} = \frac{X_L}{R^2 + X_L^2}$$

$$R^2 + X_L^2 = X_L X_C$$

$$R^2 + \omega^2 L^2 = \frac{\omega^2 L}{\omega C}$$

$$\omega^2 L^2 = \frac{L}{C} - R^2$$

$$\omega^2 = \frac{1}{L^2} \left(\frac{L}{C} - R^2 \right) = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\boxed{\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}$$


DOMS

$$f_R = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

Resistance of Parallel Circuit at Resonance,


$$= \frac{R^2 + X_L^2}{R} = R^2 + \left(\frac{L - R^2 C}{LC} \right) \cancel{X_L^2}$$
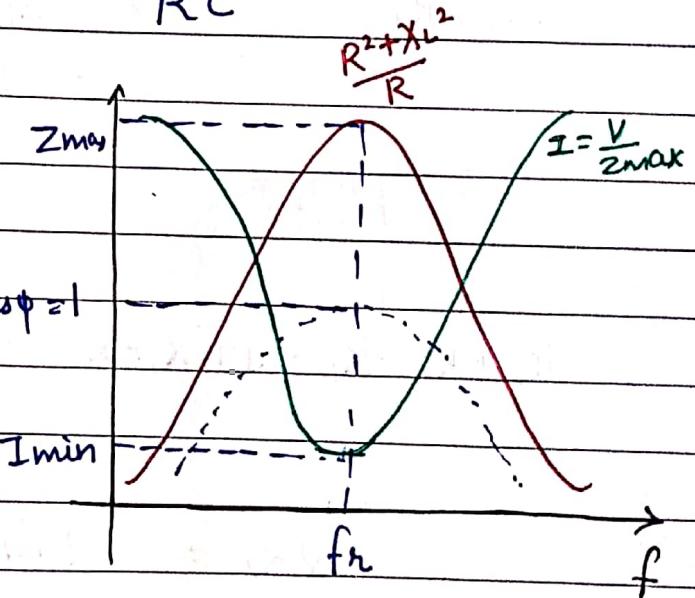
$$= \frac{R^2 + \left(\frac{L}{C} - R^2 \right)}{R} = \frac{L}{RC}$$



$$\text{PF} = \cos \phi = 1$$

Star Delta Transformation

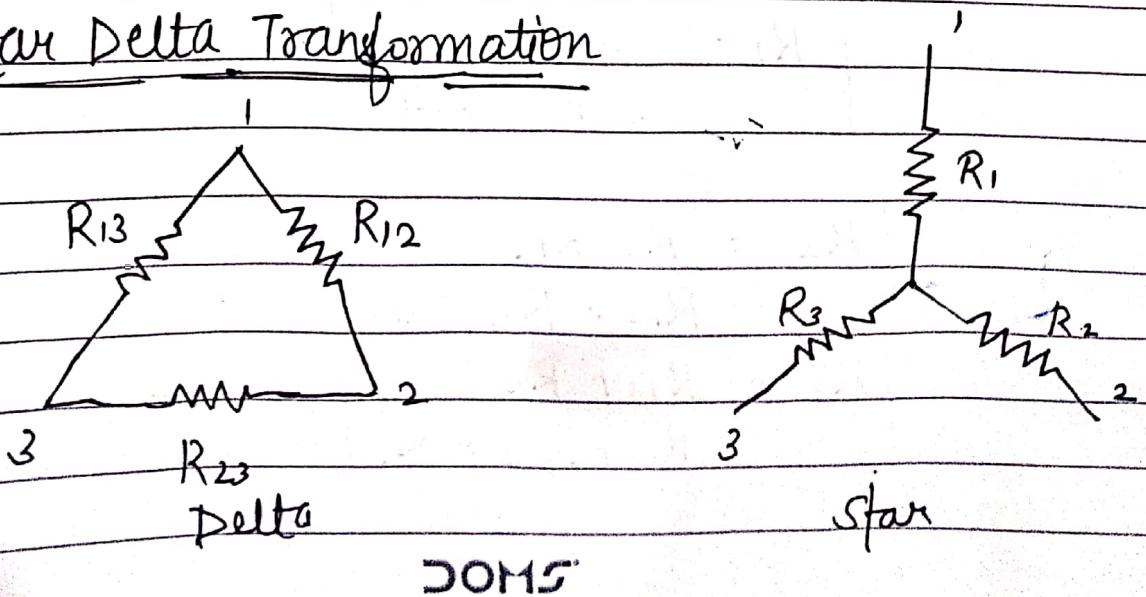

Star

Delta

$$R_1 + R_2 \Rightarrow R_{12} \parallel (R_{13} + R_{23})$$
$$= \frac{R_{12}(R_{13} + R_{23})}{R_{12} + R_{13} + R_{23}} \quad - \textcircled{1}$$

$$R_2 + R_3 \Rightarrow R_{23} \parallel (R_{13} + R_{12})$$
$$= \frac{R_{23}(R_{13} + R_{12})}{R_{23} + R_{13} + R_{12}} \quad - \textcircled{2}$$

$$R_3 + R_1 \Rightarrow R_{13} \parallel (R_{12} + R_{23})$$
$$= \frac{R_{13}(R_{12} + R_{23})}{R_{13} + R_{12} + R_{23}} \quad - \textcircled{3}$$

$$[\textcircled{1} - \textcircled{2}] + \textcircled{3}$$

$$R_1 + R_2 - R_2 - R_3 + R_3 + R_1 = R_{12}R_{13} + R_{12}R_{23} - R_{23}R_{13} - R_{23}R_{12} \\ + R_{13}R_{12} + R_{13}R_{23} \\ R_{12} + R_{13} + R_{23}$$

$$\Omega R_1 = \frac{\Omega R_{12} R_{13}}{R_{12} + R_{13} + R_{23}}$$

$$R_1 = \frac{R_{12}R_{13}}{R_{12} + R_{23} + R_{13}} \quad - \textcircled{4}$$

$$R_2 = \frac{R_{23}R_{12}}{R_{12} + R_{23} + R_{13}} \quad - \textcircled{5}$$

$$R_3 = \frac{R_{13} + R_{23}}{R_{12} + R_{23} + R_{13}} \quad - \textcircled{6}$$

DOMS

$$\frac{10 \times 10}{10+10} = \frac{100}{20} = 5 + 5 = 10$$

— / —

$$④ \times ⑤ + ⑤ \times ⑥ + ⑥ \times ④$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = R_{12}^2 R_{13} R_{23} + R_{12} R_{23}^2 R_{13}$$

$$+ R_{12} R_{23} R_{13}^2$$

$$(R_{12} R_{23} R_{13})^2$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{(R_{12} + R_{23} + R_{13})(R_{12} R_{13} + R_{23})}{(R_{12} + R_{13} + R_{23})(R_{12} + R_{13} + R_{23})}$$


$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{12} + R_{23} + R_{13}}{R_{12} + R_{23} + R_{13}}$$

$$\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = R_{12}$$

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$


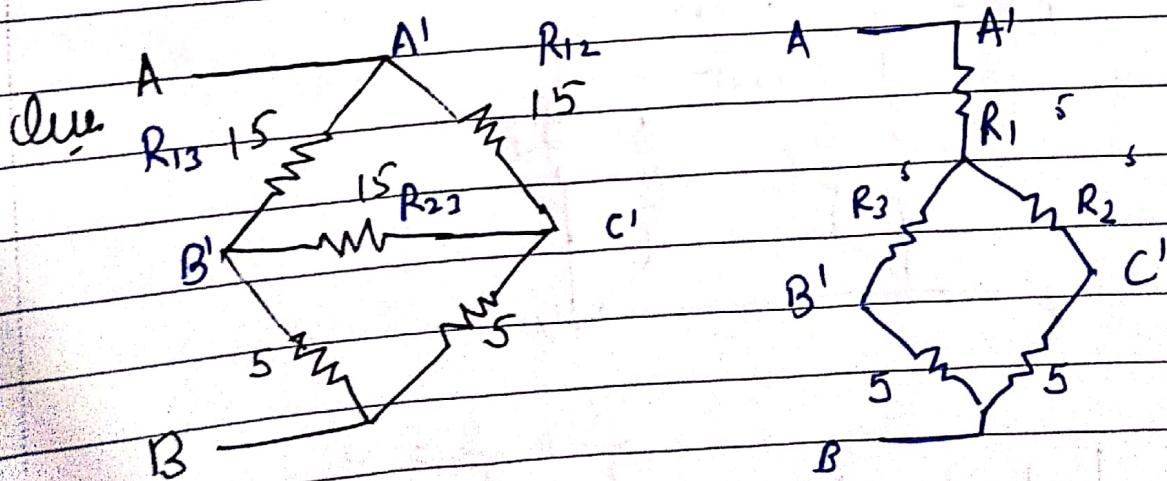
$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$



$$R_1 = \frac{15 \times 15}{15 + 15 + 15} = \frac{15}{3} = 5$$

$$R_2 = R_3 = \frac{15}{3} = 5$$

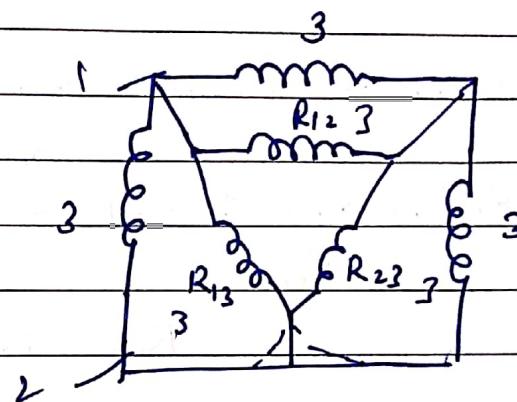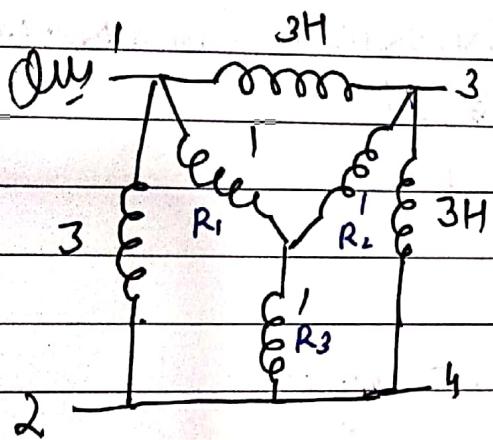
$$R_{\text{eq}} = 5 + \left(\frac{10 \times 10}{10 + 10} \right) = 5 + 5 = 10 \Omega$$



$$X_{12} = R_{12} = 1 + 1 + \frac{1 \times 1}{1} = 3$$

$$X_{13} = 3, X_{23} = 3$$

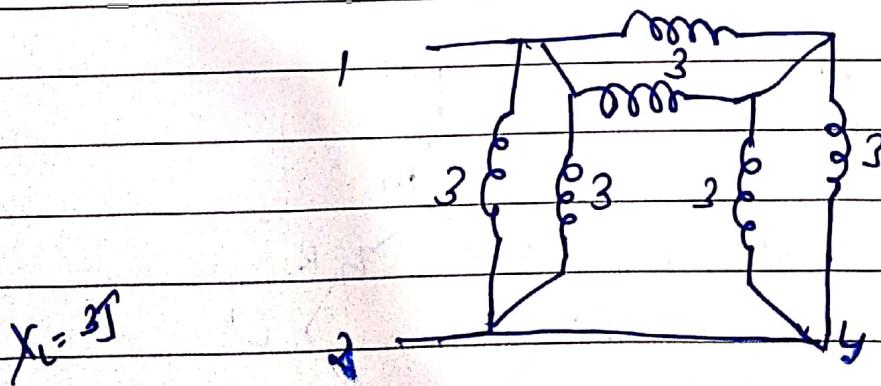Inductor in case
me $\rightarrow X_L = \omega L$
 90° is must



$$\frac{3}{2} + \frac{3}{2} = 3$$

$$\frac{1}{3} + \frac{1}{3} + \frac{1}{3} = \frac{3}{3} = 1$$

20MS