


## MOSFET Circuit:

### Limitation of BJT:

1. It has low input impedance because of forward biased emitter-base junction.
2. It has considerable noise level.

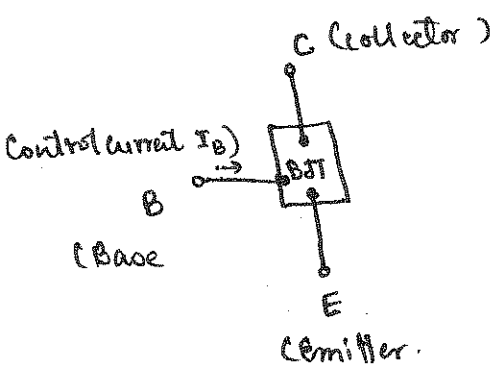
### BJT

- $\rightarrow$  Current-controlled device  
i.e.  $I_B$  controls the output current  $I_C$
- $\rightarrow$  Three terminal  
collector, Base, Emitter
- $\rightarrow$  Current conduction is due to both  $e^-$  and holes. So bipolar transistor.


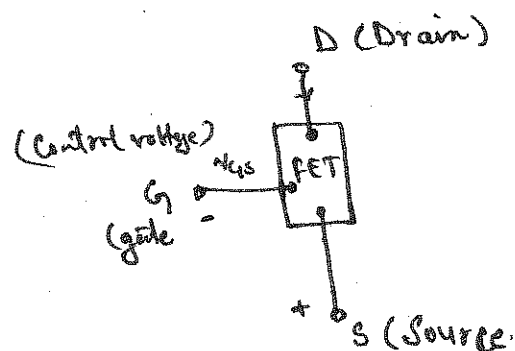
### FET


- $\rightarrow$  It is a three-terminal, voltage-controlled Semi-conductor device in which current conduction is due to the flow of only one of the two kinds of charge carriers i.e. electron or holes.  
i.e.  $V_{GS}$  controls the output current  $I_D$ .
- $\rightarrow$  Three terminal  
Drain (D)  
Source (S)  
gate (G)
- $\rightarrow$  FET can perform better amplification and Switching operation.
- $\rightarrow$  Current conduction is due to only one of the two type charge carriers.  $e^-$  or hole. So FET is called Unipolar transistor.



- The operation of the device depends on electric field intensity in the channel
- High  $\Omega/\rho$  resistance
- Power dissipation is small
- Majority carrier device
- No minority carriers.
- No leakage current and  $\therefore$  temperature effect on the device is very less and  $\therefore$  excellent thermal stability.
- FET is small in size and easy to fabricate.
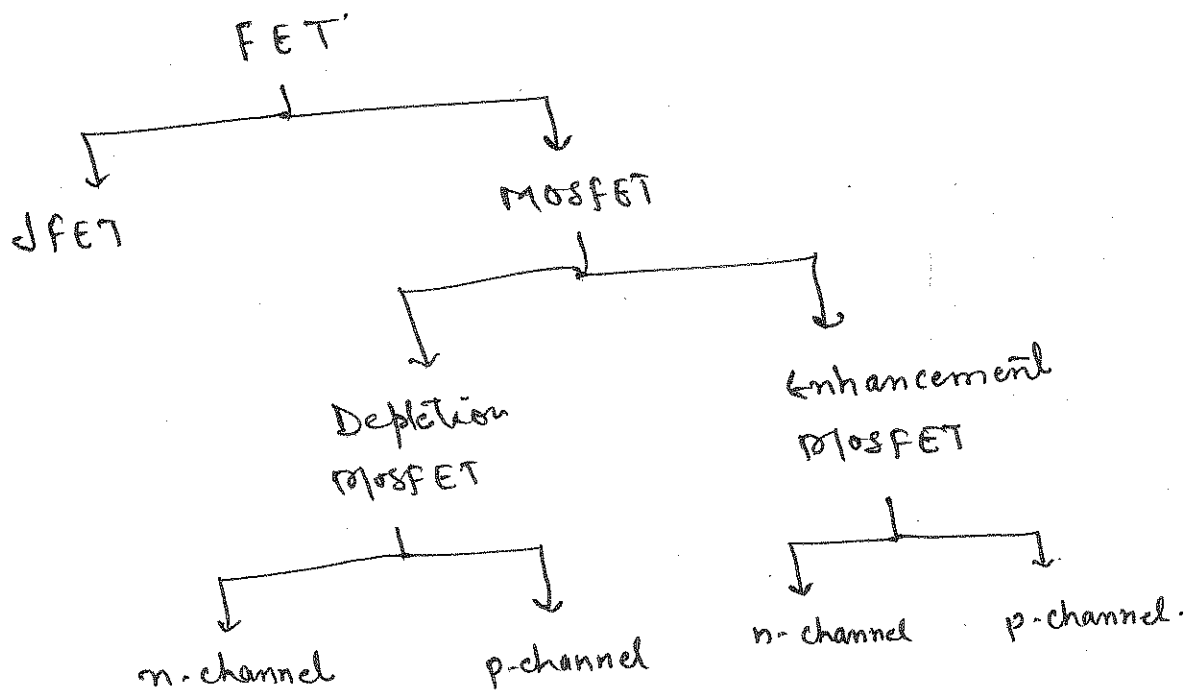
#### Disadvantage:

- Smaller ~~the~~ gain
- Smaller gain bandwidth product.



#### Regions of FET:-



**Source:** It is the source of majority carrier. i.e. It is the terminal by which majority carrier will be entering into device.

**Drain:** It drains the majority carrier. It is the terminal by which majority carrier will be leaving the device.

**Gate:** It is the terminal which control majority carriers moving from source to drain.

**Channel:** It is the region between two gates.


# 

  

## 

Take p-type <sup>substrate</sup> body and diffuse two n-type Semiconductor as in fig.

→ Conduct

 

$$V_{GS} + I_D$$

to generate current  $I_D$ .

work as an insulator (no charge passes thru, no current flow)

→ very thin layer of n-type

**IGFET**  
↓  
insulated gate

P-type Substrate

Depletion region

Internally Connected so that it can be considered as one terminal

E-F (+ to -ve)

→ Current flows from Drain to Source:

$$V_{GS} \rightarrow +ve$$

→ Depletion region



n → +ve (high potential)  
p → low potential

So depletion region res. means, charges can't flow from Drain to Source.

•  $V_{GS} \rightarrow$  no current ( $I_D = 0$ )

\*  $V_{GS} = 0$ , no channel connecting Source + drain i.e.  $I_D = 0$  (EMOSFET generally OFF)

  ie. Application of a battery b/w Drain and Source no current flows. So next is to attach a battery b/w gate + source.



collects charge. → restricted flow of charge. (insulator)  
of a dielectric in place

→ characteristics → Transfer charact. → Drain charact.

→ Induced n-channel.

→ Transfer characteristics:

It is the plot b/w drain current and gate-source voltage.


if  $V_{GS} < V_{GS(th)}$ , there is no induced channel and  $I_D = 0$ .

$$V_{GS} = V_{GS(th)}$$

EMOSFET → ON and induced channel

$$V_{GS} > V_{GS(th)}$$

 width of induced channel increases hence  $I_D$  res.




Eq<sup>n</sup> for transconductance:

for  $V_{GS} > V_{GS(th)}$   $\rightarrow$  o/p. (current)

$$I_D = K (V_{GS} - V_{GS(th)})^2$$

 
$$K = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(th)})^2}$$


 
### \* Drain characteristics:

The drain characteristics is the graph b/w drain current ( $I_D$ ) and drain-source voltage ( $V_{DS}$ ).

From the graph, it can be seen that most of the part of the curve is horizontal, showing constant drain current. Hence in this part of curve the E-MOSFET behaves as a constant current source.



Q: The data sheet for an E-MOSFET gives  $I_{D(on)} = 500\text{mA}$  at  $V_{GS} = 10\text{V}$  and  $V_{GS(th)} = 1\text{V}$ . Determine the drain current for  $V_{GS} = 5\text{V}$ .

here  $V_{GS(on)} = 10\text{V}$

$$I_D = K (V_{GS} - V_{GS(th)})^2 \rightarrow \textcircled{1}$$

$$K = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(th)})^2} = \frac{500\text{mA}}{(10\text{V} - 1\text{V})^2} = 6.17\text{mA/V}^2$$


put values in Eq<sup>n</sup> ①

$$I_D = 6.17 (5\text{V} - 1\text{V})^2$$


$$I_D = 98.7\text{mA}$$

# n-channel Depletion MOSFET:

Symbol:

 

Construction/working:

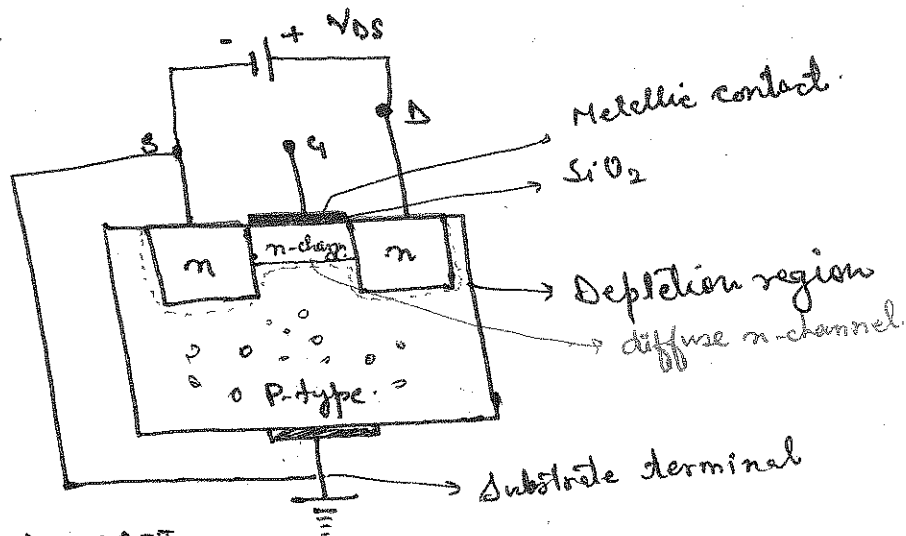

3 ways to operate: DMOSFET

i)  $V_{GS} = 0$  ( $I_{D1}$ )

$V_{DS} \rightarrow +V \rightarrow I_D$  flows.

as  $V_{DS}$   $\uparrow$   $I_D$   $\uparrow$ , at certain point  $\uparrow$ ing  $V_{DS}$   $I_D$  doesn't change i.e.  $I_D$  becomes constant.

$\because$  of the reverse biasing depletion region becomes wider and wider and channel becomes thinner

ii)  $V_{GS} = -ve$  ( $I_{D2}$ )

In this case, the -ve terminal at the gate pushes  $e^-$  towards the substrate p, where the  $e^-$  recombines with the holes, which results in thinner diffuse channel i.e.  $I_D$   $\downarrow$ .

$\Rightarrow V_{GS} \rightarrow -ve \Rightarrow I_D$   $\downarrow$ .

iii)  $V_{GS} = +ve$  ( $I_{D3}$ )

In this case, the +ve terminal at gate attracts the  $e^-$ , resulting in thicker diffuse channel.

$V_{GS} = +ve \Rightarrow I_D$   $\uparrow$

Conclusion:-

$\Rightarrow I_{D3} > I_{D1} > I_{D2}$

Q. For a certain D-MOSFET,  $I_{DSS} = 10 \text{ mA}$  and  $V_{GS(off)} = -8 \text{ V}$

i) Is this an n-channel or a p-channel

ii) Calculate  $I_D$  at  $V_{GS} = -3 \text{ V}$ .

iii) " " " "  $V_{GS} = +3 \text{ V}$ .


i) The device has a negative  $V_{GS(off)}$ .  $\therefore$  n-channel DMOSFET.

$$\begin{aligned} \text{ii) } I_D &= I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 \\ &= 10 \text{ mA} \left( 1 - \frac{-3}{-8} \right)^2 = 3.91 \text{ mA} \end{aligned}$$

$$\begin{aligned} \text{iii) } I_D &= I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 \\ &= 10 \text{ mA} \left( 1 - \frac{+3}{-8} \right)^2 = 18.9 \text{ mA} \end{aligned}$$

→ MOSFET characteristics:  $\left\{ \begin{array}{l} \text{Transfer char.} \\ \text{Drain charac.} \end{array} \right.$

 is Drain characteristics: ( $I_D$  vs  $V_{DS}$ )




Pinch off voltage.

It is the minimum drain-source voltage at which the drain current becomes constant.

ii) Transfer characteristics: ( $I_D$  vs  $V_{GS}$ ).

 i)  $V_{GS} = 0$ ,  $I_D = I_{DSS}$

i.e.  $I_{DSS}$  is the value of  $I_D$  when gate and source terminal are shorted i.e.  $V_{GS} = 0$



ii)  $V_{GS} \rightarrow -V_c$ ,  
when  $V_{GS}$  is  $-V_c$ ,  $I_D$  goes below the value of  $I_{DSS}$  till  $I_D$  reaches zero i.e.  $V_{GS} = V_{GS(off)}$ .

iii)  $V_{GS} \rightarrow +V_c$   
when  $V_{GS}$  is  $+V_c$ ,  $I_D$  goes above the value of  $I_{DSS}$ .

Drain Current:

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 \rightarrow \text{Shockley's Eqn.}$$


Control variable (input voltage)  $\rightarrow V_{GS}$

output current  $\rightarrow I_D$

constant  $\rightarrow I_{DSS}$
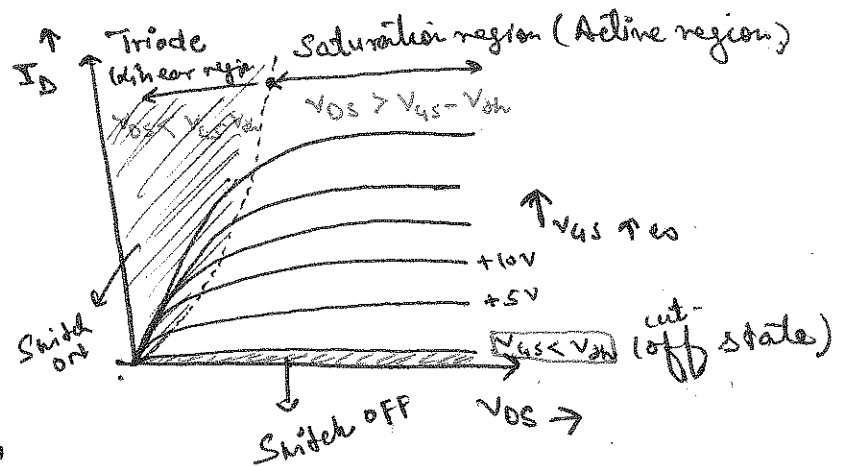
# MOSFET as a Switch:

Drain characteristics of E-MOSFET: ( $I_D$  vs  $V_{DS}$ ) for a given  $V_{GS}$




→ Cut-off Region ( $V_{GS} < V_{th}$ )

In this region, the MOSFET is in OFF state, as there is no induced channel b/w drain & source

→ In both Linear and Saturation region, the MOSFET is in ON state. Difference is that in linear region, the channel is continuous and  $I_D \propto$  to the <sup>resistance of the</sup> channel.

→ In Saturation region, as  $V_{DS} > V_{GS} - V_{th}$ , the channel pinches off i.e. broadens & resulting in a constant drain current  $I_{D0}$ .

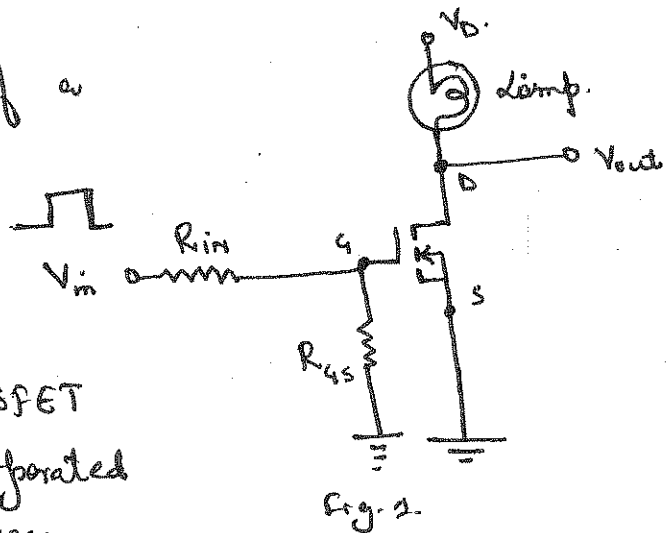To understand the operation of a MOSFET as a Switch, we consider the simple circuit as Fig. 1.



→ In order to operate a MOSFET as a Switch, it must be operated in Cut-off and linear region.

- Assume the device is initially OFF.
- i)  $V_{GS} > V_{th}$  (Switch ON).

$V_{GS}$  is made positive, the MOSFET enters in the linear region and the Switch is ON. This makes the light to turn ON.

- ii)  $V_{GS} < V_{th}$  (or  $= 0$ ) (Switch OFF):


If the input  $V_{GS}$  is 0 or  $< V_{th}$ , the MOSFET enters in cut-off state and turns OFF. This in turn will make the light to turn OFF.


 
## Small Signal operating model of MOSFET:

The main purpose of Small signal is to find the ac current and ac voltage.

So let us consider a circuit which consists of both ac and dc source.



Voltages: (3-Types)

$v_{gs} \rightarrow$  ac voltage

$V_{GS} \rightarrow$  DC voltage

$$V_{GS} \rightarrow V_{gs} + V_{GS} \rightarrow \textcircled{1}$$

↑  
Total voltage

Similarly Current:

$i_d \rightarrow$  ac current

$I_D \rightarrow$  dc current

$i_D \rightarrow$  total current

$$i_D = i_d + I_D \rightarrow \textcircled{2}$$

is current  $i_D$ :

Now:  $I_D = \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_t)^2 \rightarrow \textcircled{3}$

Annotations:   
 -  $\frac{W}{L}$ : Transistor aspect ratio i.e. width/length  
 -  $V_t$ : threshold voltage  
 -  $V_{GS}$ : total voltage

i.e. (in saturation region)

So,

$$i_D = \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_t)^2$$

total current ↑

$$= \frac{1}{2} k_n \frac{W}{L} ((V_{gs} + V_{GS}) - V_t)^2 \quad \text{or} \quad \frac{1}{2} k_n \frac{W}{L} ((V_{GS} + V_{gs}) - V_t)^2 \rightarrow \textcircled{4}$$

$$(a+b-c)^2 = a^2 + b^2 + c^2 + 2ab - 2bc - 2ca$$

$$i_D = \frac{1}{2} k_n \frac{W}{L} \left[ V_{GS}^2 + V_{GS}^2 + V_t^2 + 2V_{GS} \cdot V_{GS} - 2V_{GS}V_t - 2V_tV_{GS} \right]$$

Considering the ac component,

$$i_d = \frac{1}{2} k_n \frac{W}{L} \left[ 2V_{GS} \cdot V_{gs} - 2V_{gs}V_t \right]$$

$$i_d = \frac{1}{2} k_n \frac{W}{L} \left[ 2V_{gs}(V_{GS} - V_t) \right]$$

$$\boxed{i_d = k_n \frac{W}{L} [V_{gs}(V_{GS} - V_t)]}$$

↑  
ac Current

in a Small Signal of MOSFET

\* Transconductance: ( $g_m$ )

$$\text{Trans} \rightarrow \frac{O/P}{I/P}$$

conductance  $\rightarrow$  current/voltage.


So

$$\text{Transconductance} = \frac{i_d}{V_{gs}} \quad (g_m)$$

$$\therefore \boxed{g_m = \frac{i_d}{V_{gs}}}$$

$$\text{for small signal } i_d = k_n \frac{W}{L} [V_{gs}(V_{GS} - V_t)]$$
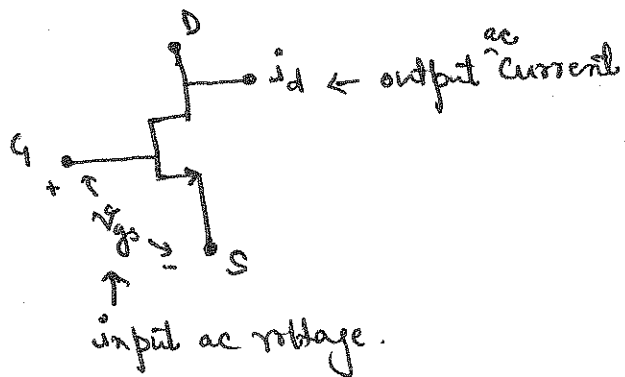
$$\therefore \boxed{g_m = k_n \frac{W}{L} [V_{GS} - V_t]}$$




### Voltage gain: ( $A_v$ )

$$\text{voltage gain} = \frac{\text{output voltage}}{\text{input voltage}}$$

$$A_v = \frac{V_{ds}}{V_{gs}}$$

$$A_v = \frac{i_d \cdot R_D}{V_{gs}}$$


 


$$A_v = g_m \cdot R_D$$

↑  
voltage gain

### Small Signal Equivalent Model is:

MOSFET

  


$$i_d = g_m \cdot V_{gs}$$

$$g_m = \frac{i_d}{V_{gs}}$$

$$A_v = g_m \cdot R_D$$

Without internal  
Resistance  $r_o$

 

$$r_o = \frac{V_o}{i_d}$$

$$A_v = g_m \cdot (R_D \parallel r_o)$$

With internal  
resistance  
 $r_o$


## Procedure for Small Signal Model:

- i) Consider 3 terminals G.D.S.
- ii) There is no connection b/w Gate and Source and there is no current (input) flowing b/w Gate and Source.
- iii) But there is a current flow b/w Drain and Source terminals.
  - That is the constant current, why? In the saturation region current is constant, so we can represent it with constant small signal current source  $g_m v_{gs}$  i.e.  $i_d$ .  
↪ ac. current.


# MOSFET Amplifier Configurations:-

(8)

 i) Common Source Configuration:- → Without  $R_s$   
→ With  $R_s$



is Small Signal model:

 

ii) Input resistance: ( $R_{in}$ )

$$R_{in} = R_{sig} = \infty$$

$$\because R = \frac{V}{i} = \frac{V}{0} = \infty$$

Any Configuration with gate (G) as input have  $R_{in} = \infty$ ,  $\because$   $i_g$  current is zero.

iii) Output resistance ( $R_{out}$ ):

$$R_{out} = r_o \parallel R_D$$

$$r_o \gg R_D$$

$$R_{out} = \frac{r_o R_D}{r_o + R_D}$$

$$= \frac{r_o R_D}{r_o}$$

$$R_{out} = R_D$$

iv) voltage gain ( $A_v$ ):

$$A_v = \frac{V_o}{V_i}$$

$$= \frac{-i_d (R_D \parallel r_o)}{V_{gs}}$$



$$A_v = -g_m (R_D \parallel r_o) \quad (\because \frac{i_d}{V_{gs}} = g_m)$$

Overall gain :- ( $G_v$ )

$$G_v = \frac{V_o}{V_{sig}} = \frac{V_o}{V_{in}} = \frac{-i_d (R_D \parallel r_o)}{V_{gs}} = -g_m (R_D \parallel r_o)$$

$$G_v = -g_m (R_D \parallel r_o)$$
  
## Common Source Configuration: (with $R_S$ )



ii) Input resistance: ( $R_{in}$ )

$$R_{in} = R_{sig} = \infty$$

iii) output resistance: ( $R_o$ ):


$$R_o = R_D$$

iv) Voltage gain ( $A_v$ ):

$$A_v = \frac{V_o}{V_i}$$

$$A_v = -i_d R_D$$

input side:

 

To get  $V_{input}$  consider the input part: as

$$V_{gs} = \frac{1/g_m}{1/g_m + R_S} V_i$$

we have used voltage divider formula, which states that resistance in that branch divided by the sum of the resistance multiplied with source voltage.

$$V_{gs} = \frac{1}{1 + g_m R_S} \cdot V_i$$

$$V_i = V_{gs} (1 + g_m R_S)$$

### Conclusion / Remarks:

- The CS amplifiers has infinite input impedance and a moderately high output resistance, and a high voltage gain
- Reducing  $R_D$  reduces the output resistance of a CS amplifier, but unfortunately, the voltage gain is also reduced.  
Alternate design can be employed to reduce the output resistance.
- A CS amplifier suffers from poor high frequency performances as most transistor amplifiers do.


$$A_v = \frac{-i_d \cdot R_D}{V_{gs} (1 + g_m R_s)}$$

$$A_v = \frac{-g_m R_D}{(1 + g_m R_s)} \quad \left( \text{as } \frac{i_d}{V_{gs}} = g_m \right)$$
 
## ② Common drain Configuration is

In Common drain Configuration the drain terminal is common between input and output. So Drain terminal connected to ground. Source as output and Gate as input.

\* If there is a resistance connected to source terminal, then hybrid T-model is considered for the MOSFET.



ii Input resistance:  $R_{in}$



$$R_{in} = R_{sig} = \infty \quad \text{if } g = 0$$

iii output resistance:  $R_o$

$$R_o = \frac{1}{g_m} \parallel R_s$$

$$\because R_s \gg \frac{1}{g_m}$$
  
$$R_o \approx \frac{1}{g_m} \quad \left( R_o = \frac{\frac{1}{g_m} \cdot R_s}{\frac{1}{g_m} + R_s} \right)$$






Voltage gain ( $A_v$ ):

Considering the output part.

using the voltage divider formula

 

$$V_o = \frac{R_s}{R_s + 1/g_m} \cdot V_i$$

$$A_v = \frac{\frac{R_s}{R_s + 1/g_m} \cdot V_i}{V_i} \quad \left( \text{as } A_v = \frac{V_o}{V_{in}} \right)$$


$$\therefore \boxed{A_v = \frac{R_s}{R_s + 1/g_m}}$$

Total/overall gain:  $G_v$ .

$$G_v = \frac{V_o}{V_i}$$

$$\boxed{G_v = \frac{R_s}{R_s + 1/g_m}}$$

## JET Amplifier Configuration:

 


- i) Common Source
- ii) Common Gate
- iii) Common drain

### Concepts:

Configuration	G	S	D
CS	i/p	GND	o/p
CG	GND	i/p	o/p
CD	i/p	<del>o/p</del>	GND

In general

G → i/p.
D → o/p.

 

### Steps:

- i) Amplifier circuit is converted to Small Signal model
- ii) Get expression from  $R_{in}$ ,  $R_o$ .
- iii) Get gain,  $A_v$ ,  $V_i$ ,  $V_o$ .