
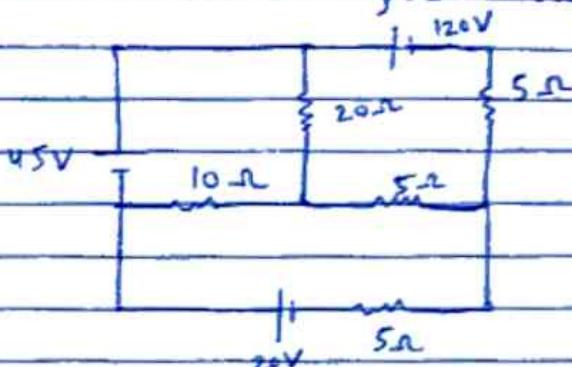


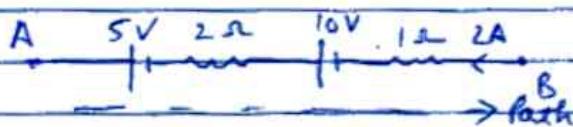Q) Determine current through 2Ω resistor in the circuit shown




Q) Find potential diff. b/w 2 points



$$V_A - 5 + 2 \times 2 - 10 + 2 \times 1 = V_B$$

$$V_A - 8 = V_B$$


$$V_A - V_B = 8$$

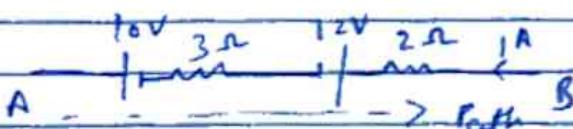


$$V_A - 10 + 3 \times 1 + 12 + 2 \times 1 = V_B$$

$$V_A - V_B = 7$$

Q) Find p.d. b/w A & B

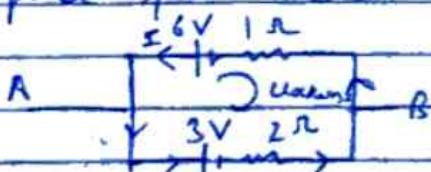

$$-6 + 1 + 2I + 3 = 0, 3I = 3, I = 1A$$

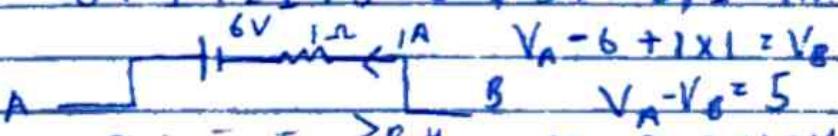

$$V_A - 6 + 1 \times 1 = V_B$$

$$V_A - V_B = 5$$

$$V_A - 3 - 2 \times 1 = V_B$$

$$V_A - V_B = 5V$$

Applying KVL to loop (II)

$$-2.5I_1 - 5I_1 + 3(I - I_1) = 0$$

$$-7.5I_1 + 3I - 3I_1 = 0$$

$$3I = 10.5I_1$$

$$I = 3.5I_1$$

$$6(3.5)I_1 - 3I_1 = 12.5$$


$$18I_1 = 12.5$$

$$I_1 = \frac{12.5}{180}$$

$$= \frac{12.5}{180}$$

$$I = 3.5 \times \frac{12.5}{180} = 2.43 A$$

(Q) Find current through all loops

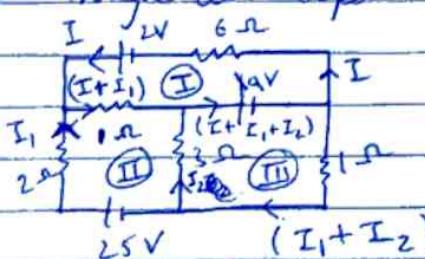

clockwise

$$2I_1 + 2I_2 = 8$$

$$I_1 + 4I_2 = 19 \times 2$$

$$2I_1 + 2I_2 = 8$$

$$2I_1 + 84I_2 = 399$$

Apply KVL in Mesh (I)

$$-2 + 6I + 19 + I + I_1 = 0$$

$$7I + I_1 = 17 \quad \text{--- (1)}$$

$$-63I_2 = 399$$

Mesh (II)

$$-2I_1 - I - I_1 - 3I_2 + 25 = 0$$

~~$$-2I_1 - I - 3I_2 + 25 = 3I_1 + I + 3I_2$$~~

$$I_2 = \frac{399}{63}$$

$$= 6.2 A$$

Mesh (III)

$$-19 - I_1 - I_2 - 3I_2 = 0$$

$$-I_1 - 4I_2 = -19$$

~~$$2I_1 + 3I_2 = 51$$~~

$$7I + I_1 = 17 \quad \text{--- (2)}$$

~~$$3I_1 + I + 8I_1 = 25$$~~

~~$$- - -$$~~

48

$$7I + I_1 = 17$$

$$2I_1 + 2I_2 = 8$$

~~$$2I_2 + 7I + 2I_1 = 25$$~~

Q4


~~$$-2I_2 - 2I_1 = -8$$~~

Supermesh is when there is current source b/w 2 loops

Page No. _____

Date: _____

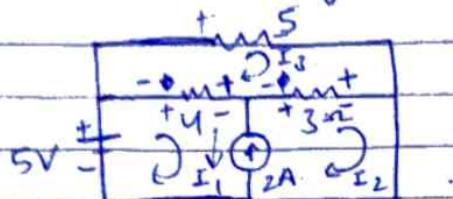Q Find current through 5Ω using mesh analysis



2


$$I_1 \downarrow \oplus_{in} \uparrow I_2$$

$$\begin{aligned} I_2 + 2 &= I_1 \dots 0 \\ I_2 - I_1 &= -2 \end{aligned}$$

From

Equation of current source
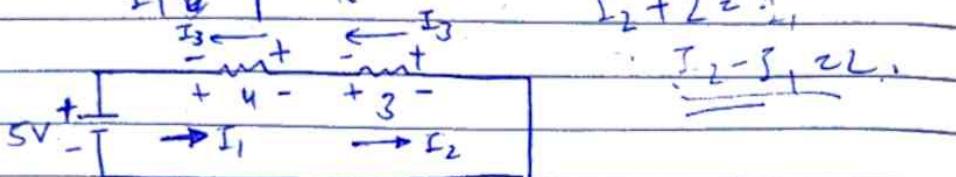
$$I_1 \downarrow \oplus_{in} \uparrow I_2 \quad I_2 - I_1 = 2 \dots ①$$



Applying KVL to Supermesh

$$-4I_1 + 4I_3 - 3I_2 + 3I_3 + 5 = 0$$

$$-7I_3 - 3I_2 - 4I_1 = -5 \dots ②$$

Applying KVL to Loop ③

$$-5I_3 - 3I_3 + 3I_2 - 4I_3 + 4I_1 = 0$$



$$-12I_3 + 3I_2 + 4I_1 = 0 \dots ③$$

Solving eq ①, ②, ③.

$$I_1 = 0.8571 A, I_2 = 2.8571 A, I_3 = 1 A$$

$$I_{5\Omega} = 1 A$$

Q Find V so that $I_1 = 0 A$.

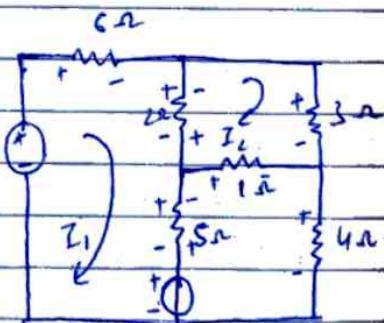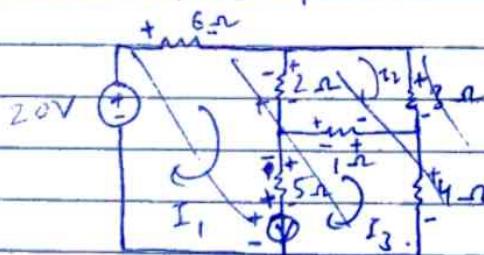

Current source $\frac{V}{R}$
Voltage source $\frac{I}{R}$
Redundant (reduce)

Nodal analysis

Page No.:

Date:

Ans

Applying KVL to mesh ①

$$20 - 6I_1 + 2I_1 - 2I_2 + 5I_1 - 5I_3 - V = 0$$

$$I_1 = 0 \text{ A}$$

$$20 - 2I_2 - 5I_3 - V = 0$$

$$20 = V + 2I_2 + 5I_3$$

Applying KVL to mesh ②

$$-2I_1 + 2I_2 - 3I_2 + I_2 + I_3 = 0$$

$$I_1 = 0$$

$$I_3 = 0$$

$$3I_2 - 3I_2$$

Applying KVL to mesh ③

$$20 - 6I_1 - 2I_1 + 2I_2 - 5I_1 + 5I_3 - V = 0$$

$$I_1 = 0$$

$$2I_2 + 5I_3 - V = -20 \quad \text{--- } ①$$

Apply KVL to mesh ④

$$-3I_2 - I_2 + I_3 - 2I_2 + 2I_1 = 0$$

$$2I_1 - 6I_2 + I_3 = 0$$

$$-6I_2 + I_3 = 0 \quad \text{--- } ②$$

Mesh ⑤

$$-I_3 + I_2 - 4I_3 + V - 5I_3 + 5I_1 = 0$$

$$I_1 = 0$$

$$I_2 - 10I_3 + V = 0 \quad \text{--- } ③$$


Solving ①, ② & ③

$$I_2 = 0.7407 \text{ A}, I_3 = 4.44 \text{ A}$$

$$V = 43.7037 \text{ V}$$

* Nodal analysis

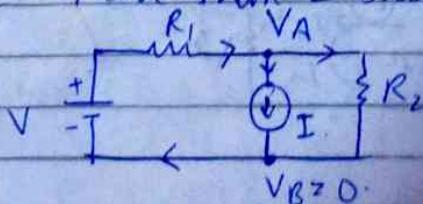
Node - More than 2 branches are connected




① Identification of nodes

② One node is a reference (V of a node is zero)

-  $\Rightarrow I_{AB} = I$

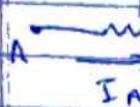-  $\Rightarrow I_{AB} = \frac{V_A - V_B}{R}$

-  $I_{BA} = \frac{V_B - V_A}{R}$

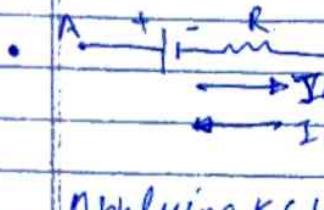-  $\Rightarrow I_{AB} = \frac{V_A - V_B - V}{R}$
 $I_{BA} = \frac{V_B - V_A + V}{R}$

Applying KCL at Node A

~~$0 = V_A - V_A + V = I + \frac{V_A - 0}{R_1} + \frac{V_A - V}{R_2}$~~


$$\frac{V}{R_1} - I = \frac{V_A + V_A}{R_2 R_1}$$

$$\frac{V}{R_1} - I = V_A \left(\frac{1}{R_2} + \frac{1}{R_1} \right)$$

$$IR_1 = 0 - V_A + V, \quad IR_2 = \frac{V_A - 0}{R_2}$$


Q Supermesh

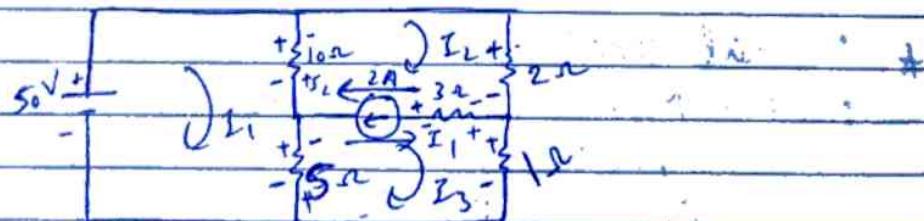By mesh analysis, find the current through 5Ω resistor in the circuit




As 3 Ω resistor is in series with current source of 2 A
 \therefore 3 Ω resistor becomes redundant

\therefore Applying KVL to current loop

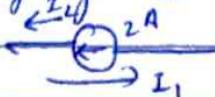

$$I_2 - I_3 = 2 \quad \text{--- (1)}$$

Applying KVL in Supermesh

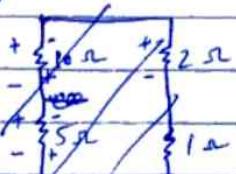

Applying KVL to loop ①.

$$\begin{aligned} 50 - 10I_1 + 10I_2 - 5I_1 + 5I_3 &= 0 \\ -15I_1 + 10I_2 + 5I_3 &= -50 \quad \text{--- (2)} \end{aligned}$$

Applying KVL to Supermesh

$$\begin{aligned} -2I_2 - I_3 - 5I_3 + 5I_1 - 10I_2 + 10I_1 &= 0 \\ 15I_1 - 12I_2 - 6I_3 &= 0 \quad \text{--- (3)} \end{aligned}$$


$$\begin{array}{c|cccc} & a & b & c & d \\ \hline 1 & 0 & 1 & -1 & 2 \\ 2 & -15 & 10 & 5 & -50 \\ 3 & 15 & -12 & -6 & 0 \end{array}$$


$$a_1x + b_1y + c_1z = d_1$$

$$I_1 = 20 \text{ A}, I_2 = 17.33 \text{ A}, I_3 = 15.33 \text{ A}$$

$$\begin{aligned} \text{Current through } 5\Omega \text{ resistor} &= I_1 - I_2 \\ &= 20 - 17.33 \text{ A} \\ &= 4.67 \text{ A} \end{aligned}$$

* Star-Delta Transformation:

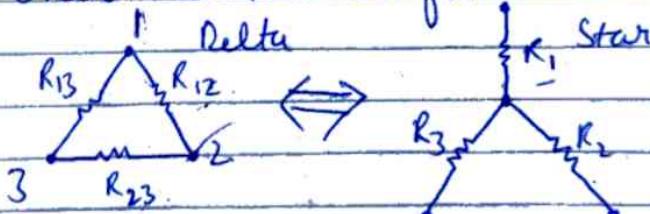

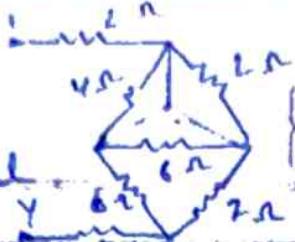

Paper No. _____
Date _____

D.S. is more useful

• Delta to Star Conversion

$$(1) R_1 = \frac{R_{12} \times R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$(2) R_2 = \frac{R_{12} \times R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$(3) R_3 = \frac{R_{23} \times R_{31}}{R_{12} + R_{23} + R_{31}}$$


• Star to Delta Conversion :-

$$(1) R_{11} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$(3) R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$

$$(2) R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

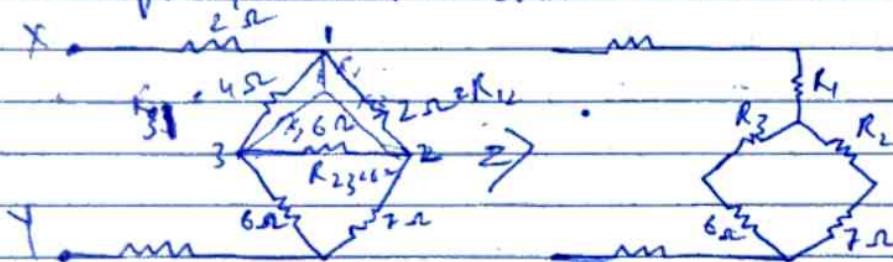
(Q) Find R_{eq} b/w terminals X and Y in the network,



Ans. Delta to Star conversion.

$$R_1 = \frac{2 \times 4}{2+4+6} = \frac{8}{12} = 0.66 \Omega$$
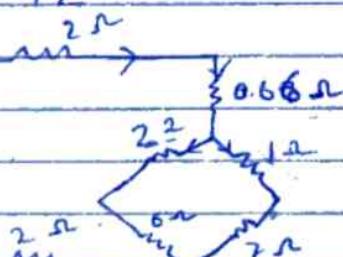
$$R_2 = \frac{2 \times 6}{12} = 1 \Omega, R_3 = \frac{4 \times 6}{12} = 2 \Omega$$



~~Q10.66~~

~~Q10.66~~ $\Rightarrow 2\Omega \text{ and } 0.66\Omega \text{ are in series}$

$$2 + 0.66 = 2.66 \Omega$$

$$2 + 6 = 8 \Omega$$

$$1 + 7 = 8 \Omega$$

$$2.66 + 8 = 10.66$$


$$8 = 10.66$$

$$R_{eq} = \frac{2.66 \times 8}{8 + 2.66 + 8} = \frac{170.14}{18.66} = 9.12$$

$$R_{eq} = \frac{8 \times 8}{8 + 8} = \frac{64}{16} = 4$$

$$R_{final} = 2 + 0.66 + 4 + 2 = 8.66$$

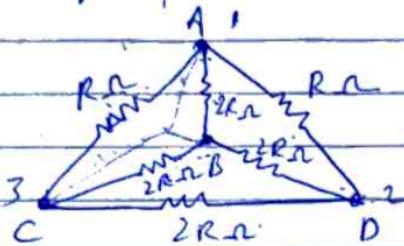(Q) Find R_{eq} b/w terminals A & B in the network



Ans Delta to Star conversion


~~$$R_1 = \frac{R \times R}{R + 2R + R} = \frac{R^2}{4R} = \frac{R}{4}, \quad R_3 = R \times 2R = \frac{R}{2}$$~~

~~$$R_2 = \frac{R \times 2R}{2R + R} = \frac{R}{3}$$~~



~~$$2R = \frac{R}{3}$$~~

(Q) Find equivalent resistance b/w terminals X and Y in the n/w shown

Ans

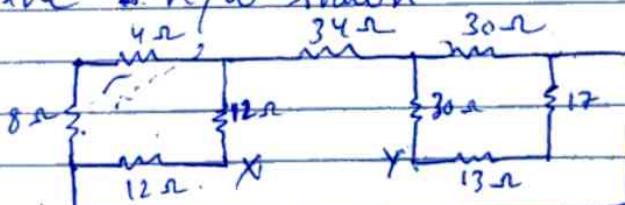
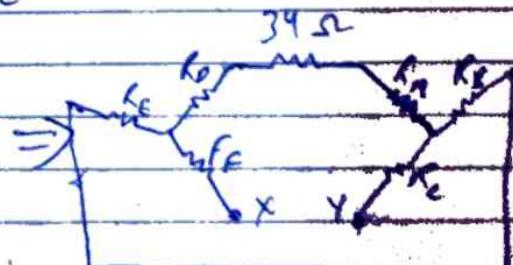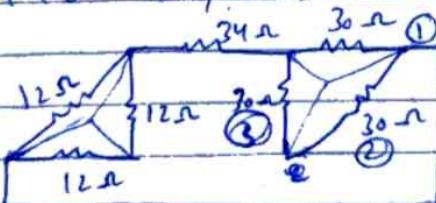
$$4 + 8 = 12 \text{ ohms}, \quad 13 + 17 = 30 \text{ ohms}$$





$$R_A = \frac{30 \times 30}{30+30} = \frac{900}{60} = 15\Omega, R_C = 10\Omega$$

$$R_B = \frac{30 \times 30}{90} = 10\Omega$$


$$R_D = \frac{12 \times 12}{12+12+12} = \frac{144}{36} = 4\Omega, R_{DFF} = R_F = 4\Omega$$

4Ω & 34Ω & 10Ω are in series

$$4 + 34 + 10 = 48\Omega$$

$$4 \times 14 \Omega$$

∴ 48Ω will short.

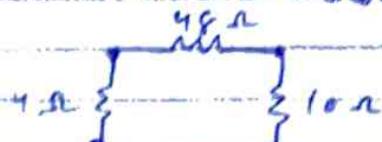

$$(48||10)\Omega \leftarrow \dots$$


$$R_{eq} = \frac{48 \times 10}{48+10} = 10.84\Omega \quad \frac{672}{62}$$

$$R_{eq} = 10.84 + 4 + 10 = 24.84\Omega$$

* Nodal analysis (KCL)^{no. of Node branches} \Rightarrow ^{no. of Equations}

$$V = IR, I = \frac{V}{R} = \frac{V_2 - V_1}{R}$$

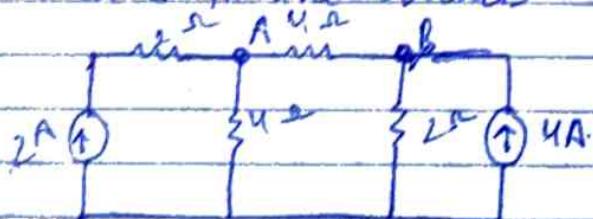Q. By Nodal analysis, determine Voltages at nodes A and B in the circuit



Agar A node ke passaa jaha tu +ve

Agar B node ke passaa jaha tu -ve

Applying KCL to node A,

$$2 = \frac{V_A}{4} + \frac{V_B - V_A}{4}$$


$$8 = 2V_A - 2V_B, 2V_A - V_B = 4$$

Apply KCL to node B

$$4 = \frac{V_B}{2} + \frac{V_C - V_A}{4}$$

$$16 = V_A + 3V_B$$

$$V_B = 8V, V_A = 8V$$

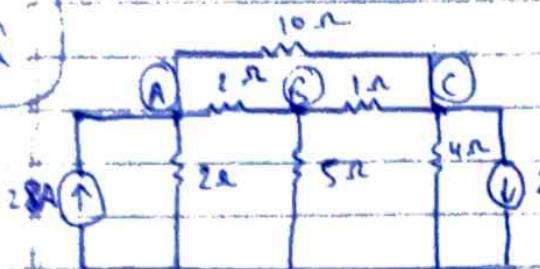

Find the currents in various resistors of circuit shown in fig.

According to KCL to node A)

$$\frac{28 - V_A}{2} + \frac{V_A - V_B}{2} + \frac{V_A - V_C}{10} = 0$$

$$1.1V_A - 0.5V_B - 0.1V_C = 28 \quad \text{--- (1)}$$

According to KCL to node B)

$$0 = \frac{V_B}{5} + \frac{V_B - V_A}{2} + \frac{V_B - V_C}{1}$$


$$-0.5V_A + 1.7V_B - V_C = 0 \quad \text{--- (2)}$$

According to KCL to node C)

$$-2 = \frac{V_C}{4} + \frac{V_C - V_B}{1} + \frac{V_C - V_A}{10}$$

$$-0.1V_A - V_B + 1.35V_C = -2 \quad \text{--- (3)}$$

(Q) Find node voltage across all nodes

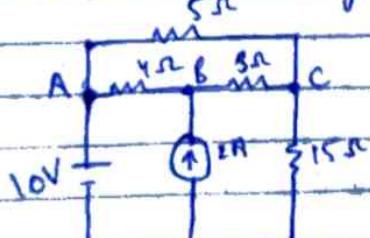

Applying KCL to node A

$$0 = \frac{V_A - V_B}{2} + \frac{V_A - V_C}{4} + \frac{V_A - V_B}{5}$$

Applying KCL to node B

$$2 = \frac{V_B - V_A}{2} + \frac{V_B - V_C}{5}$$

Applying KCL to node 3


$$0 = \frac{V_c}{15} + \frac{V_c}{3} - V_B + \frac{V_c - V_B}{5}$$

* Thévenin's Theorem

$$I = \frac{V}{R}$$

For Thévenin's circuit, $I_T = \frac{V_{TH}}{R_{TH} + R_L}$

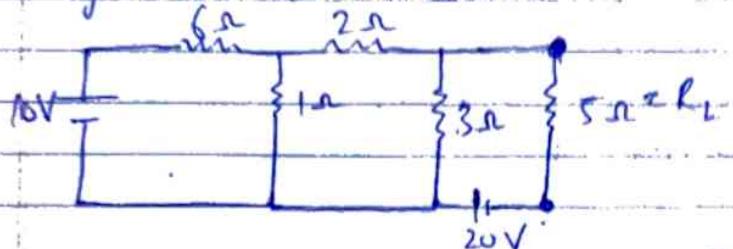
Q. Determine current through 5Ω resistor in network by Thévenin's theorem



R_L is resistance near the voltage

V_{TH} nikalne ke liye
parallel branch ke
resistance ko I se multiply
+ agar voltage dhali

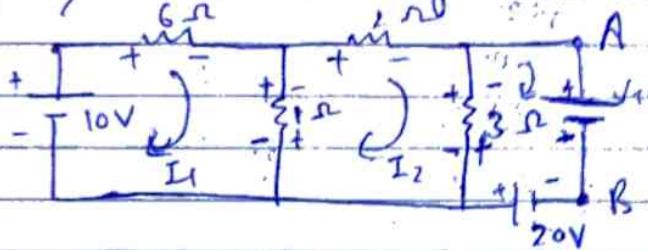Step-1) Calculation of V_{TH} : [Open circuit, $R_L = 0\Omega$]



V_{TH} ke liye

Jo voltage dhali
useke mere wale
resistance se
nikalta
nai

Applying KVL in Loop 1

$$10 - 6I_1 - I_1 + I_2 = 0 \quad 10 = 7I_1 - I_2 \quad \textcircled{1}$$

$$V_{TH} = \frac{10}{2 + 3I_2}$$

Applying KVL in Loop 2

$$-2I_2 - 3I_2 - I_2 + I_1 = 0 \quad -6I_2 = -I_1$$

V_{TH} ke liye
old but
page 111


$$10 = 4I_2 - I_2 \quad \textcircled{2}$$

$$I_2 = \frac{10}{4} = 0.25A$$

$$V_{TH} = (I_2 + 3) \times 20V \\ = (0.25 + 3) \times 20V \\ = 6.75V \\ = 6.75V$$


$$V_{TH} = V_B = 20 + 3I_2 = 20 + 3(0.25) \\ = 20.75V$$

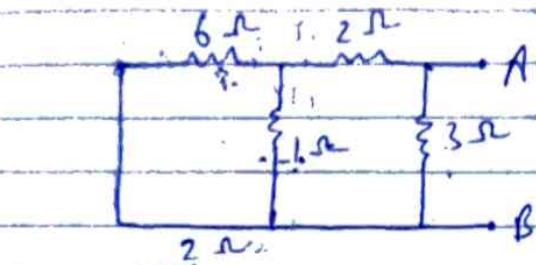Step-② Calculation for $R_{Th} = V \rightarrow$ short circuit
 $I \rightarrow$ open circuit



$$6 \parallel 1$$
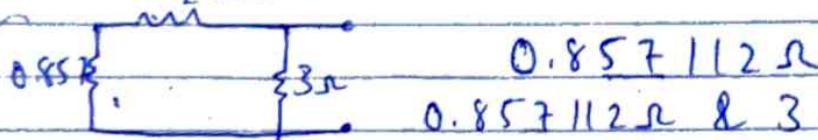
$$R_{Th} = \frac{6 \times 1}{6+1} = \frac{6}{7} = 0.857\Omega$$



0.857112Ω & 3Ω are in series


$$R_{Th} = 1.46\Omega$$

Step ③ $I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{20.73}{1.46 + 5} = \frac{20.73}{6.46}$


$$I_L = 3.21\text{ A}$$

Q Determine the current through 1.5Ω resistor in network by Thevenin theorem

Ans

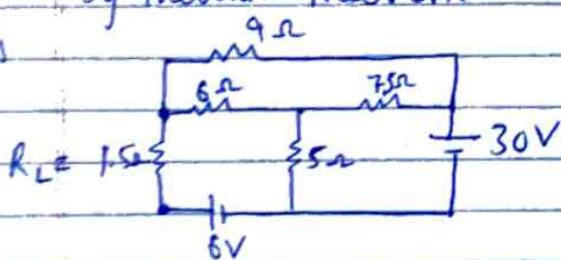

Step-1 $I_L \rightarrow$ Open circuit

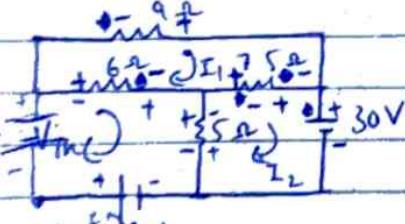

Applying KVL in Loop 1

$$7.5I_1 - 7.5I_2 + 6I_1 + 9I_1 = 0$$

$$22.5I_1 - 7.5I_2 = 0$$

$$3I_1 = I_2, I_1 = \frac{I_2}{3}$$

Loop 2

$$-7.5I_1 + 7.5I_2 - 30 + 5 = 0$$

$$-8.5I_2 + 7.5I_2 = 25 = 0$$

$$5I_2 = 25$$

$$I_2 = 5\text{ A}$$

$$10I_2 = 30$$

$$I_2 = 3, I_1 = 1\text{ A}, I_1 = \frac{5}{3} = 1.66\text{ A}$$


$$-6I_1 - 5I_2 + 6 + V_{TH} = 0$$

$$6 - 15 + 15 \Rightarrow V_{TH} = -6 + 15$$

$$V_{TH} = 15V$$

Page No.
Date

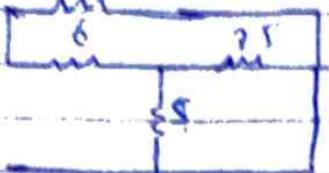Step ② $V \rightarrow$ Short circuit, Current \rightarrow Open Circuit



$$7.5 // 5 = \frac{7.5 \times 5}{7.5 + 5} = 3\Omega$$


$$6 + 3 = 9\Omega$$

$$V_{TH} = 7.5 + 6 \times 5 = 15V$$


$$9 // 9 = \frac{9 \times 9}{9 + 9} = \frac{81}{18} = 4.5V$$

Step ③ $I_1 = \frac{V_{TH}}{R_{Th} + R_L} = \frac{15}{4.5 + 7.5} = \frac{15}{12} = 2.5A$

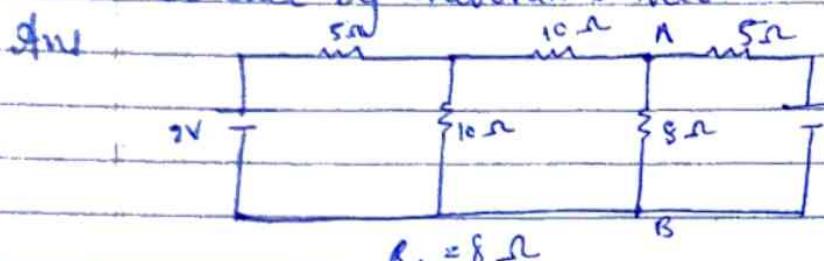Determine the current through 8Ω resistor in the circuit by Thévenin's theorem.



Step ① Open circuit R_L

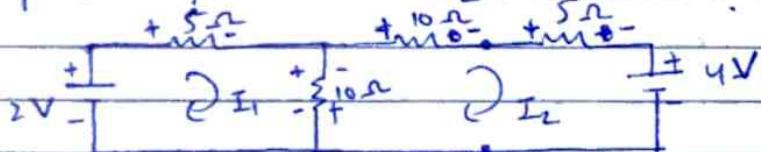

Applying KVL to Loop ①

$$2 - 5I_1 - 10I_1 + 10I_2 = 0$$

$$2 + 15I_1 - 10I_2 = 0 \quad \text{--- (1)}$$

Applying KVL to Loop ②

~~$$-4 - 10I_2 + 10I_1 + 10I_2 + 5I_1 = 0$$~~

~~$$10I_1 + 5I_2 = 4 \quad \text{--- (2)}$$~~

~~$$15I_1 - 10I_2 = 2$$~~

~~$$20I_1 + 10I_2 = 8$$~~

~~$$15I_1 - 10I_2 = 2 \times 11$$~~

~~$$10I_1 + 5I_2 = 4 \times 11$$~~

~~$$150I_1 - 100I_2 = 20$$~~

~~$$150I_1 + 75I_2 = 40$$~~

$$175I_2 = 40$$

$$I_2 = 0.228A$$

$$10V + 5(0.1) = 4$$

$$10I_1 + 4 - 10V, I_1 = \frac{3.15}{10} = 0.315$$

Applying KVL to Loop 1.

$$2 - 5I_1 - 10I_1 + 10I_2 = 0$$

$$2 + 15I_1 - 10I_2 = 0$$

Applying KVL to loop 2

$$-10I_1 + 10I_2 - 10I_2 - 5I_2 = 4$$

$$10I_1 - 25I_2 = 4 \quad \text{--- (1)}$$

$$(15I_1 - 10I_2 = 2) \times 10$$

$$(10I_1 - 25I_2 = 4) \times 15$$

$$150I_1 - 100I_2 = 20$$

$$180I_1 - 375I_2 = 60$$

$$\begin{array}{r} + \\ + \\ \hline \end{array}$$

$$275I_2 = 40$$

$$I_2 = 0.145A$$

$$V_{Th} = 4 + 5I_2 = 4 + 5(0.145) = 4 - 0.725 = 3.275V$$

Step ② Voltage \rightarrow S.C, Current \rightarrow O.C



~~5 || 10~~

$$R_{eq1} = \frac{5 \times 10}{5+10} = \frac{50}{15} = 3.33$$

~~5 || 8~~

$$R_{eq2} = \frac{5 \times 8}{5+8} = \frac{40}{13} = 3.07$$

~~5 || 10~~



$$R_A = 5 \times 10 = \frac{50}{15} = 3.33,$$

~~6 || 8~~

$$R_{eq3} = \frac{15 \times 10}{15+10} = \frac{150}{25} = 6$$

$$R_{eq} = \frac{6 \times 5}{6+5} = \frac{30}{11} =$$

Series
Left to Right

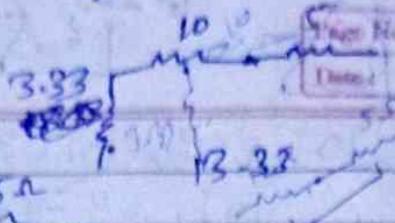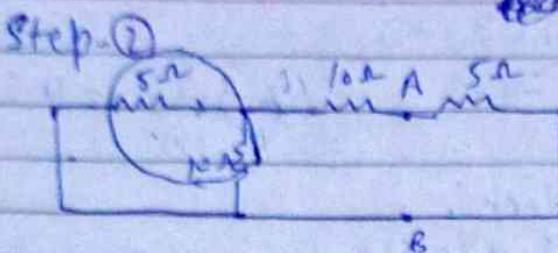


$$R_N = \frac{5 \times 10}{5+10} = \frac{50}{15} = 3.33, \quad 3.33 + 10 < 13.33$$


$$R_{Th} = \frac{13.33 \times 5}{13.33 + 5} = \frac{66.65}{18.33} = 3.63\Omega$$

$$\text{Step. ③} \quad I_L = \frac{V_{in}}{R_{Th} + R_L} = \frac{3.275}{3.63 + 8} = 0.281\text{A}$$

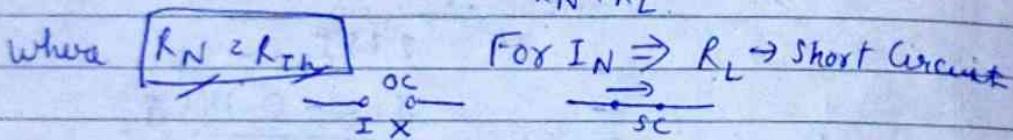
* Norton's Theorem: $I_L = I_N \frac{R_N}{R_N + R_L}$



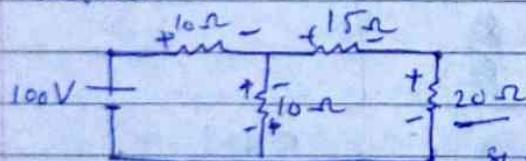Q1 By Norton's theorem, find current in $\underline{20\Omega}$ in the network.



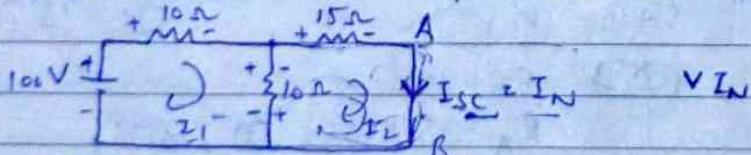Step ① $R_L = 20\Omega$ Short open circuit $\rightarrow R_L$



Applying KVL to Loop 1

$$100 - 10I_1 - 10I_1 + 10I_2 = 0$$

~~$$10I_1 + 10I_2 = 100$$~~

$$100 = 20I_1 - 10I_2 \quad 100 = 2I_1 - I_2$$

Applying KVL to Loop 2

$$-15I_2 - 10I_2 + 10I_1 = 0$$

$$10I_1 = 25I_2$$

$$I_1 = 2.5I_2 \quad I_1 = 6.25\Omega$$

$$5I_2 - I_2 = 0$$

$$I_2 = 0.25\Omega = 0.25\text{A}$$

$$I_2 \in I_N \stackrel{?}{=} S^A$$

Step ② Calculation of R_N , $V \rightarrow SC$, $I \rightarrow OC$




4002e 10.11.15

$$R_A = \frac{10 \times 10}{10 + 10} = \frac{100}{20} = 5$$


$$R_N = R_{IN} = 5 + 15 = 20 \text{ n}$$

$$\text{Step ③} \quad I_L = \frac{I_N R_N}{R_N + R_L} = \frac{2.5 \times 20}{20 + 20} = \frac{50}{40} = 1.25A$$

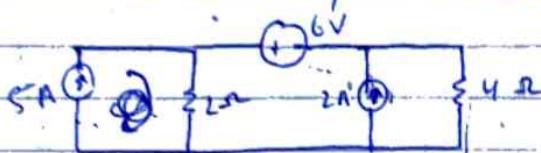Q : By Norton's theorem, Find current in $\underline{Y_R}$ in network



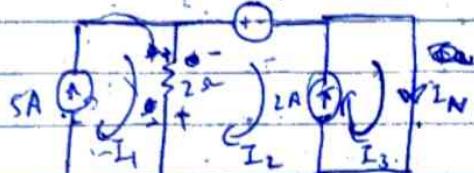Ans Step ① $R_L = 4 \Omega$ $\xrightarrow{S.C.} R_L$



$$I_2 - I_3 = 2$$

Current through mesh 1

$$I_1 = 5A$$

For 2 A source (supermesh)

$$I_3 - I_2 = 2$$

Equation for supermish

$$\cancel{-6 + 7} \cancel{z_2} = 25, 20$$

$$-6 - 2J_1 + 2I_1 < 0$$

$$I_1 - I_2 = 3$$


$$5 - 3 = I_2, I_2 = 2A$$

$$I_3 - 2 = 2, I_3 = 4 \text{ A}$$

$$I_N = 4A$$


Step ② Calculation for R_N V-SC, $I \rightarrow 0C$

$$I_N + R_{th} \cdot I_2$$

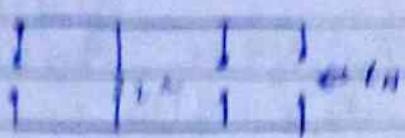


Step (5) Calculation of $I_N = \frac{I_{th} R_{th}}{R_{th} + R_L} = \frac{4 \times 2}{2 + 4} = \frac{8}{6} = 1.33A$

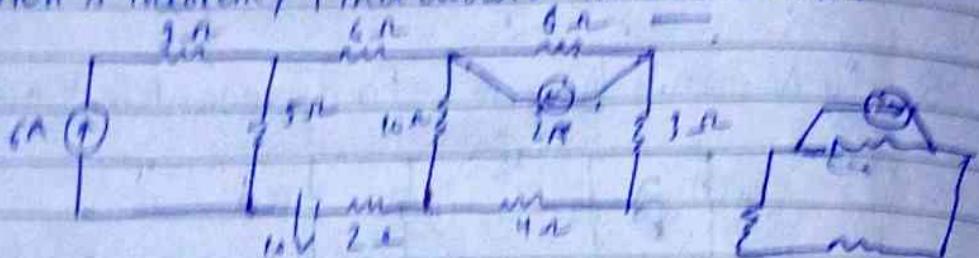
(6) By Norton's theorem, find current in 5 ohm resistor



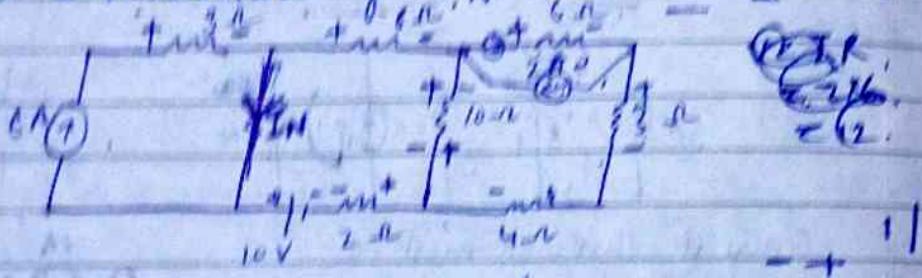Step (6) Calculation of I_N $\leftarrow R_L = 5\Omega$



$$V = IR = 2 \times 6 = 12V$$

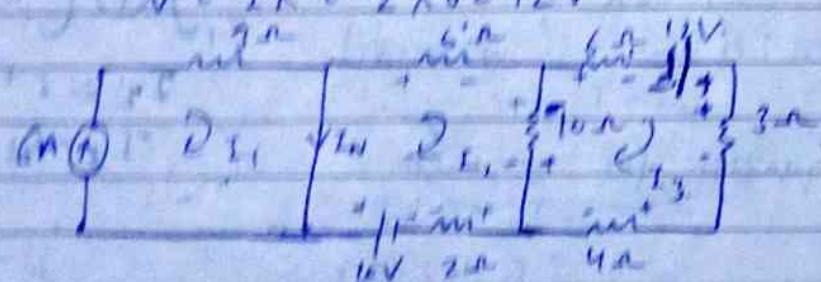

Applying KVL to Loop 2

$$-6I_3 - 10I_2 + 10I_3 - 2I_2 + 10 = 0$$

Applying KVL to loop 3

$$+18I_2 - 10I_3 = 0$$

$$-6I_3 - 12 - 3I_3 - 4I_3 - 10I_3 + 10I_2 = 0$$

$$-23I_3 + 10I_2 = 12$$

Current Division Rule

$$I_L = I_T \times \frac{R_L}{R_p + R_L}$$

$$I_L = I_T \times \frac{R_p}{R_p + R_L}$$



R_L = Load resistance
 R_p = Resistance parallel to R_L
 Opposite branch means no current
 branches are divided later back to
 R_L off distributor ka jiske
 par

* Source Transformation:

Ideal Current





Ideal Voltage

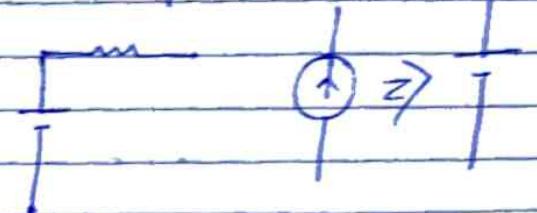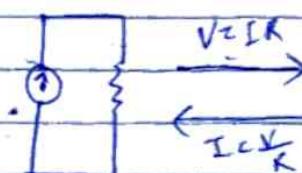


When current source is parallel with resistor, then voltage source will be in series with resistor & vice versa

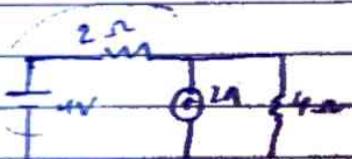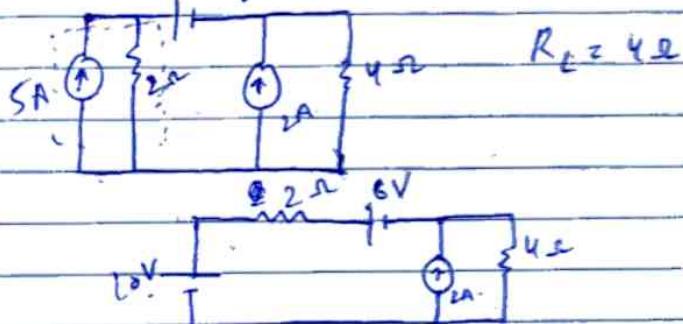Q) By Source transformation, Find current in 4Ω resistor



According to $V = IR = 5 \times 2 = 10V$

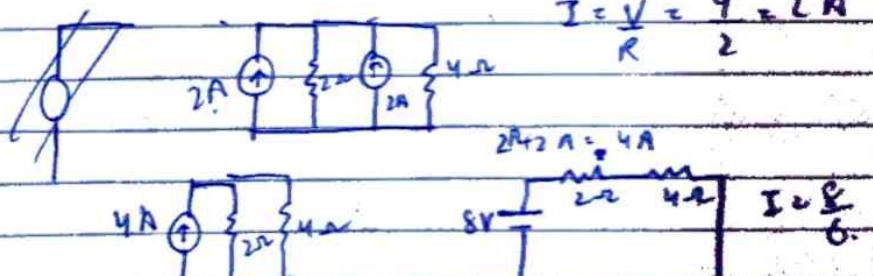

According to Current division rule

$$I_L = I_T \times \frac{R_p}{R_p + R_L} \quad R_L = \text{Load resistance}$$

$$R_p = \text{Resist. parallel to Load resistance}$$

Ohm's law, Limitations
All definitions

{ Page No.
122 }

$$I_L = I_T \times \frac{R_L}{R_P + R_L} = \frac{6 \times 0.3}{0.3 + 3} = \frac{1.8}{3.3} = 0.54$$

* Superposition theorem:- In any linear and bilateral network or circuit having multiple independent sources, the response of an element will be equal to algebraic sum of responses of that element by considering one source at a time.

Q Find current I_T for circuit shown using Superposition theorem.

Ans.

$$-20I_2 + 30I_2 + 30I_1 = 0$$

$$30I_1 = 50I_2$$

$$I_1 = 1.6I_2$$

$$I_1 = 3.2 \text{ A}$$

Step 1) Consider 50 V voltage source & S.C. 20 V

$$R_1 = \frac{20 \times 30}{20 + 30} = \frac{600}{50} = 12 \Omega$$

$$R_{eq} = 12 + 10 = 22 \Omega$$

$$I_T = \frac{50}{22} = 2.27 \text{ A}$$

$$50 - 10I_1 - 30I_2 + 30I_T = 0$$

$$50 - 10I_1 + 30I_2 = 0$$

$$4I_1 - 3I_2 = 5$$

$$I_1 = \frac{2.272 \times 20}{22 + 30} = 0.908 \text{ A}$$

Step 2) Consider 20 V voltage source

$$R_1 = \frac{10 \times 30}{10 + 30} = 7.5 \Omega$$

$$R_{eq} = 7.5 \Omega + 20 = 27.5 \Omega$$

$$I_T = \frac{20}{27.5} = 0.727 \text{ A}$$

$$6.4I_2 - 3I_1 = 5$$

$$I_2 = \frac{5}{6.4} = 0.781 \text{ A}$$

$$2.27 = \frac{50}{22} = 2.27 \text{ A}$$


$$I_{\frac{1}{4}} = I_T \times \frac{R_P}{R_P + R_i} = \frac{0.727 \times 10}{10 + 30} = \frac{7.27}{40} = 0.1825 \text{ A}$$

If resistor is connected with
if a short circuit is connected across resistor then it becomes
redundant



$$\text{Total } I \text{ through } 5\Omega = I_1 + I_2 = 0.708 + 0.181A \\ = 1.089$$

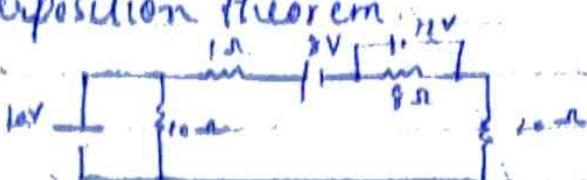(d)
iii

Determine the current in 2Ω resistor in network by superposition theorem.



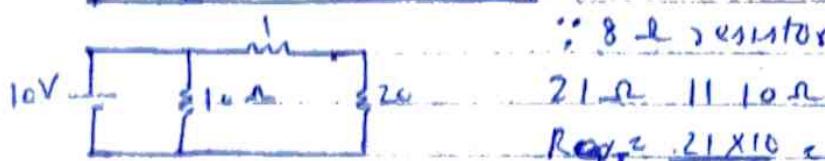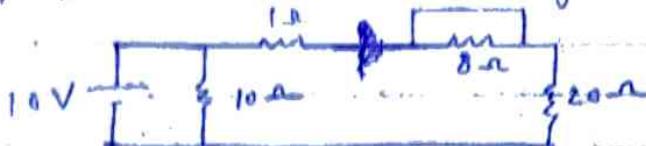Step (1). Consider 10V voltage only & short circuit other



$$R_{eq} = \frac{21 \times 10}{21 + 10} = 6.774\Omega$$


iv

$$I = \frac{V_i}{R_e} = \frac{10}{6.77} = 1.49A$$


Step (2)

(d)

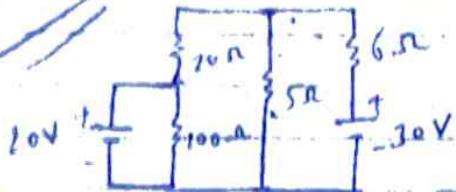~~Find~~ Find current through ~~5Ω~~ resistance by superposition.




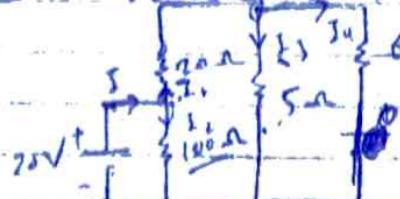Step (1) Considering 30V as single source:



$$R_f = \frac{6 \times 5}{6 + 5} = \frac{30}{11} = 2.72\Omega$$
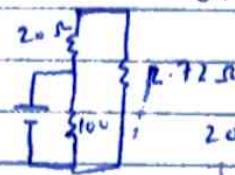
$$R_T = \frac{100 \times 2.72}{100 + 2.72} = 18.51\Omega$$



$$20 + 2.72 = 22.72\Omega$$




$$I_T = \frac{20}{10+20} = 1.08A$$

$$I_{R_1} = \frac{I_T \times R_p}{R_p + R_L} = \frac{1.08 \times 100}{100 + 20}$$

$$I_{R_1} = 0.88A$$

$$I_3 = \frac{0.88 \times 6}{5+6} = 0.48A$$

Step 6) Consider 30V voltage source

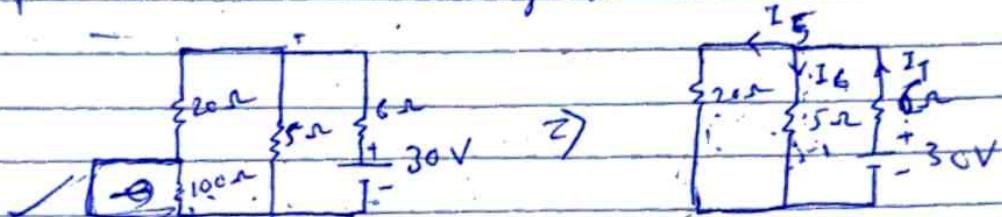

$$R_{eq} = \frac{V_T}{I_{in}} = \frac{30}{20+5+6} = 19.35\Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{30}{19.35} = 1.53A$$

$$I_{R_1} = \frac{I_T \times R_p}{R_p + R_L} = \frac{1.53 \times 20}{30+20} = 0.612$$

$$R_1 = \frac{20 \times 5}{20+5} = 4 \Rightarrow R_T = 4+6=10\Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{30}{10} = 3A$$

$$I_6 = I_T \times \frac{R_p}{R_p + R_L} = 3 \times \frac{20}{20+5} = \frac{60}{25} = 2.4A$$

$$\text{Total current through } 5\Omega = I_3 + I_6 = 0.48 + 2.4 = 2.88A$$

- * Max Power Transfer theorem: All steps same as theorem, only condition are diff. According to this, the condition for max power flow through load resistor R_L can be achieved when load resistor equals thevenin equivalent resistance of the circuit.


$$P = I_L^2 R_L \quad \text{--- (1)}$$

$$P = \frac{(V_{Th})^2}{R_{Th} + R_L} R_L \quad \text{---}$$


$R_L = R_{Th}$ This is required condition for max Power flow

$$P_{\max} = \frac{V_{Th}^2}{4R_{Th}}$$

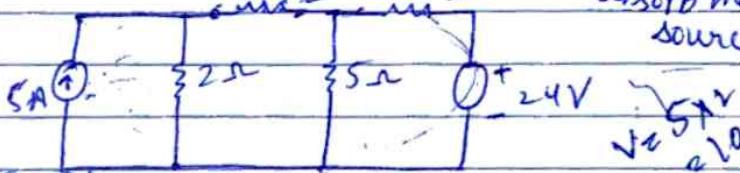Q In given network find the value of R_L which will absorb more power from source. Find P_{\max}



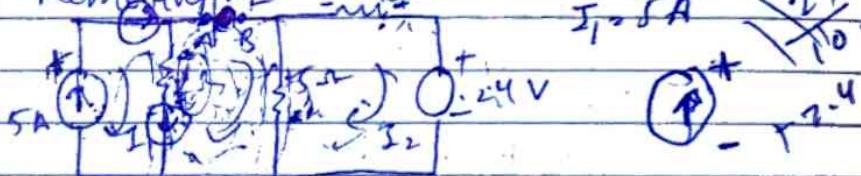Ans. step ① Removing R_L ~~in parallel~~ $I_1 = 5A$ ~~$\frac{24}{10}$~~



$$I_1 = 5A$$


$$3.33$$

Applying KV in mesh 2


$$-24 + 5I_2 + 10I_2 = 0$$

$$15I_2 = 24$$

$$I_2 = \frac{24}{15} = 1.6A$$

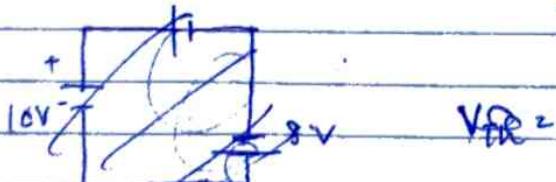

$$V_{Th} =$$

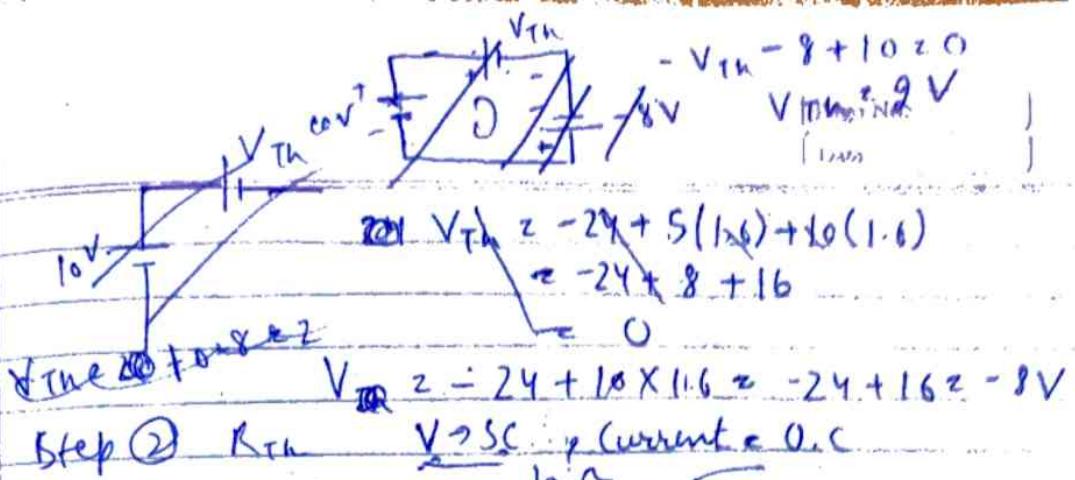


$$201 \quad V_{TH} = 2 - 24 + 5(1.6) + 10(1.6)$$

$$= -24 + 8 + 16$$

$$= 0$$

$$\text{At node } 201 \quad V_{TH} = 2 - 24 + 10 \times 1.6 = -24 + 16 = -8V$$

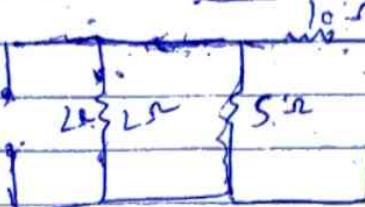Step ② R_{TH} $\underline{V_{TH}}$ (current = 0.0)



$$202 \quad R_{TH} = 2 + 5 = 7\Omega$$

$$10V \parallel 5\Omega, R_1 = \frac{10 \times 5}{2+5} = \frac{50}{7} = 7.14\Omega$$


$$7.14 + 2\Omega = 9.14\Omega$$

$$R_L = R_{TH} = 5.33\Omega$$


$$P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{4}{2 \times 7} = \frac{4}{14} = 0.187$$

- Q. Find the value of resistance R_L for max Power transfer
Also calculate Maximum Power

Ans

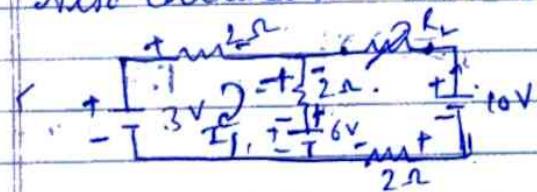

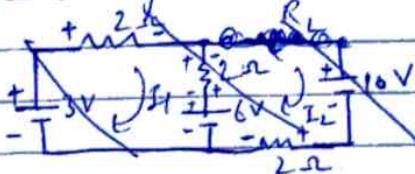Removing R_L $\rightarrow R_L$ For V_{TH}



Apply KVL to Loop 1

$$3 - 2I_1 - 2I_2 + 2I_2 - 6 = 0$$

$$2I_2 - 4I_1 = 3 \quad \text{---} ①$$

Apply KVL to Loop 2

$$-2I_2 + 2I_1 - 10 - 2I_2 + 6 = 0$$

$$2I_1 - 4I_2 = 4$$

$$2I_2 - 8 - 8I_2 = 3$$

$$-6I_2 = 11$$

$$I_2 = -1.83A$$

$$I_1 - 2I_2 = 2 - \text{---} ②$$


$$I_1 = 2 + 2I_2$$

V_{Th}

$$V_m = -10 - 2I_1 - 2I_2 = \cancel{-10} + 6$$

$$V_{Th} = -10 + 2I_2 + 6 = 2I_2 +$$
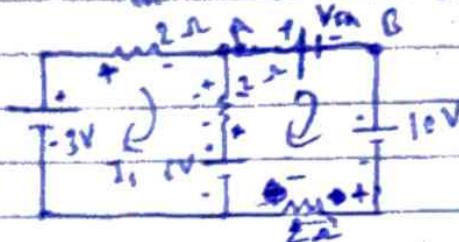
$$V_m = -10 - 2I_2 = -10 - (2x - 1.93) = -6.34$$



Applying KVL to loop 1

$$3 - 2I_1 - 2I_2 - 6 = 0$$

$$4I_2 = -3$$

$$I_2 = -\frac{3}{4} = -0.75A$$


V_{Th}

$$-V_{Th} - 10 = 10V + 2I_1 = 0 \quad V_{Th} = -10 - 2I_1 + 6 = 2I_1$$

$$V_{Th} = 2I_1 - 10 = -1.5 - 10$$

$$= -11.5V + 6.$$

$$= -5.5V$$

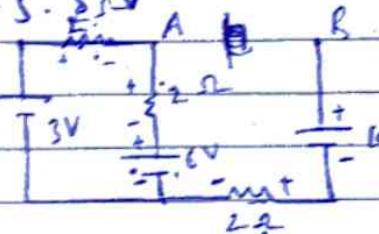

$$V_{Th} = -10 - 2I_1 + 6 - 2I_2$$

$$= -10 - 2(0.75) + 6 - (-0.75)$$


$$= -10 + 1.5 + 6 + 0.5 = -4 - 1.5 = -5.5V$$

$$R_L = R_{Th} = 3\Omega$$


$$\frac{282}{2+2} = \frac{4}{4} = 1 \quad P_{max} = \frac{V_m^2}{4R_{Th}} = \frac{2.52W}{1.4\Omega} = 1.8W$$

Q. For given circuit find the value of R_L so that max power is dissipated in it. Also find P_{max}

Ans

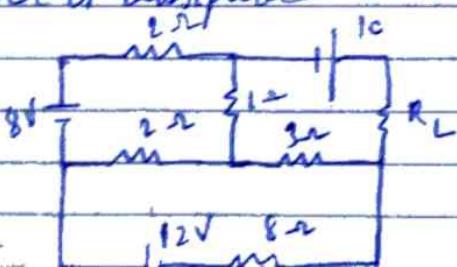

Removing R_L & open circuit for V_{Th}

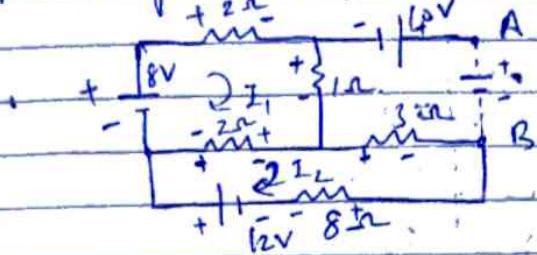

Applying KVL in mesh 1

$$8 - 2I_1 - 10I_1 - 2I_1 + 2I_2 = 0$$

$$5I_1 - 2I_2 = 8 \quad \times 2$$

Applying KVL in mesh 2

$$2I_1 - 2I_2 - 3I_2 - 8I_2 + 12 = 0$$

$$-13I_2 + 2I_1 = -12 \quad \times 5$$

$$10I_1 - 4I_2 = 16$$

$$10I_1 - 65I_2 = -60$$

$$- \quad + \quad +$$

$$61I_2 = 76, \quad I_2 = 1.24A$$

$$5I_1 = 2.48 \quad \times 8$$

$$I_1 = \frac{10.48}{5} = 2.096A$$

For V_{Th} , $-V_{Th} + 3I_2 + I_1 + 10 = 0$

$$V_{Th} = 10 + 2.096 + 3.72 = 15.816$$

$$\left\{ \begin{array}{l} I_{max} \\ I_{min} \end{array} \right.$$

Main Power Transfer Theorem

* Time-Domain Analysis of RL & LC

$R \rightarrow$ Energy dissipated

L & $C \rightarrow$ Energy stored

- Circuit having one energy storage element is called first order (RL , RC)
- Circuit having 2 energy storage elements - second order.

Charging At $t = 0$.

of Capacitor $V(t) = Ae^{-pt}$, $\Omega = 0$, $V = 0$, $p = \frac{1}{RC}$


$$V_c(t) = Ae^{-t/RC}$$

At $t = \infty$, $C_l = \text{max}$, $I = 0$.

$$V_c = Ae^{-t/RC} + V \quad (\text{time constant})$$

$$V_c = -Ve^{-t/RC} + V$$

$$V_c(t) = V(1 - e^{-t/RC})$$

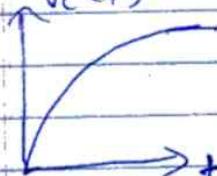


$t = t_f = 5RC = 0.99V$ (Capacitor is fully charged)


Time constant of RC is defined as time in which it charges upto 63% of its final value

Discharging At $t = 0$

Of Capacitor. $V_c(t) = V_0 e^{-t/RC}$

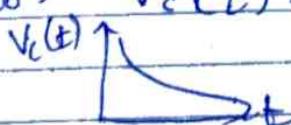

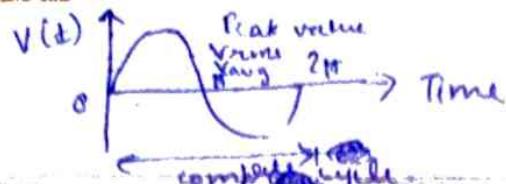Time constant of RC circuit is defined as time required to discharge the capacitor by 36% of its initial value



Page No.

Date

DC :- Current which remains constant in magnitude wrt time.

AC :- Current which changes periodically wrt time in both magnitude & direction.

Instantaneous Value :- Value of alternating quantity at a particular instant.

Amplitude :- Max. Value attained by an alternating quantity during +ve or -ve half cycle.

Cycle :- Each repetition of a set of +ve and -ve instantaneous values of alternating quantity is called a cycle.

Time period = Time taken by alternating quantity (AO) to complete 1 cycle.

Frequency = No of cycles completed by AO per sec
 $f = \frac{1}{T}$

$$A = A_0 \sin \omega t$$

AQ(2)

RMS :- The square root of mean of squares of instantaneous values gives RMS value

$$I_{rms} = I_0 = \frac{0.707}{\sqrt{2}} I_0, V_{rms} = 0.707 V$$

Average value :- Avg of all instantaneous values of an alternating voltage and currents over complete cycle gives avg value

$$I_{avg} = \frac{2I_0}{\pi} = 0.637 I_0$$

$$I_{\text{rms}} = \sqrt{\frac{1}{T_2 - T_1} \int_{T_1}^{T_2} i^2 dt}$$


$$I_{\text{avg}} = \frac{1}{T_2 - T_1} \int_{T_1}^{T_2} i dt$$

{ Major Min
Minor }

Peak Value :- Max value reached by A.D. in 1 cycle

$$V_{\text{peak}} = \sqrt{2} V_{\text{rms}}$$

Q) $I(t)$

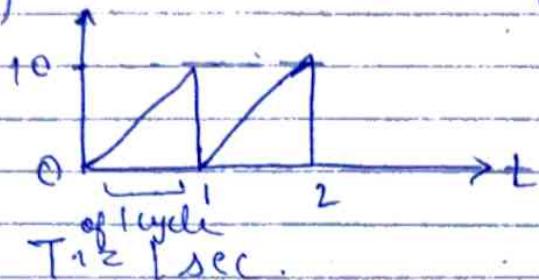

Find I_{avg} , I_{rms}

$$\frac{y_2 - y_1}{x_2 - x_1} = \frac{y_1 - y}{x_1 - x}$$

$$\frac{10 - 0}{1 - 0} = \frac{0 - y}{-t}$$

$$\Rightarrow i(t) = 10t \quad 0 < t < 1$$

$$I_{\text{avg}} = \frac{1}{T} \int_0^T i dt$$


$$I_{\text{avg}} = \frac{10}{2} \times 1 = 5 \text{ A}$$

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T (10t)^2 dt}$$

$$= \sqrt{\frac{100}{3}} = 5.77 \text{ A.}$$

Q)

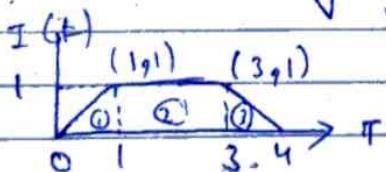

I_{avg} & I_{rms} .

~~$I_{\text{avg}} = \frac{1}{T} \int_0^T i dt$, Time = 4 sec~~

$$\frac{1}{4} = \frac{-I(t)}{-t}, \quad I(t) = T \quad \text{for } 0 < t < 3$$

$$I(t) = 1 \quad \text{for } 0 < t < 3$$

(3,1)

Page No.
Date

(H,D)

$$x(t) = 4 - t \quad \text{for } 3 \leq t \leq 4$$

$$I_{avg} = \frac{1}{T} \int_0^T i(t) dt$$

$$= \frac{1}{4} \left[\int_0^1 t dt + \int_1^3 1 dt + \int_3^4 4-t dt \right]$$

$$= 0.75 A$$

$$I_{rms} = \sqrt{\frac{1}{T} \left[\int_0^1 t^2 dt + \int_1^3 1^2 dt + \int_3^4 (4-t)^2 dt \right]}$$

$$= 0.66 A.$$

* Power :- Rate of doing work / Work per unit time
 $P = VI$ SI unit = W (J/S)

$$P = \frac{dW}{dt}$$

* Energy :- Ability to do work

$$E = \frac{1}{2} m V^2 \quad \text{Joules}$$

* KCL - Acc to KCL, total current entering the junction is equal to total current leaving junction

* KVL - Algebraic sum of all voltages in a loop must be equal zero.

* Thevenin's theorem - Any 2 terminal linear & bilateral network or circuit having multiple sources can be represented in a simplified equivalent circuit consisting of V_{Th} in ~~across~~ series with R_{Th} .

Step ① Remove R_L and Calculate V_{Th}

Step ② Calculation of $R_{Th} \Rightarrow V \rightarrow \text{Short}, I = 0$

$$I_L = \frac{V_{Th}}{R_m + R_L}$$

Thevenin :- Any linear circuit can be simplified into equivalent circuit consisting of voltage source and series resistance connected to load.

- * Norton :- Any linear circuit can be simplified to an equivalent circuit consisting of single current source and parallel resistance connected to a load.


Step ① Short R_L (Plain wire) Find I_N

I_N = Current through shorted R_L

Step ② Calculation of R_N/R_{Th} :- $V \rightarrow SC, I = 0C$


$$\text{Step ③ } I_L = \frac{I_N R_N}{R_N + R_L}$$
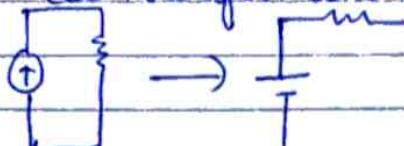
$$\star I_L = I_T \times \frac{R_p}{R_p + R_L} \quad \text{Source transformation}$$



* Superposition theorem :- In any linear and bilateral network or circuit having multiple independent sources, the response of an element will be equal to algebraic sum of responses of that element by considering one source at a time.

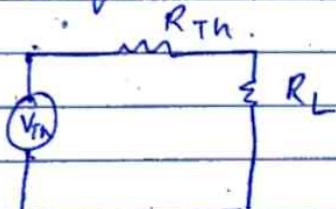* Max Power Transfer :- Explains that to generate max external power through a finite resistance, R_L must be equal to R_{Th} .



$$I = \frac{\sqrt{V_{th}}}{R_{th} + R_L}$$

$$\text{We know, } P = I^2 R_L$$

$$P = \frac{\sqrt{V_{th}}^2 R_L}{(R_{th} + R_L)^2}$$

Differentiating w.r.t R_L

$$\frac{df}{dR_L} = V_{Th}^2 \left(\frac{1 \times (R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L)}{(R_{Th} + R_L)^4} \right)$$

$$= V_{Th}^2 \left(\frac{R_{Th}^2 + 2R_{Th}R_L + 2R_L^2 - 2R_L R_{Th} - 2R_L^2}{(R_{Th} + R_L)^4} \right)$$

$$= V_{Th}^2 \frac{(R_{Th}^2 - R_L^2)}{(R_{Th} + R_L)^4}$$


Putting $\frac{dP}{dR_L} = 0$.

$$(R_{Th}^2 - R_L^2) V_{Th}^2 = 0$$

$$R_{Th} = R_L$$

$$P = \frac{V_{Th}^2 R_L}{(2R_L)^2} = \frac{V_{Th}^2}{4R_L}$$

* Delta to Star

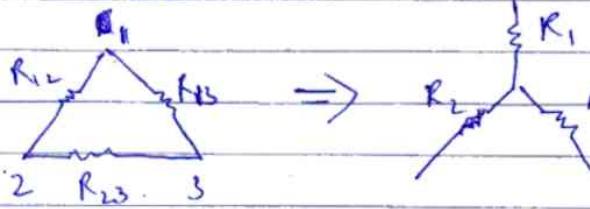

③ - ① \Rightarrow Result - ④

Result + ② \Rightarrow ⑤

⑤ \times ⑥ + ⑥ \times ④ \Rightarrow ⑦

For branch R_{23}

$$(R_{12} + R_{13}) \parallel R_{23}$$

$$R_{23} = \frac{(R_{12} + R_{13}) R_{23}}{R_{12} + R_{23} + R_{31}} \quad - \textcircled{1}$$

$$R_{23} = R_2 + R_3$$

Similarly; for R_{13}

$$(R_{12} + R_{23}) \parallel R_{13}$$

$$R_{13} = \frac{(R_{12} + R_{23}) R_{13}}{R_{12} + R_{23} + R_{31}} \quad - \textcircled{2}$$

$$R_{13} = R_1 + R_3$$

For R_{12}

$$R_{12} = \frac{(R_{13} + R_{23}) R_{12}}{R_{12} + R_{23} + R_{31}} \quad - \textcircled{3}$$

$$R_{12} = R_1 + R_2$$

Now, subtracting $\textcircled{1}$ from $\textcircled{3}$

$$\begin{aligned}
 R_1 + R_2 - R_2 - R_3 &= \frac{(R_{13} + R_{23})R_{12} - R_{23}(R_{12} + R_{13})}{R_{12} + R_{13} + R_{31}} \\
 &\equiv \frac{R_{13}R_{12} + R_{23}R_{12} - R_{12}R_{23} - R_{13}R_{23}}{R_{12} + R_{23} + R_{31}} \\
 R_1 - R_3 &\equiv \frac{R_{13}(R_{12} - R_{23})}{R_{12} + R_{23} + R_{31}} - (4)
 \end{aligned}$$

Add (2) + (4)

$$\begin{aligned}
 R_1 + R_3 + R_1 - R_3 &\equiv \frac{R_{13}R_{12} - R_{13}R_{23} + R_{13}R_{12} + R_{13}R_{23}}{R_{12} + R_{23} + R_{31}} \\
 2R_1 &\equiv \frac{2R_{13}R_{12}}{R_{12} + R_{23} + R_{31}} - (5)
 \end{aligned}$$

Similarly :- $R_2 = \frac{R_{12}R_{23}}{R_{12} + R_{23} + R_{31}} - (6)$, $R_3 = \frac{R_{13}R_{23}}{R_{12} + R_{23} + R_{31}} - (7)$

Star \rightarrow Delta

Multiply (5) \times (6), (6) \times (7), (7) \times (8)

$$R_1R_2 = \frac{R_{12}^2 R_{13}R_{23}}{(R_{12} + R_{23} + R_{31})^2} - (8), R_2R_3 = \frac{R_{23}^2 R_{12}R_{13}}{(R_{12} + R_{23} + R_{31})^2} - (9)$$

$$R_3R_1 = \frac{R_{13}^2 R_{12}R_{23}}{(R_{12} + R_{23} + R_{31})^2} - (10)$$

Add (8), (9), (10)

$$\begin{aligned}
 R_1R_2 + R_2R_3 + R_3R_1 &= \frac{R_{12}^2 R_{13}R_{23} + R_{23}^2 R_{12}R_{13} + R_{13}^2 R_{12}R_{23}}{(R_{12} + R_{23} + R_{31})^2} \\
 &\equiv \frac{R_{12}R_{23}R_{13}(R_{12} + R_{23} + R_{31})}{(R_{12} + R_{23} + R_{31})^2}
 \end{aligned}$$

$$R_1R_2 + R_2R_3 + R_3R_1 = \frac{R_{12}R_{23}R_{13}}{(R_{12} + R_{23} + R_{31})}$$

$$R_{12} = \frac{R_1R_2}{R_3} + R_2 + R_1, R_{23} = \frac{R_2R_3 + R_2 + R_3}{R_1}$$

$$R_{31} = R_3 + R_1 + \frac{R_3R_1}{R_1}$$

Unit - 2

* AC Circuits

Current

DC

↓

R/Voltage

A.C

↓

P/L/C

F

* Average Value

Avg Value = Area of half cycle

Base length of half cycle

$$I_{avg} = \frac{1}{\pi} \int_0^{\pi} I_0 \sin \theta d\theta \quad I = I_0 \sin \theta$$

$$= \frac{1}{\pi} \int_0^{\pi} I_0 \sin \theta d\theta$$

$$= \frac{I_0 [-\cos \theta]}{\pi} \Big|_0^{\pi} = \frac{I_0 [1+1]}{\pi} = \frac{2I_0}{\pi} = 0.637 I_0$$

$$I_{avg} = \frac{2I_0}{\pi} = 0.637 I_0$$

* RMS value (Root Mean Square)

$$I_{RMS} = \sqrt{\frac{1}{\pi} \int_0^{\pi} I^2 d\theta} = \sqrt{\frac{I_0^2}{\pi} \int_0^{\pi} \sin^2 \theta d\theta}$$

$$= \sqrt{\frac{I_0^2}{\pi} \int_0^{\pi} (1 - \cos 2\theta) d\theta} \quad \cos 2\theta = 1 - 2 \sin^2 \theta$$


$$= \sqrt{\frac{I_0^2}{2\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^{\pi}} = \sqrt{\frac{I_0^2 \pi}{4}}$$

$$= \frac{I_0 \sqrt{\pi}}{2}$$

$$I_{RMS} = \frac{I_0}{\sqrt{2}} = 0.707 I_0$$

Q1 - Find the avg value of waveform

$$V \uparrow 20V$$

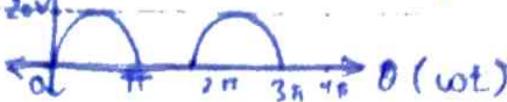

$$\begin{aligned} V &= V_0 \sin \theta \\ &= 20 \sin \theta \end{aligned}$$

Ans - Given waveform is continuous

Equation	Interval
$V = 20 \sin \theta$	$0 < \theta < \pi$
$V = 0$	$\pi < \theta < 2\pi$
(2)	

~~Ans~~


$$V_{avg} = \frac{\text{Area of full cycle}}{\text{Base length of full cycle}}$$

$$= \frac{1}{2\pi} \int_0^{\pi} 20 \sin \theta d\theta + \int_{\pi}^{2\pi} 0 d\theta$$

$$= \frac{20}{2\pi} [-\cos \theta]_0^\pi$$

$$= \frac{10}{\pi} [2] = \frac{20}{\pi} = 6.3666V$$

Q2 Find the avg value of the waveform

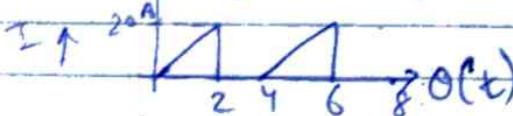

Ans - Given waveform is continuous

Equation	Interval
$I = 20 \sin \theta$	$0 < \theta < \pi$
$I = 0$	$\pi < \theta < 2\pi$

$$I_{avg} = \frac{1}{4} \int_0^{\pi} I d\theta = \frac{1}{4} \left[\int_0^{\pi} 20 \sin \theta d\theta + \int_{\pi}^{2\pi} 0 d\theta \right]$$

$$= \int_0^2 [1 - \cos \theta]^2$$

Given waveform is continuous.

Area of trapezoid

Equation	Interval
① $I = 10t$	$0 < t < 2$
② $I = 0$	$2 < t < 4$

$$\frac{1}{2} \times 2 \times 10$$


$$I_{avg} = \frac{1}{4} \int_0^4 I dt$$

$$m(\text{slope}) = \frac{y_2 - y_1}{x_2 - x_1} = \frac{10 - 0}{2 - 0}$$

$$= \frac{1}{4} \left[\int_0^2 10t dt + \int_2^4 0 dt \right]$$

$$= \frac{10}{4} \left[\frac{t^2}{2} \right]_0^2$$

$$= \frac{10}{8} \times 4 = 5A$$

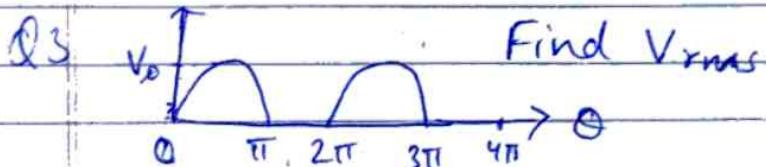

Ans Given waveform is continuous.

$$\textcircled{1} \quad V = V_0 \sin \theta \quad 0 < \theta < \pi$$

$$\textcircled{2} \quad V = 0 \quad \pi < \theta < 2\pi$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V^2 d\theta}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^\pi [V_0 \sin \theta]^2 d\theta}$$

$$= \sqrt{\frac{V_0^2}{2\pi} \int_0^\pi (\cos \theta)^2 d\theta}$$


$$= \sqrt{\frac{V_0^2}{2\pi} \cdot \frac{\pi}{2}}$$

$$= \frac{V_0^2}{4\pi} \int_0^\pi (1 - \cos 2\theta) d\theta$$

$$= \frac{V_0^2}{4\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^\pi$$

$$V_{rms} = \frac{V_0^2}{4\pi} \times \pi = \frac{V_0^2}{4}$$

$$V_{rms} = \frac{V_0}{2} = 0.5V_0$$

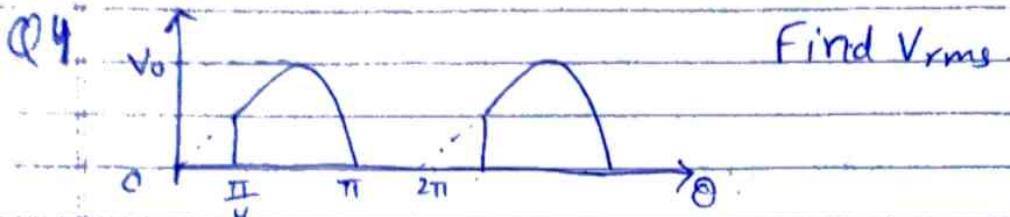

Ans.

Equation
① $V = 0$

Interval
 $0 < \theta < \frac{\pi}{4}$

② $V = V_0 \sin \theta$

$\frac{\pi}{4} < \theta < \pi$

③ $V = 0$

$\pi < \theta < 2\pi$

$$V_{rms}^2 = \frac{\int_0^{\pi/4} V^2 d\theta + \int_{\pi/4}^{\pi} V^2 \sin^2 \theta d\theta + \int_{\pi}^{2\pi} V^2 d\theta}{2\pi}$$

$$= \frac{V_0^2}{2\pi} \int_0^{\pi/4} (1 - \cos 2\theta) d\theta$$

$$= \frac{V_0^2}{4} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^{\pi/4}$$

$$= \frac{V_0^2}{4} \left[\frac{\pi}{2} - \frac{\sin \pi}{2} - \frac{\pi}{4} + \frac{\sin \pi}{2} \right]$$

$$= \frac{V_0^2}{4} \left[\frac{3\pi}{4} + \frac{1}{2} \right]$$

$$V_{rms}^2 = V_0^2 (0.227)$$

$$V_{rms} = V_0 (0.476)$$

* Some Important formulas.

① $\omega = 2\pi f = \frac{2\pi}{T}$, ② $I_{rms} = \frac{I_0}{\sqrt{2}}$, $V_{rms} = \frac{V_0}{\sqrt{2}}$

(3) $I_{avg} = 0.637 I_0$

(4) Form factor $= \frac{I_{rms}}{I_{avg}}$

- Q5. The equation of an A.C is $I = 62.35 \sin 323t$. Determine
(1) max value (2) frequency (3) RMS value (4) Avg Value
(5) Form factor

Ans) $I = 62.35 \sin 323t$ Amperes

Comparing with $I = I_0 \sin \omega t$

$$I_0 = 62.35 \text{ A}, \omega = 323$$

$$\omega = 2\pi f, f = \frac{323}{2\pi} = 51.403 \text{ Hz}$$

$$I_{rms} = \frac{I_0}{\sqrt{2}} = \frac{62.35}{\sqrt{2}} = 44.08 \text{ A}$$

$$I_{avg} = 0.637 \times 62.35 = 39.71 \text{ A}$$

$$\text{Form factor} = \frac{I_{rms}}{I_{avg}} = \frac{44.08}{39.71} = 1.11$$

* Phasor Algebra

(1) Length of phasor: $V = \frac{V_0}{\sqrt{2}}$

(2) Rectangular form / Cartesian form: $x + iy = x + jy$

(3) Polar form: $r \angle \theta = r(\cos \theta + i \sin \theta)$

* Rectangular form

$$z_1 = x_1 + jy_1, z_2 = x_2 + jy_2$$

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2) \quad (\text{Addition})$$

$$z_1 - z_2 = (x_1 + jy_1) - (x_2 + jy_2)$$

$$= (x_1 - x_2) + j(y_1 - y_2) \quad (\text{Subtraction})$$

* Polar form

$$z_1 = r_1 \angle \theta_1, \quad z_2 = r_2 \angle \theta_2$$

$$(z_1, z_2) = (r_1 \angle \theta_1) \cdot (r_2 \angle \theta_2)$$

$$= (r_1, r_2) \angle (\theta_1 + \theta_2)$$

$$\frac{z_1}{z_2} = \frac{r_1 \angle \theta_1}{r_2 \angle \theta_2} = \frac{r_1}{r_2} \angle (\theta_1 - \theta_2) \dots \text{(Division)}$$

Mult (Multi)

Q6(1) $V_1 = 42.43 \angle 0^\circ, V_2 = 28.28 \angle 60^\circ$

Calculate $V_1 + V_2$ in polar form

Ans) $V_1 + V_2 = (42.43 \angle 0^\circ) + (28.28 \angle 60^\circ)$

$= \text{Rec}(42.43, 0) + \text{Rec}(28.28, 60) \rightarrow$ In calcii

$$= [42.43 + 0 \hat{j}] + (14.14 + 24.49 \hat{j})$$

$$= 56.57 + 24.49 \hat{j}$$

$$V_1 + V_2 = \text{Pol}(56.57, 24.49) \rightarrow \text{In calcii}$$

$$= 61.64 \angle 23.41 \rightarrow \text{Polar Form}$$

Q7 Find the resultant of the following voltages

$$V_1 = 25 \sin \omega t, V_2 = 40 \sin(\omega t + \frac{\pi}{6}), V_3 = 30 \cos \omega t$$

$$V_4 = 20 \sin(\omega t - \frac{\pi}{4})$$

Imp

Ans) $V_3 = 30 \cos \omega t = 30 \sin(\omega t + \frac{\pi}{2})$

$$\cos \theta = \sin(\frac{\pi}{2} + \theta)$$

$$V_1 + V_2 + V_3 + V_4$$

Converting the standard sine waveform

$$\bar{V}_1 = \frac{V_0}{\sqrt{2}} \angle 0^\circ = \frac{25}{\sqrt{2}} \angle 0^\circ = 17.68 \angle 0^\circ$$

$$\bar{V}_2 = \frac{40}{\sqrt{2}} \angle 30^\circ = 7.07 \angle 30^\circ, \bar{V}_3 = 21.21 \angle 90^\circ$$

$$V_4 = 14.14 \angle -45^\circ$$

∴ For resultant voltage

$$V = \bar{V}_1 + \bar{V}_2 + \bar{V}_3 + \bar{V}_4$$

Addⁿ & Subⁿ \rightarrow Rectangular form
 Mult & Div \rightarrow Polar

Max Min
 1 min

$$V = (17.68 \angle 0^\circ) + (7.07 \angle 30^\circ) + (21.21 \angle 90^\circ) + (14.14 \angle 45^\circ)$$

$$V = \text{Rec}(17.68, 0) + \text{Rec}(7.07, 30) + \text{Rec}(21.21, 90) + \text{Rec}(14.14, 45)$$

$$= 17.68 + 0j + 6.12 + 3.5j + 0 + 21.21j + 10 - 10j$$

$$V = 33.80 + 14.75j \rightarrow \text{Rectangular}$$


$$\approx \text{Pol}(33.80, 44.75)$$

$$V = (36.88 \angle 23.58^\circ) V \rightarrow \text{Polar}$$

* Resistive Circuit

According to Ohm's law,
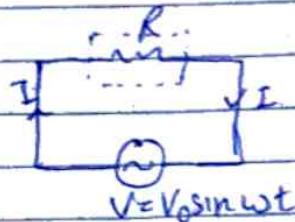
$$I = \frac{V}{R} = \frac{V_0 \sin \omega t}{R}$$



For maximum, $\sin \omega t \approx 1$

$$I_0 = \frac{V_0}{R}$$

$$\text{Instantaneous power } P = VI = V_0 \sin \omega t \cdot I_0 \sin \omega t$$

$$= V_0 I_0 \sin^2 \omega t$$

$$= V_0 I_0 \left(\frac{1 - \cos 2\omega t}{2} \right)$$

Imp.

$$P_{\text{inst}} = \frac{V_0 I_0}{2} - \frac{V_0 I_0 \cos 2\omega t}{2}$$

$$\text{Power consumed } (P) = \frac{1}{2\pi} \int_0^{2\pi} P d\omega t$$

$$= \frac{1}{2\pi} \int_0^{2\pi} \left[\frac{V_0 I_0}{2} - \frac{V_0 I_0 \cos 2\omega t}{2} \right] d\omega t$$

$$= \frac{1}{2\pi} \left[\frac{V_0 I_0}{2} \left[\int_0^{2\pi} d\omega t - \int_0^{2\pi} \cos 2\omega t d\omega t \right] \right]$$

$$= \frac{V_0 I_0}{4\pi} \left[(2\pi)^2 - \left(\frac{\sin 2\omega t}{2} \right)_0^{2\pi} \right]$$

$$= \frac{V_0 I_0}{4\pi} \times 2\pi$$

Ans

$$P_{\text{consumed}} = \frac{V_0 I_0}{2} = \frac{V_0}{\sqrt{2}} \frac{I_0}{\sqrt{2}} = V_{\text{rms}} I_{\text{rms}}$$


* Pure Inductive Circuit

$$I = I_0 \sin(\omega t - \frac{\pi}{2})$$



Current lagging behind the voltage by 90°



$$V = V_0 \sin \omega t$$

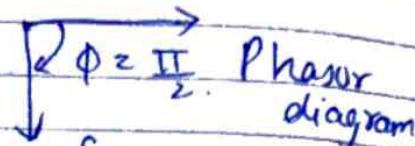

* Pure Capacitive Circuit

$$I = I_0 \sin(\omega t + \frac{\pi}{2})$$

Current leading Voltage by 90°

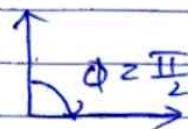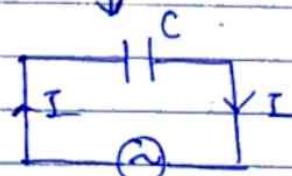

* Pure L circuit

- Opposition to current (Z):

$$Z = \frac{V_0}{I_0} = \frac{V_0}{\omega L}, \quad \frac{V_0}{I_0} = \omega L$$

Multiplying & Dividing by $\sqrt{2}$

$$\frac{V_0/\sqrt{2}}{I_0/\sqrt{2}} = \omega L$$

$$\frac{V}{I} = \omega L$$

~~Opposition to current~~

$$X_L = \omega L = 2\pi f L$$


Inductive Reactance

* Pure C circuit

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

Capacitive Reactance

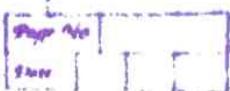Inductive \rightarrow lag $\rightarrow \frac{\pi}{2}$
Capacitive \rightarrow lead $\rightarrow -\frac{\pi}{2}$



AC circuits

Q8 A $318\text{ }\mu\text{F}$ capacitor is connected across a 230V , 50Hz supply. Determine
① Capacitive reactance
② RMS value of current
③ Equation for V & I

Ans) $C = 318 \times 10^{-6} \text{ F}$, $V = 230\text{V}$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 318 \times 10^{-6}} \\ X_C = 10 \Omega$$

$$I_{\text{RMS}} = \frac{V}{X_C} = \frac{230}{10} = 23\text{A}$$

$$V = V_0, V_0 = \sqrt{2} V = \sqrt{2} \times 230 = 325.27\text{V}$$

$$I_o = \sqrt{2} I = \sqrt{2} \times 23 = 32.53\text{A}$$

Equation for V and I

$$V = V_0 \sin \omega t = 325.27 \sin(2\pi \times 50)t$$

$$V = 325.27 \sin(314t)$$

$$I = I_o \sin \omega t = 32.53 \sin\left(314t + \frac{\pi}{2}\right)$$

* A.C series circuit.

- ① R-L circuit ② R-C circuit ③ R-L-C circuit

* Series R-L circuit

$$\checkmark V_R = IR$$

$$\checkmark V_L = IX_L$$

$$\checkmark \text{Power factor} = \cos \phi$$

$$\checkmark \phi = \tan^{-1} \left(\frac{V_L}{V_R} \right) \Rightarrow \text{Phase angle}$$

$$\checkmark Z = \sqrt{R^2 + X_L^2}$$

$$\checkmark Z = R + X_L j \approx Z \angle \phi$$

$$P_{\text{consumed}} = V I \cos \phi$$

* Series R-L-C circuit

$$V_R = IR$$


$$V_C = IX_C$$

$$\checkmark \text{ Power factor} = \cos \phi$$

$$\phi = \tan^{-1} \left(\frac{V_C}{V_R} \right) = \tan^{-1} \left(\frac{X_C}{R} \right)$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$Z = R - jX_C = Z \angle -\phi$$

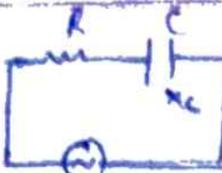

Q9 A coil having resistance of $7\ \Omega$ and inductance of $31.8\ \text{mH}$ is connected to $230\ \text{V}$, $50\ \text{Hz}$.

Calculate ① Circuit current ② Phase angle

③ Power factor ④ Power consumed

$$\text{Ans} 9) \quad ① X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 31.8 \times 10^{-3}$$

$$X_L = 10\ \Omega$$

$$② Z = \sqrt{R^2 + X_L^2} = \sqrt{7^2 + 10^2} = 12.21\ \Omega$$

$$③ I = \frac{V}{Z} = \frac{230}{12.21} = 18.84\ \text{A}$$

$$④ \phi = \tan^{-1} \left(\frac{X_L}{R} \right) = \tan^{-1} \left(\frac{10}{7} \right)$$

$$\phi = 55^\circ$$

$$⑤ \text{Power factor} = \cos 55^\circ = 0.574 \text{ (Lagging)}$$

$$⑥ P_{\text{consumed}} = V I \cos \phi$$

$$= 230 \times 18.84 \times 0.574$$

$$P_{\text{consumed}} = 2487.26\ \text{W}$$

series

* $\sim R-L-C$ circuit

$$① \text{Phase angle } (\phi) = \tan^{-1} \left(\frac{V_L - V_C}{V_R} \right) = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$$② Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = R + (X_L - X_C)j \quad \dots \text{Rectangular.}$$

$$Z = |Z| \angle \phi \quad \dots \text{Polar.}$$

- Q10 For given circuit, determine ① Circuit Impedance
 ② Circuit Current ③ Power factor ④ Active power
 $R = 20\Omega$, $L = 0.1H$, $C = 50\mu F$, $V = 200V$, $f = 50Hz$
 Ans) $X_L = 2\pi f L = 2\pi \times 50 \times 0.1$
 $X_L = 31.4\Omega$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}} \\ X_C = 63.69\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \\ Z = \sqrt{20^2 + (63.69 - 31.4)^2} \\ Z = \sqrt{400 + 1039.41}$$

$$Z = 37.93$$

$$Z = R - (X_C - X_L)j \\ Z = 20 - 32.24j \quad \text{... Rectangular} \\ Z = 37.94L - 58.19 \quad \text{... Polar}$$

~~$Z = 37.94 \angle -58.19$~~


$$I = \frac{V}{Z} = \frac{200}{37.94L - 58.19} = 5.27L 58.19$$

$$\text{Power factor} = \cos \phi = \cos(-58.19) = 0.527 \text{ (lagging)}$$

$$\text{Active Power} = P = VI \cos \phi \\ = 200(5.27)(0.527)$$


$$P = 555.46W$$

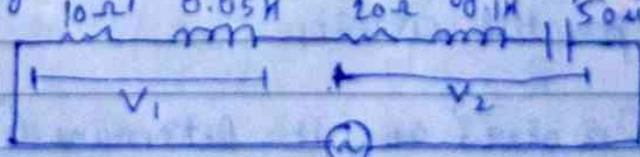- Q11 From given circuit, determine ① circuit current,
 ② Voltage drop V_1 ③ Voltage drop V_2



200V, 50Hz

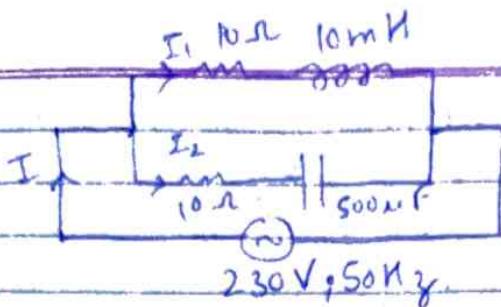- Ans) $R_1 = 10\Omega$, $L_1 = 0.05H$, $R_2 = 20\Omega$, $L_2 = 0.1H$, $C = 50\mu F$
 $X_{L_1} = 2\pi f L_1 = 2\pi \times 50 \times 0.05 = 15.7\Omega$
 $X_{L_2} = 31.4\Omega$
 $R_{eq} = 30\Omega$, $X_{L_{eq}} = 47.1\Omega$



$$\text{Ans} \quad X_L = 2\pi f L = 2\pi \times 3.14 \times 50 \times 10 \times 10^{-3} \Omega = 3.14 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 3.14 \times 50 \times 500 \times 10^{-6}} \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 3.14 \times 50 \times 500 \times 10^{-6}} \Omega = 6.37 \Omega$$

$$Z_1 = \sqrt{R^2 + (X_L)^2} = \sqrt{10^2 + (3.14)^2} \Omega = 10.48 \Omega$$

$$Z_2 = \sqrt{R^2 + (X_C)^2} = \sqrt{10^2 + (6.37)^2} \Omega = 11.85 \Omega$$

$$Z_1 \parallel Z_2$$

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{10.48} + \frac{1}{11.85} = \frac{22.33}{124.188}$$

$$Z_{eq} = \frac{124.188}{22.33} = 5.56 \Omega$$

$$I_{\text{total}} = \frac{V}{Z_{eq}} = \frac{230}{5.56} = 41.36 A$$

$$I_1 = \frac{V}{Z_1} = \frac{230}{10.48} = 21.95 A$$

$$I_2 = \frac{V}{Z_2} = \frac{230}{11.85} = 19.39$$

$$\text{Re} \quad \phi_1 = \tan^{-1} \left(\frac{X_L}{R} \right) = \tan^{-1} \left(\frac{3.14}{10} \right) = 17.43^\circ$$

$$\text{Power factor} = \cos \phi_1 = \cos 17.43^\circ = 0.954$$

$$\phi_2 = \tan^{-1} \left(\frac{X_C}{R} \right) = \tan^{-1} \left(\frac{6.37}{10} \right) = 32.49^\circ$$

$$\text{Power factor} = \cos \phi_2 = \cos 32.49^\circ = 0.843$$

Total power factor

$$\phi_f = \tan^{-1} \left(R \left(\frac{1}{X_L} - \frac{1}{X_C} \right) \right)$$

$$\phi_f = \tan^{-1} \left(10 \left(\frac{1}{3.14} - \frac{1}{6.37} \right) \right) = 0.447$$

$$\phi_L = \tan^{-1} \left(\frac{10(6.37 - 3.14)}{2\pi} \right)$$

$$= \tan^{-1}(1.615)$$

$$\phi_C = \tan^{-1} \left(\frac{(R+X_L)(X_C)}{R+X_L + R+X_C} \right)$$

$$= \tan^{-1} \left(\frac{10(13.14 \times 6.37)}{10 + 13.14 + 6.37} \right)$$

$$\cos \phi = \frac{P}{V}$$


$$\phi_r = \tan^{-1} \left[R \left(\frac{1}{X_L} - \frac{1}{X_C} \right) \right]$$

$$= \tan^{-1} \left[\frac{10}{2\pi} \left(6.37 - 3.14 \right) \right]$$

Power consumed = $P_1 = I_1^2 R = (21.45)^2 / 10 = 4.818 \text{ kW}$

$$P_2 = I_2^2 R = (19.39)^2 / 10 = 3.76 \text{ kW}$$

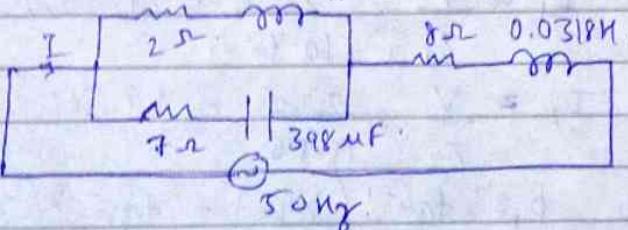Q13 Determine equivalent impedance of circuit.



Ans. $X_L = 2 \times 3.14 \times 50 \times 0.0191 = 6 \Omega$

$$X_C = \frac{1}{2 \times 3.14 \times 398 \times 10^{-6}} = 8 \Omega$$

$$Z_1 = 2 \times 3.14 \times 50 \times 0.0318 = 10 \Omega$$

$$Z_2 = \sqrt{4 + 36} = \sqrt{40} = 6.32 \Omega$$

$$Z_3 = \sqrt{49 + 64} = \sqrt{113} = 10.6 \Omega$$

$$Z' = 6.32 \times 12.8 = 4.23$$

$$Z_{eq} = Z' + \frac{6.32 + 12.8}{2}$$

16.95

Date _____

$$Z' = 3.96 \Omega$$

$$Z_T^2 = 3.96 + 12.80 = 16.76$$

* Resonance Circuit :-

Parameter | Series circuit

(1) Impedance

Parallel circuit

$$\text{Max } (Z = \frac{1}{CR})$$

(2) Current

$$\text{Min } (I = \frac{V}{Z_0})$$

(3) Resonant frequency

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$

$$f_R = \frac{1}{2\pi\sqrt{LC}} \cdot \frac{1}{L} \cdot \frac{L^2}{L^2}$$

(4) Q factor

$$Q = V_L \text{ or } Q_C$$


$$Q = I_L \text{ or } I_C$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{V}{I}$$

Q14 An inductive coil of resistance 20Ω and inductance 0.2 H is connected in parallel with $200 \mu\text{F}$ capacitor with var. freq., 230V supply. Find resonant freq at which total current taken from supply is in-phase with supply voltage. Also find the value of current

Ans

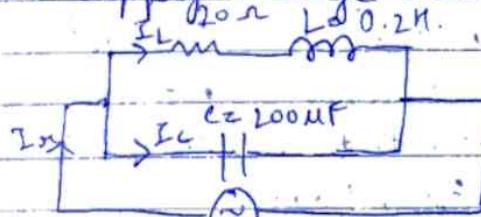

$230\text{V}, \text{fr}$

$$f_R = \frac{1}{2\pi\sqrt{LC}} \cdot \frac{1}{L} \cdot \frac{L^2}{L^2}$$

$$Z = \frac{1}{2\pi\sqrt{0.2 \times 200 \times 10^{-6}}} = \frac{1}{2\pi\sqrt{0.2^2}} = \frac{1}{2\pi\sqrt{0.2^2}} = 50 \Omega$$


$$= \frac{1}{2\pi} \sqrt{15000}$$

$$f_R = 59.49 \text{ Hz}$$

$$Z_T^2 = \frac{L}{CR} = \frac{0.2}{200 \times 10^{-6} \times 20} = 50 \Omega$$

$$I_T = \frac{V}{Z_T} = \frac{230}{50} = 4.6 \text{ A}$$

* Generation of Three Phase

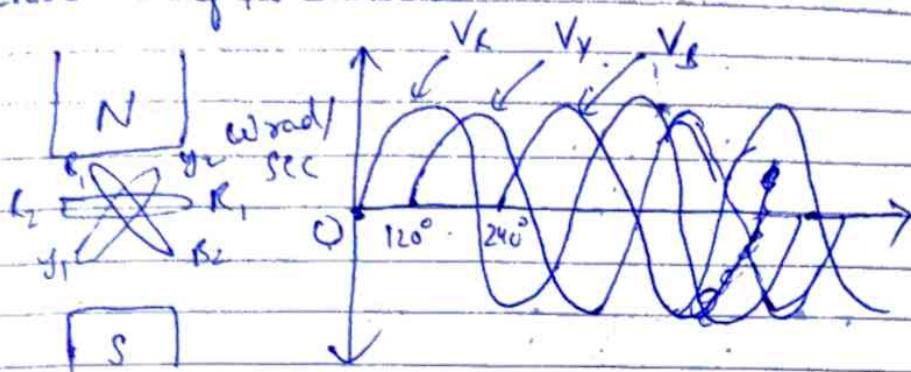


→ Equation for Voltages.

$$V_R = V_0 \sin \omega t$$

$$V_Y = V_0 \sin (\omega t - 120^\circ)$$
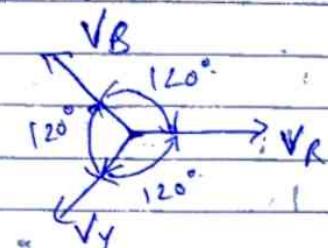
$$V_B = V_0 \sin (\omega t - 240^\circ)$$




(1) Phase Sequence
(2) Phase Voltage

(3) Phase Current
(4) Line Voltage

(5) Line Current

→ Star Connection

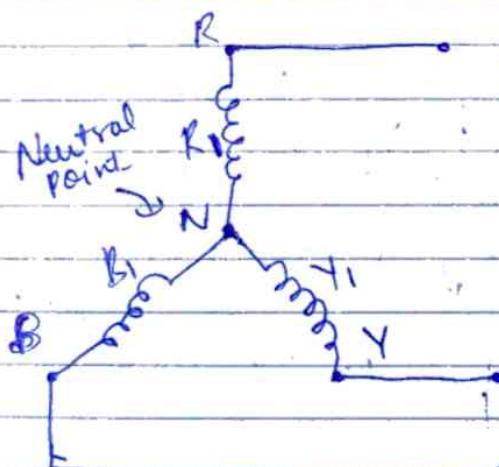

• Line Current ($I_L = I_{ph}$)

$$I_R = I_0 \sin \omega t$$

$$I_Y = I_0 \sin (\omega t - 120^\circ)$$

$$I_B = I_0 \sin (\omega t - 240^\circ)$$

• Line Voltage (V_L)

• V_{ph} = Phase Voltage

$$V_L = \sqrt{3} V_{ph}$$

• Power:-

Total power = $3 \times$ Power in each phase


$$= 3 V_{ph} I_{ph} \cos \phi$$

∴ For star connection:

$$V_L = \sqrt{3} V_{ph}$$

$$P = 3 \times \frac{V_L}{\sqrt{3}} \times I_L \cos \phi \quad [P = \sqrt{3} V_{ph} I_{ph} \cos \phi]$$

Delta connection

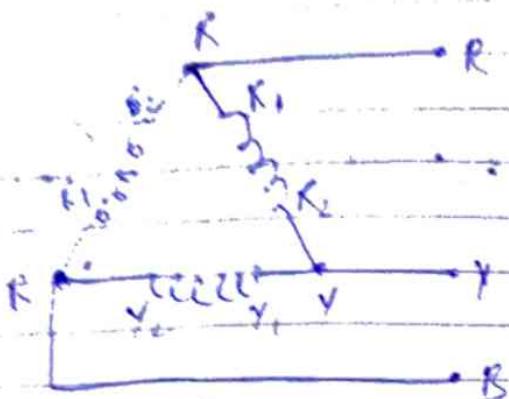

$$\text{Phase voltage} = V_{ph} = V_L$$

$$\text{Line current} = I_L = \sqrt{3} I_{ph}$$

$$\text{Power} = P = 3 \times V_{ph} \times I_{ph} \times \cos \phi$$

$$= 3 V_L I_L \frac{\cos \phi}{\sqrt{3}}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

* Comparison b/w Star & Delta

Star

$$V_L = \sqrt{3} V_{ph}$$

$$I_L = I_{ph}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

- ④ Line Voltage leads the resp. phase voltage by 30°

Delta

$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

- ④ Line current lags behind I_{ph} by 30° .

- Q8. Three similar coils, each of resistance 8Ω and inductance $0.02H$ are connected in Star. Across a 3 phase, 50 Hz , 230 V supply. Calculate the line Current, total Power.

$$\text{Active Power } P = \sqrt{3} V_L I_L \cos \phi$$

$$\text{Apparent Power } S = \sqrt{3} I_L V_L$$

$$\text{Reactive Power } Q = \sqrt{3} V_L I_L \sin \phi$$

Page No.	
Date	

Ans) $R_{ph} = 8\Omega, L = 0.02H, f = 50Hz, V_L = 230V$

$$X_L = 2\pi f L = 2\pi (50)(0.02) = 6.28\Omega$$

For star connection, $V_L = \sqrt{3} V_{ph}$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{230}{\sqrt{3}} = 132.79V$$

$$Z = 8 + j 6.28 = 10.1 \angle 38.13^\circ$$

~~$I_L = \frac{V_L}{Z} = \frac{230}{10.1} = 22.79A$~~ $I_{ph} = V_{ph} = 132.79 \angle 0^\circ$

$$= 10.1 \angle 38.13^\circ$$
$$= 13.14 \angle -38.13^\circ$$

$$I_L = I_{ph} = 13.14 \angle -38.13^\circ$$

$$P = \sqrt{3} V_L \bullet I_L \cos \phi = \sqrt{3} \times 230 \times 13.14 \cos(-38.13)$$
$$= 4117.98W$$