

Name: NAVEEN SHARMA

Enrol. No: 10519011722

"Analog Electronics"

IIOT-B2

"Assignment - III"

Q MOSFET Amplifier Configuration

(i) Common Source


(ii) Common Base

(iii) Common Drain

Sol<sup>n</sup>

(I) Common Source.

(1) Without Source Resistance

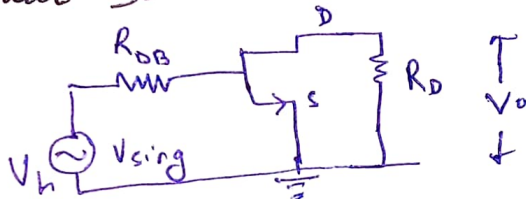

(i) Input resistance ( $R_{in}$ )

$$R = \frac{V}{i} \rightarrow 0$$

$$R_{in} = R_{gs} = \infty$$

(ii) Output Resistance ( $R_{out}$ )

$$R_{out} = r_o \parallel R_D$$

$$r_o \gg R_D$$

$$R_{out} = \frac{r_o R_D}{R_D + r_o} = \frac{r_o R_D}{r_o}$$

$$R_{out} = R_D$$

(iii) Voltage gain ( $A_v$ )

$$A_v = \frac{V_o}{V_{in}} = \frac{i_v (r_o \parallel R_D)}{V_{in}}$$

$$A_v = -g_m (r_o \parallel R_D) \quad \text{where } g_m = \frac{i_o}{V_{in}}$$


↓ transconductance

Overall gain:  $G_v$

$$G_v = \frac{V_o}{V_{sig}} = \frac{-i_a (r_o \parallel R_D)}{V_{gs}}$$

$$\text{Total gain transcond.} = G_v = -g_m (r_o \parallel R_D)$$

## II With Source Resistance

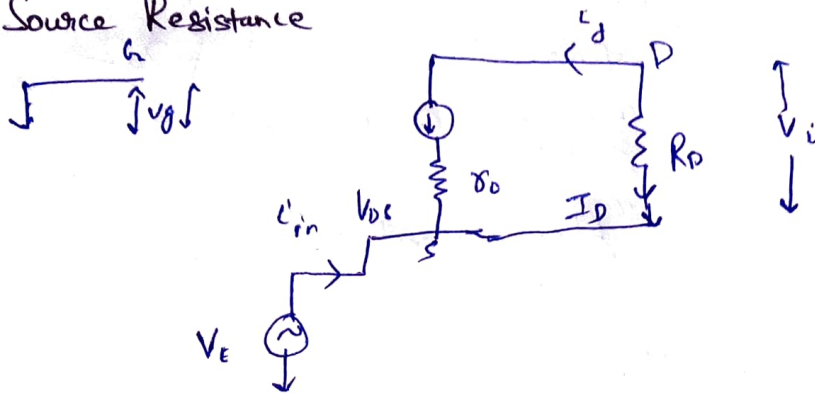

(i) Input Resistance

$$\frac{V_{in}}{i_{in}} = R_{in}$$

$$i_{in} + i_d = 0$$

$$\Rightarrow i_{in} = -i_d = -I_m V_{gs}$$

$$V_{gs} = -V_i$$

$$\Rightarrow V_{in} = r_o (g_m V_{gs} + i_{in})$$

$$V_{in} = r_o = g_m (-V_{in}) + r_o i_{in}$$

$$\frac{V_{in}}{i_{in}} = \frac{r_o}{1 + g_m r_o} = \left( \frac{1}{g_m} \parallel r_o \right)$$

(ii) Output Resistance

$$R_{out} = \frac{V_{in}}{i_{in}} \Big|_{v_{in}=0}$$

$$R_{out} = (r_o \parallel R_D)$$

$$R_{out} = R_D$$

(iii) Voltage Gain

$$V_{gs} = -V_i$$

$$V_D = (i_d - g_m V_{gs}) r_o + V_i$$


$$V_o = r_o i_d - g_m r_o V_i + V_i$$

$$V_o = -i_d R_D$$


$$V_o = -\frac{r_o}{R_D} V_o + (1 + g_m r_o) V_i$$

$$\Rightarrow A_v \cdot \frac{V_o}{V_i} = \frac{1 + g_m r_o}{1 + r_o/R_D}$$

## ⑧ Common Drain:

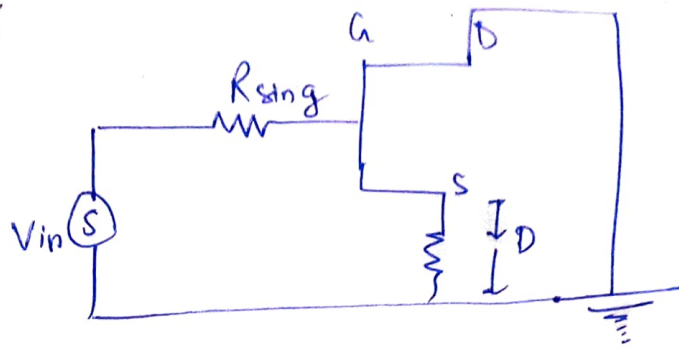

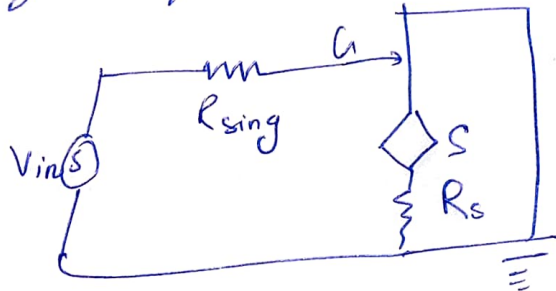→ Small Signal Equivalent Circuit Diagram



(i) Input Resistance ( $R_{in}$ )

$$R_{in} = R_{sig} = \infty$$

(ii) Output Resistance ( $R_{out}$ )

$$R_{out} = \frac{1}{g_m} \parallel R_s$$

$$\text{as } R_s \gg \frac{1}{g_m} \Rightarrow R_s \approx \frac{1}{g_m}$$

(iii) Voltage Gain ( $A_v$ )


Using Voltage divider formula

$$V_s = \frac{R_s}{R_s + 1/g_m} \cdot V_{in}$$

$$A_v = \frac{R_s}{R_s + 1/g_m} \cdot V_{in}$$

$$A_v = \frac{R_s}{R_s + 1/g_m} \cdot \frac{I_{DQ} V_{gs}}{I_{DQ} V_{gs}}$$

### 3. Common Gate

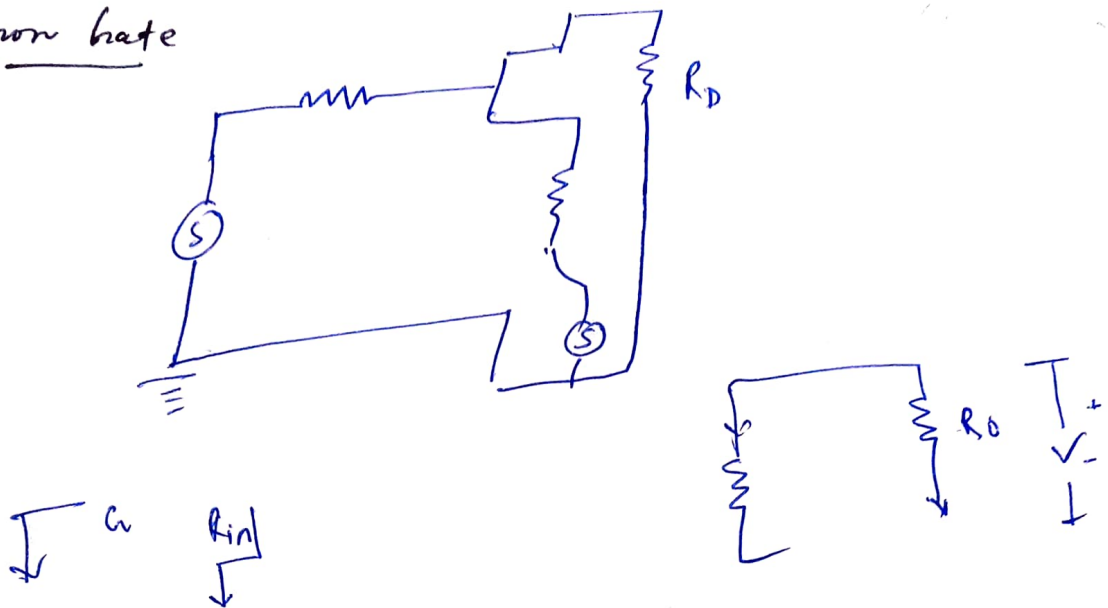

(i) Input Resistance

$$\frac{V_{in}}{i_{in}} = R_{in}$$

$$i_n \rightarrow i_d = 0$$

$$i_{in} = -i_d = -I_m V_{gs}$$

$$V_{gs} = -V_i$$

$$V_{in} = r_o (g_m V_{gs}) + i_{in}$$

$$V_{in} = r_o g_m (-V_{in}) + r_o i_{in}$$

$$\frac{V_{in}}{i_{in}} = \frac{-r_o}{1 + g_m r_o} = \left( \frac{1}{g_m} \parallel r_o \right)$$

(ii) Output Resistance

$$R_{out} = \frac{V_o}{i_{in}} \Big|_{v_{in}=0}$$

$$R_{out} = (r_o \parallel R_D)$$

$$R_{out} = R_D$$

(iii) Voltage Gain

$$V_{gs} = -V_i$$

$$V_D = (-i_d - g_m r_o V_i) + V_i$$

$$V_o = -i_d R_D$$

$$-\frac{r_o}{R_D} V_o = V_D + (1 + g_m r_o) V_i$$

$$A_v = \frac{V_o}{V_i} = \frac{1 + g_m r_o}{1 + r_o/R_D}$$